

Lab 5: Audio Amplifier

GOAL

To implement a two-stage audio amplifier (BJT common emitter + BJT emitter follower).

OBJECTIVES

To build, test, simulate, and understand an emitter follower to drive an audio speaker.

GENERAL GUIDELINES

- 1) Each student must build, test, and demo all circuits.
- 2) During the lab session, students may need to share test stations.
- 3) Students are allowed (even encouraged) to help each other. Hedrick and/or the lab teaching assistant will be around to help as well.
- 4) Ask questions! The more questions you ask, the more you learn (assuming Hedrick can provide adequate answers 😊).
- 5) Build your circuits with neat wiring and the correct wire colors.
- 6) Please keep your lab kit and work area organized.



Fig. 0: (Left) Small signal BJT (Center) Power BJT (Right) Audio speaker.

PARTS AND MATERIALS

- Lab kit (breadboard, wire stripper, wire)
- Circuit from Lab 3 (if you need to re-build, that's fine).
- Scope, scope probes, multimeter, function generator, coaxial cable (with alligator clips), benchtop power supply
- Transistors:
 - 2N3904 (1)
 - TIP 31 (1)
- Resistors:
 - 16 ohm (brown/blue/black) (1)
 - 68 ohm (blue/gray/black) (1)
 - 12 kohm (brown/red/orange) (1)
 - 33 kohm (orange/orange/orange) (1)
 - 100 kohm (brown/black/yellow) (1)
- Capacitors:
 - 10 uF (1), 470 uF (1)
- Audio speaker + cable

PART 1: COMMON EMITTER (STAGE 1 OF AUDIO AMPLIFIER)

- **Step 1a:** Rebuild the lab 4 circuit and ensure that it still works correctly.

- Do NOT cram your circuit into a tiny area!
- Use neat and color-coded wiring!
 - RED wire = +9V
 - BLACK wire = ground
 - YELLOW wire = everything else
- The 2N3904 pin diagram is on the course website.
- Careful with the orientation of C_{in} and C_{out} !
- The input comes from the function generator (NOT the microphone).

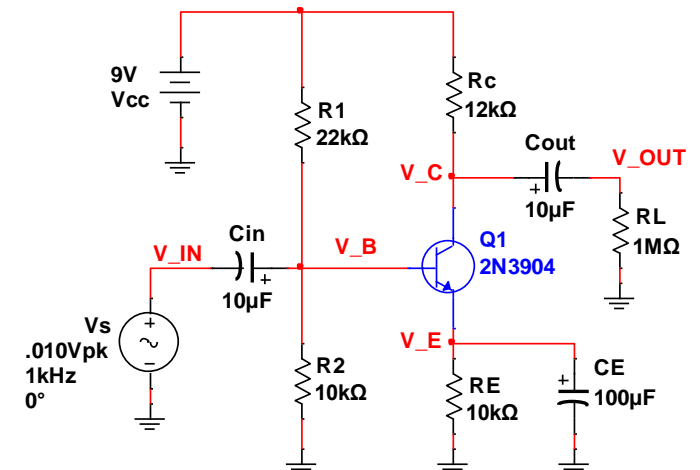


Fig. 1: Common emitter circuit from Lab 3. The input comes from the function generator (NOT the microphone).

- V_S is a sine wave (20 mV_{PP}, 1 kHz).
- Set the function generator to “High Z” (see Lab3 pdf, if necessary).
- Use a coaxial cable to connect the “SYNC” output to the scope’s “EXT TRIG” port.
- Configure the scope to measure V_{OUT} :
 - CH1 (measure V_{OUT}): Probe = 1X, BW Limit = ON
 - Trigger: Source = EXT, Level = 1V
 - Adjust the horizontal and vertical scales to see about two cycles of V_{OUT} .
 - V_{OUT} should be roughly 1.9 V_{PP} (can be higher or lower by 0.1V).

DO NOT DISASSEMBLE THIS CIRCUIT!

(End of Part 1)

PART 2: DARLINGTON FOLLOWER (STAGE 2 OF AUDIO AMPLIFIER)

The extra high β of a Darlington pair means the low speaker impedance (16 ohm) looks like a much larger impedance to the source (over 10 kohm!).

For this lab, we are using a “firm” divider, rather than a “stiff” divider, to bias the Darlington follower. A firm divider is defined by $R1/R2 < 0.1 (\beta+1)R_E$. A firm divider is nice because it raises the input impedance Z_{IN} by a factor of 10. This is highly useful for a variety of applications.

- **Step 2a:** On a different part of your breadboard, build the circuit (emitter follower) shown in Fig. 2.

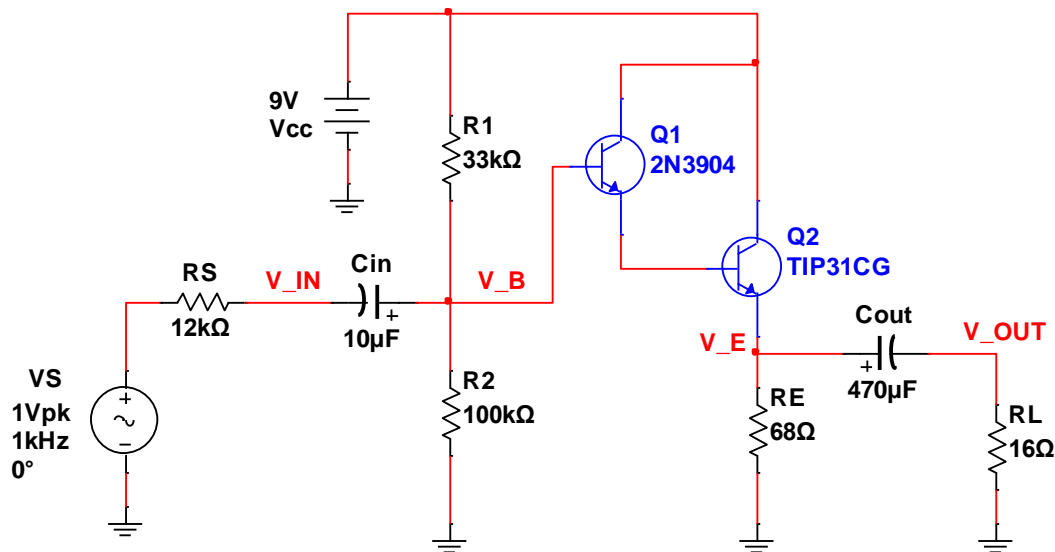


Fig. 2: Darlington follower using a 2N3904 with a TIP31 transistor. The input comes from the function generator ($2V_{PP}$ sine wave), while the load is a 16 ohm resistor. Do NOT use the speaker as the load (not yet).

- Do NOT cram your circuit into a tiny area! Consult Hedrick's breadboard, if necessary.
- V_S is a $2V_{PP}$ sine wave at 1 kHz.
- The $R_S = 12$ kohm resistor mimics the output impedance of the Lab3 common emitter circuit.
- Pay attention to the orientation of the electrolytic capacitors.
- The pin diagram for the 2N3904 and TIP31 transistors are on the course website.
- The load is a 16 ohm resistor (NOT the speaker – at least for now).

- **Step 2b:** Make some DC voltage measurements.

- Use the multimeter to measure the DC values of V_B and V_E . Enter these values into Table 1. They should be similar to your PreLab results!

Table I: DC operating point

V_{BB}	V_{EQ}

- **Step 2c:** Measure the voltage gain.

- Next, use the scope to measure the peak-to-peak values of V_{IN} and V_{OUT} . Enter these values into Table 2.
- Compute the voltage gain. It should be similar to your PreLab "Transient analysis" results!
- **Save scope traces of both V_{IN} and V_{OUT} and combine them into a single MATLAB plot for your report.**

Table II: Voltage Gain with $R_L = 16$ ohm

$V_{IN,PP}$	$V_{OUT,PP}$	Gain

• **Step 2d:** Measure the input impedance Z_{IN} of your emitter follower.

- The key concepts are the following:

- We know Z_S and Z_{IN} form a voltage divider where:

$$V_{IN} = V_S \times Z_{IN} / (Z_{IN} + Z_S) \quad (\text{Eqn. 1})$$

- If we know the values for V_S , V_{IN} , and Z_S , then we can solve Eqn. 1 for Z_{IN} .

- So how do we determine the values for V_{IN} , V_S , and Z_S ?

- You already have all the data you need!
- From Fig. 2, we know $V_S = 2V_{PP}$ (function generator output) and $Z_S = 12 \text{ kohm}$.
- We know V_{IN} (see your Table 2).
- Using your known values for V_S , Z_S and V_{IN} , use Eqn. 1 and some algebra to calculate Z_{IN} . Your Z_{IN} should be roughly 25 kohm (may be 5 kohm higher or lower).
- **Record your Z_{IN} for your lab demo and report.**

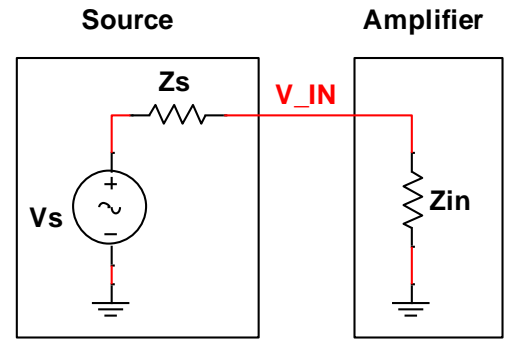


Fig. 3: General description of input impedance Z_{in} .

• **Step 2e:** Measure the output impedance Z_{OUT} of your emitter follower.

- The key concepts are the following:

- We know Z_{OUT} and R_L form a voltage divider where:

$$V_{OUT} = V_O \times R_L / (Z_{OUT} + R_L) \quad (\text{Eqn. 2})$$

- If we know the values for V_O , V_{OUT} , and R_L , then we can solve Eqn. 2 for Z_{OUT} .

- So how do we determine the values for V_O , V_{OUT} , and R_L ?

- You already have V_{OUT} and R_L (from Table 2).
- V_O is the open circuit output voltage of the amplifier.
 - Looking at Fig. 4, $R_L = \infty$ means $V_{OUT} = V_O$.
 - How to make $R_L = \infty$? Just remove the 16 ohm load resistor from the breadboard.
 - Use the **scope** to measure the peak-to-peak value of V_{OUT} . Your measurement is therefore V_O !
- Using your known values for V_O , V_{OUT} , and R_L , solve Eqn. 2 for Z_{OUT} . Your Z_{OUT} should be roughly 1.5 ohm (may be 0.5 ohm higher or lower).
- **Record your Z_{OUT} for your lab demo and report.**

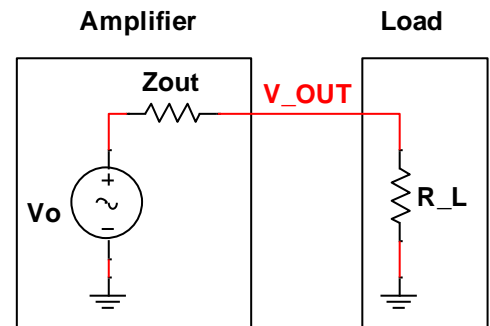


Fig. 4: General description of output impedance Z_{out} .

(End of Part 2)

PART 3: MULTISTAGE AMPLIFIER

OK, now we need to connect your two stages (common emitter and emitter follower) together to make an audio amplifier!

- **Step 3a:** Assemble the multistage amplifier following the steps below (see Fig. 5):
 - Emitter follower:
 - Move the function generator V_S to the common emitter input and set the amplitude to 20 mV_{PP} .
 - Remove the $R_S = 12\text{ kohm}$ resistor from the input.
 - Common emitter:
 - Remove the 1 Mohm load and 10 uF output coupling capacitor
 - Use a sort-of-long yellow wire to connect V_C to the emitter follower's input.
 - Your final two-stage amplifier should look like Fig. 5

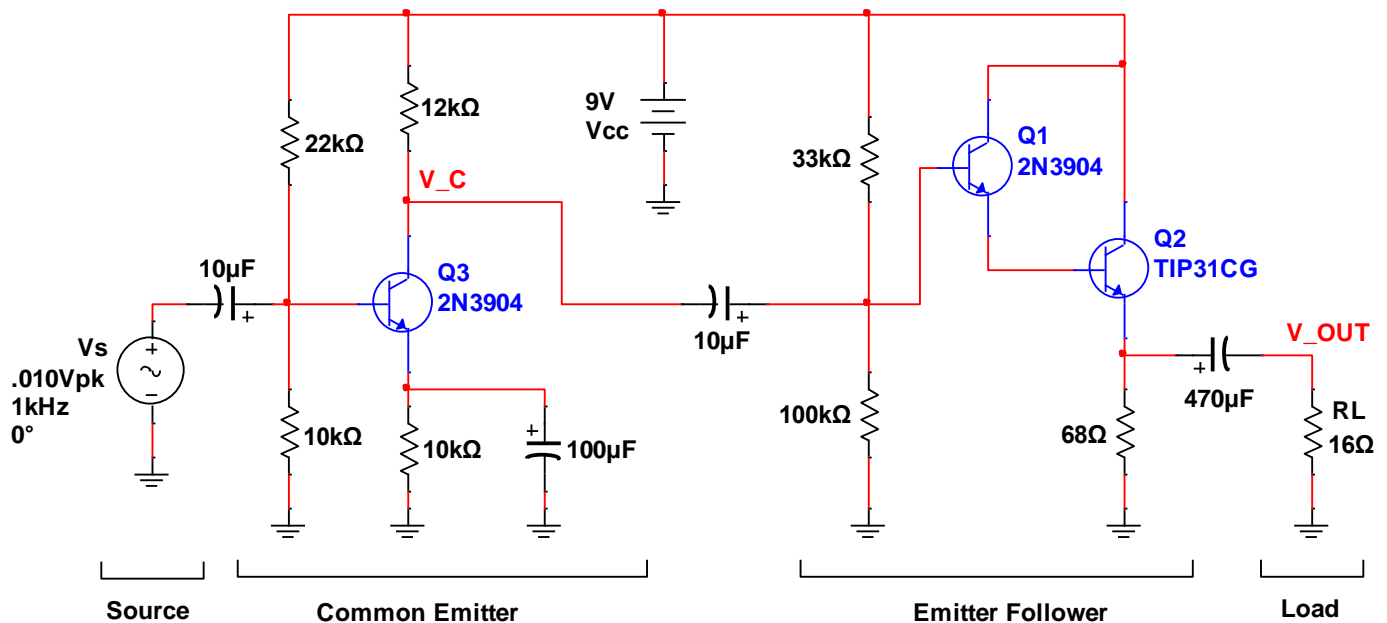


Fig. 5: Schematic of the multistage amplifier. The source V_S is the function generator while the load R_L is a 16 ohm resistor.

- **Step 3b:** Measure the overall gain of your circuit:
 - Measure the peak-to-peak value of V_{OUT} and complete Table 3.
 - You know $V_S = 20\text{ mV}_{PP}$, so compute the overall gain. It should be around -55 (may vary from -50 to -60).
 - Based on your overall gain (Table 3) and follower gain (Table 2), compute your common emitter gain. It should be roughly -60 .
 - Answer the following question: The common emitter gain is around -90 when its load is 1 Mohm . Why is the common emitter gain only -60 (roughly) in the multistage amplifier?

Table III: Overall voltage gain

$V_{OUT,PP}$	V_{OUT}/V_S

(End of Part 3)

PART 4: AUDIO AMPLIFIER

OK, now we can finally listen to some sounds!

- Step 4a: Make the following modifications to your breadboard:
 - Amplifier input:
 - Remove the function generator from the amplifier input.
 - Connect the audio cable to your breadboard.
 - The “red” wire goes to your amplifier input.
 - The “copper” wire goes to GND.
 - Insert the audio cable jack into your phone, or laptop, or the desktop computer.
 - Choose your music, or podcast, or whatever.
 - Set the volume VERY LOW.
 - Amplifier output:
 - Remove the 16 ohm load resistor.
 - Connect the audio speaker.
 - You will need two wires to connect the speaker’s two-pin socket to the breadboard.
 - If all goes well, you should hear stuff coming out of the speaker! 😊

(End of Lab 5)