

## Lab 7: MOSFET Switch Design

### GOAL

To understand how to build some circuits using MOSFET switches.

### OBJECTIVES

To build and test MOSFET switches for the following circuits:

- 1) LED night light
- 2) High-side load switch for fan.



Fig. 0: From left to right: Photocell, small-signal MOSFET, power MOSFET, 12V brushless DC fan.

### GENERAL GUIDELINES

The usual ...

# And

**There is no lab report to hand in. Just demonstrate your circuits.**

### PARTS AND MATERIALS

- Lab kit (breadboard, wire stripper, wire)
- Oscilloscope, scope probes, multimeter
- Function generator, coaxial cable (with alligator clips), benchtop power supply
- Transistors:
 

2N7000	(2)
IRF9520	(1)
- Resistors: **Your lab kit should already have all/most of the resistors for this lab:**

330 ohm (orange/orange/brown)	(1)
1 kohm (brown/black/red)	(1)
33 kohm (orange/orange/orange)	(1)
100 kohm (brown/black/yellow)	(1)
1.0 Mohm (yellow/purple/green)	(1)
- Photocell (1)
- Photocell cap (1)
- White LED (1)
- 12V DC fan (1)

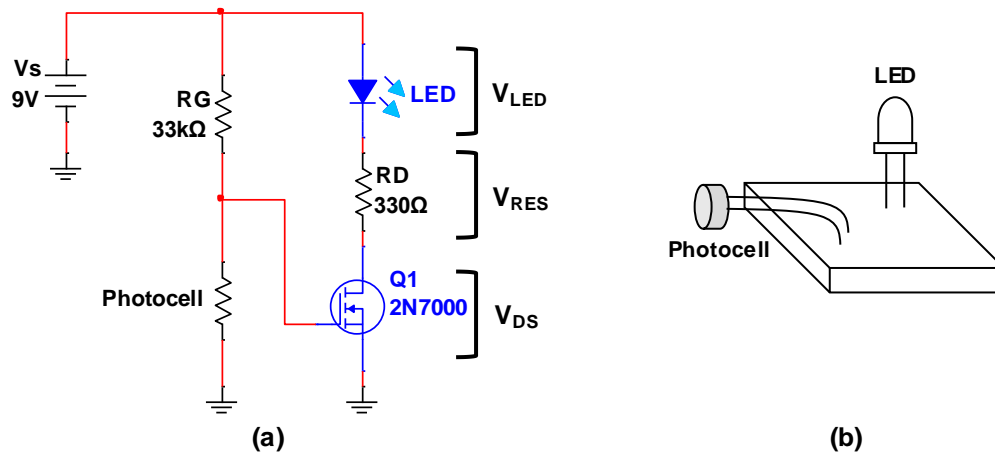
**PART 1: LED NIGHT LIGHT**

Fig. 1: (a) LED night light circuit. **DO NOT CLIP** the photocell leads. (b) Bend the photocell away from the LED.

- **Step 1a:** Build and test the circuit shown in Fig. 1a.
  - **Do NOT cram your circuit into a tiny area!**
  - See the course website for the 2N7000 pin diagram (data sheet).
  - The photocell is basically a resistor, so there is no “right” or “wrong” orientation.
    - **Do not clip the photocell leads! Bend the photocell to the side (see Fig. 1b).**
  - Wire the benchtop power supply to provide TWO outputs:
    - +9V is for the LED circuit. Set the max current of the power supply to 0.1A.
    - +12V is for the fan circuit. Set the max current to 3A.
  - The colored terminals on your breadboard should be the following:
    - RED terminal = +12V (use red wire on breadboard)
    - YELLOW terminal = +9V (use blue wire on breadboard)
    - GND terminal = GND (use black wire on breadboard)
  - The LED should turn on when you cover it with the black “photocell cap”.
  - Use the multimeter to complete Table 1 (see Fig. 1a for locations of  $V_{DS}$ ,  $V_{RES}$ , and  $V_{LED}$ ).
    - You should get  $V_{GATE} < 1V$  (bright),  $V_{GATE} > 4V$  (dark),  $V_{DS} < 200\text{ mV}$ ,  $V_{RES} \approx 6V$ ,  $V_{LED} \approx 3V$

**Table I: Multimeter measurements for LED night light ( $R_G = 33\text{ kohm}$ )**

Ambient = Bright	Ambient = Dark			
$V_{GATE}$	$V_{GATE}$	$V_{DS}$	$V_{RES}$	$V_{LED}$

- **Step 1b:** Test your circuit with two different values for  $R_G$ .
  - The purpose of this step is to see the different effects of using incorrect values for  $R_G$ .
  - Replace the 33 kohm resistor with  $R_G = 1$  kohm:
    - Is the LED always on or always off in bright and dark conditions?
    - Make the necessary multimeter measurements to complete the first row of Table 2.
      - You should get  $V_{GATE} > 5V$  for both bright and dark.
  - Replace the 1 kohm resistor with  $R_G = 1.0$  Mohm:
    - Is the LED always on or always off in bright and dark conditions?
    - Make the necessary multimeter measurements to complete the second row of Table 2.
      - You should get  $V_{GATE} < 2V$  for both bright and dark.

**Table II: Multimeter measurements with different  $R_G$**

$R_G$	$V_{GATE}$ (bright)	$V_{GATE}$ (dark)
1 kohm		
4.7 Mohm		

(see next page for Part 2)

## PART 2: HIGH-SIDE LOAD SWITCH FOR 12V FAN

- Step 2a: Build and test the circuit shown in Fig. 2.
  - **Do NOT cram your circuit into a tiny area!**
  - The IRF9520 pin diagram is on its data sheet (course website).
  - The control signal is the Agilent function generator with the following settings:
    - HighZ output
    - Configure a 5V DC signal (Press “Utility”, select “DC ON”, then enter “Offset = 5 VDC”).
    - Keep the “Output” button turned ON.

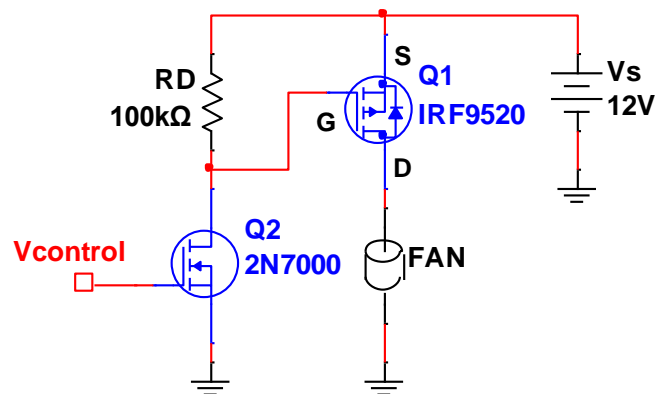


Fig. 2: High-side load switch for 12V fan. Q2 is a logic-level shifter while Q1 is the power MOSFET switch.

- **Your circuit works properly when the fan turns on (Offset = 5VDC) and off (Offset = 0V).**
  - Remember to avoid getting blown away by the fan.
- Use the multimeter to complete Table 3. See Fig. 2 for the gate (G), source (S), and drain (D) locations of Q1.
  - $V_{SD}$  is the voltage between the source and drain of Q1.
  - When the fan is ON, you should get  $V_{G1} < 20 \text{ mV}$ ,  $V_{SD} < 400 \text{ mV}$ ,  $I_D \approx 700 \text{ mA}$ .
  - When the fan is OFF, you should get  $V_{G1} \approx 12\text{V}$  and  $V_{SD} \approx 12\text{V}$ .
  - Use the appropriate multimeter range to get accurate measurements.

Table III: Multimeter measurements for fan switch.

Fan State	$V_{GATE}(Q1)$	$V_{SD}(Q1)$	$I_D(Q1)$
ON			
OFF			-----

## PART 3: CIRCUIT DEMOS

- LED night light
  - Show your completed Table 1 and 2.
  - Show that your LED properly turns on when the photocell is in darkness.
- Fan switch (Hedrick will NOT reset the function generator. Nice! 😊)
  - Show your completed Table 3.
  - Show that your fan properly turns on (Offset = 5V) and off (Offset = 0V).

(End of Lab 7)