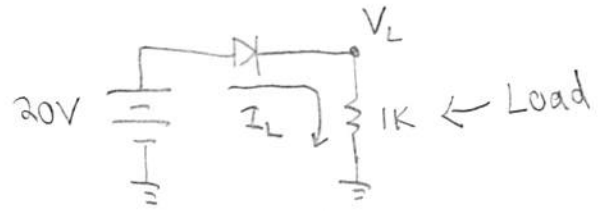


3.9

$$V_L = 20 - 0.7 = 19.3V$$



+6

$$I_L = \frac{V_L}{1k} = 19.3mA$$

$$P_L = I_L V_L = (19.3mA)(19.3V) = 372.5mW$$

$$P_D = I_L \times 0.7V = (19.3mA)(0.7V) = 13.5mW$$


$$P_T = P_L + P_D = 386mW = I_L \times 20V$$

3.11

$$V_L = 12 - 0.7 = 11.3V$$

+6

$$I_L = \frac{V_L}{470} = 24mA$$

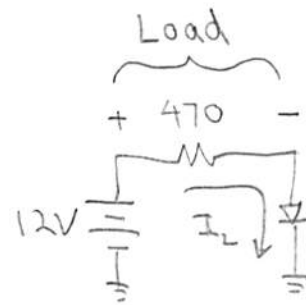

$$P_L = I_L V_L = (24mA)(11.3V) = 271.2mW$$

$$P_D = I_L \times 0.7V = (24mA)(0.7V) = 16.8mW$$

$$P_T = P_L + P_D = 288mW = I_L \times 12V$$

3.28

$$I = \frac{5 - 0.7}{R} = 20mA$$

+5

$$R = \frac{4.3V}{20mA} = 0.215k = 215\Omega$$



3.29 (6)


Since we know  $I_D$ ,

$$V' = I_D \times 5K + 0.7V$$

$$= (0.25 \text{ mA})(5K) + 0.7V = 1.95V$$

By KCL,  $I_a = I_1 - I_D = \frac{12 - 1.95}{30K} - 0.25 \text{ mA}$
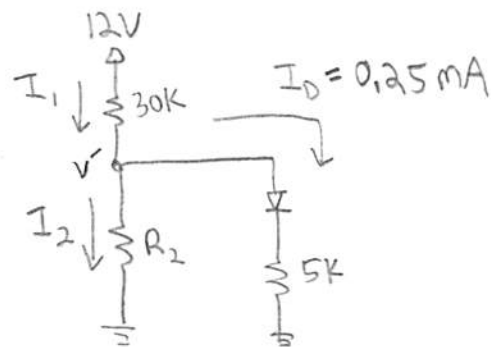
$$= 0.085 \text{ mA} = \frac{V'}{R_2} = \frac{1.95V}{R_2} \Rightarrow R_2 = \frac{1.95V}{0.085 \text{ mA}} = 22.9K \sim \boxed{23K}$$



3.33

(6)

• When 15V source is ON,


• D1 is ON and D2 is OFF

⇒ Load sees 14.3V

• When 15V source is OFF,

• D1 is OFF and D2 is ON

⇒ Load sees 11.3V

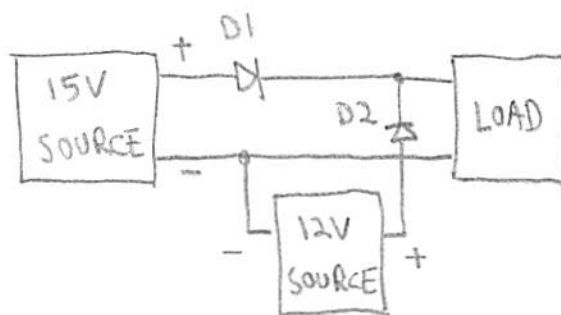

4.3

Need peak  $V_{OUT}$ , so we need peak  $V_{IN}$



+6

$$50 V_{rms} = \frac{1}{\sqrt{2}} V_{peak}$$

$$\Rightarrow V_{peak} = 50 \times \sqrt{2} = 70.7V$$

$$\Rightarrow V_{OUT,p} = 70.7 - 0.7 = \boxed{70V}$$
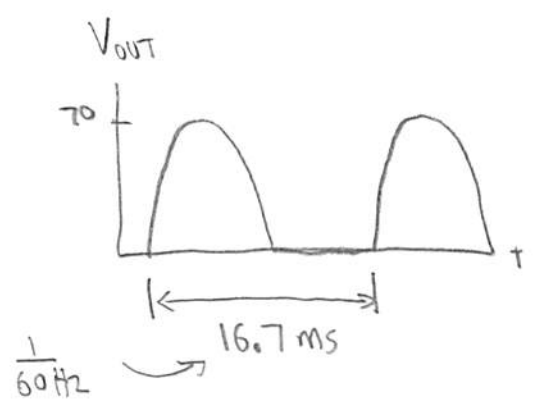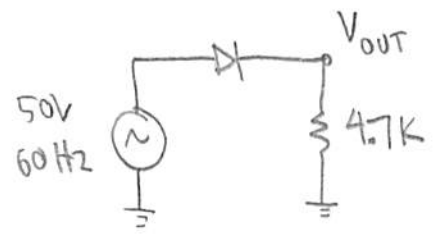
$$V_{AVG} = V_{DC} = \frac{V_{OUT,p}}{\pi} = \boxed{22.3V}$$



4.4



$$V_{peak,IN} = 15 \times \sqrt{2} = 21.2V$$

+6

Negative output peak is:

$$V_{OUT,p} = -21.2 + 0.7 = \boxed{-20.5V}$$
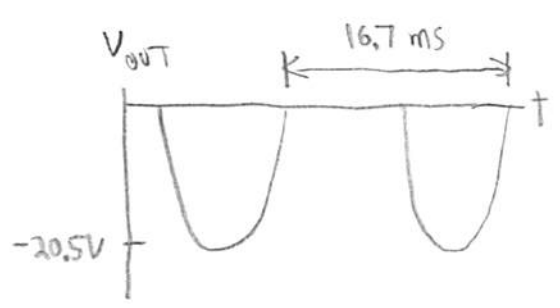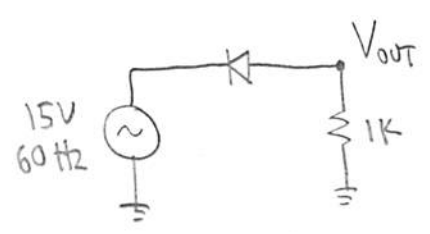
$$V_{DC} = \frac{-20.5}{\pi} = \boxed{-6.5V}$$



4.17



+6

$$V_{s,peak} = \frac{1}{8} \times V_{LINE,p}$$

$$= \frac{1}{8} \times \sqrt{2} \times 120V = 21.2V$$

$$V_{OUT,p} = 21.2 - 0.7 = \boxed{20.5V}$$
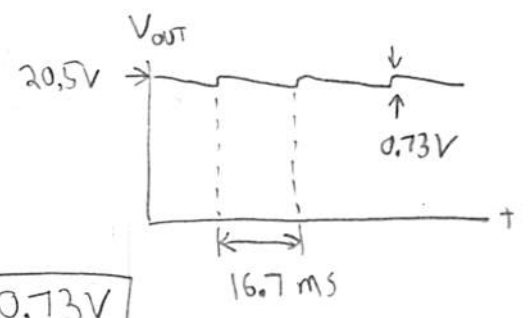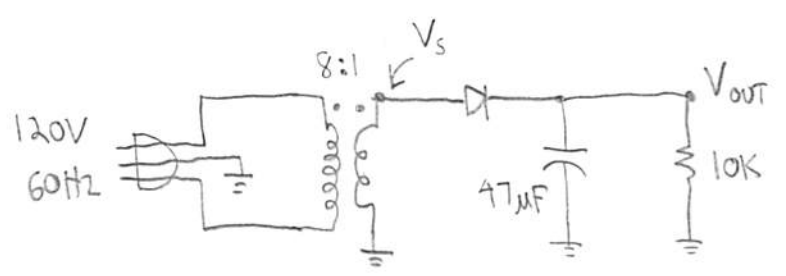
$$V_{ripple} = \frac{V_{OUT,p}}{R_L} \frac{1}{fC} = \frac{20.5V}{10^4 \Omega} \times \frac{1}{(60Hz)(47 \times 10^{-6} F)} = \boxed{0.73V}$$




4.20

+6

Since  $V_{ripple} = \frac{V_{peak}}{R} \frac{1}{fC}$   $\left( \frac{500\Omega}{10000\Omega} = \frac{1}{20} \right)$

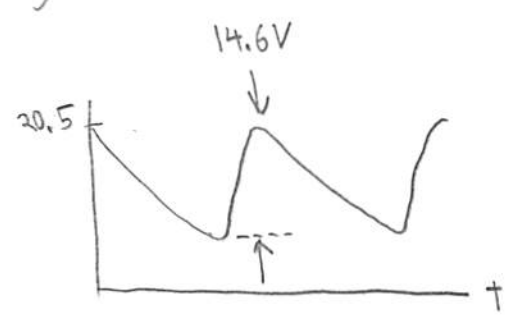If R is reduced by 20,  
then  $V_{ripple}$  increases by 20  
due to larger current draw.




$V_{ripple} = 20 \times 0.73V = \boxed{14.6V}$  ! Not a good DC supply ☹

4.xx

+6

$$V_{dc} = \frac{1}{T} \int_0^T V_p(t) dt$$
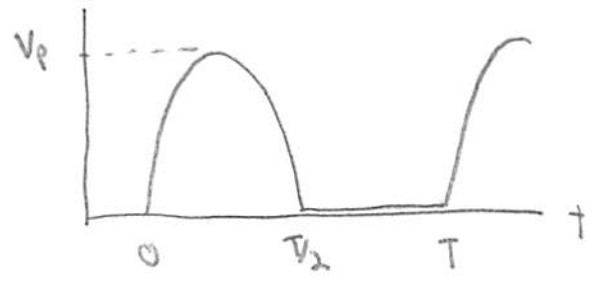
$$= \frac{1}{T} \int_0^{T/2} V_p \sin 2\pi f t dt$$



~~$+\frac{1}{T} \int_{T/2}^T 0 dt$~~

$$= \frac{1}{T} \times \frac{V_p}{-2\pi f} \cos 2\pi f t \Big|_0^{T/2} = \frac{-V_p}{2\pi f T} [\cos \pi f T - \cos 0]$$

Since  $f = \frac{1}{T} \Rightarrow fT = 1 \Rightarrow V_{dc} = \frac{-V_p}{2\pi} [\cos \pi - 1]$

$V_{dc} = \frac{V_p}{\pi}$  ✓



4.33 Positive clipper chops off above 0.7V

+6

For  $V_{IN} < 0.7V$ , diode is OFF

$$V_L = V_{IN} \times \frac{10k}{10k+1k}$$

When  $V_{IN} = -50V$ ,  $V_L = -45.5V$

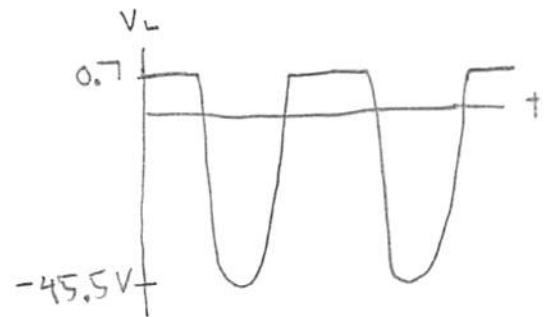
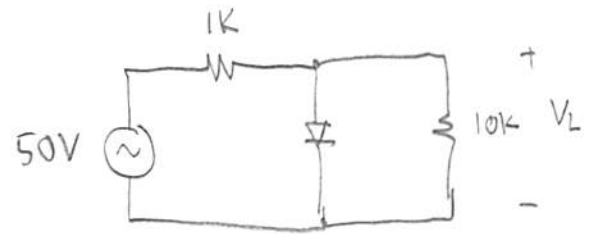


4.34 Negative clipper clamps at -0.7V

+6

When  $V_{IN} > -0.7V$ ,  $V_L = V_{IN} \times \frac{10k}{10k+1k}$

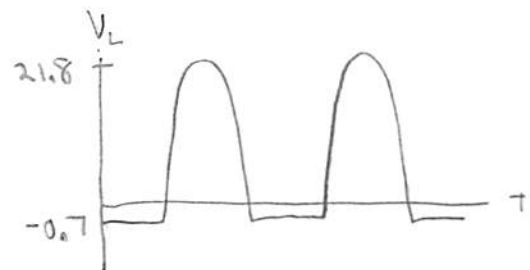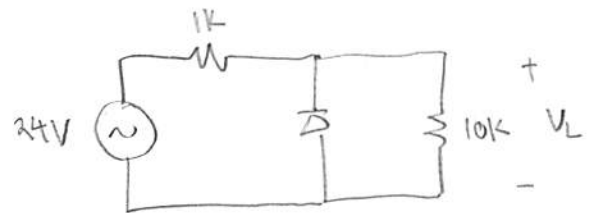
When  $V_{IN} = 24V$ ,  $V_L = 24 \times \frac{10}{11} = 21.8V$



4.35

Limiting levels are  $\pm 1.4V$


+5

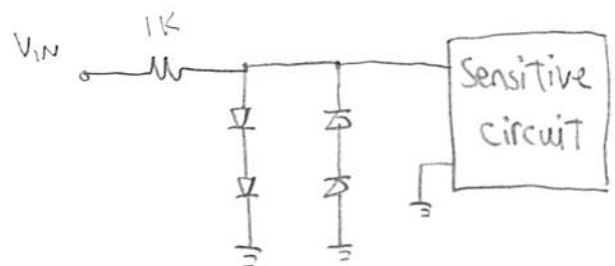

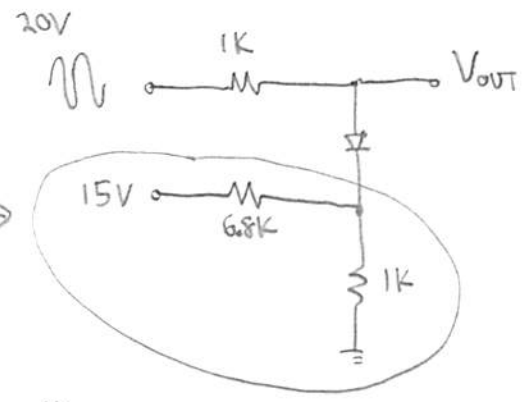
4.36

+6


To find max voltage, need to determine Thevenin equivalent of voltage divider




open circuit voltage:

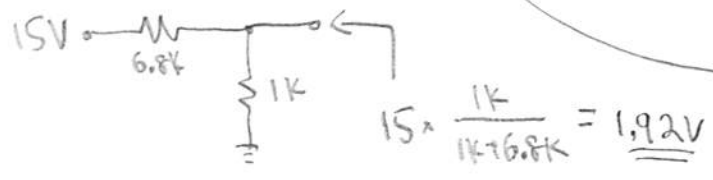

Equivalent resistance:

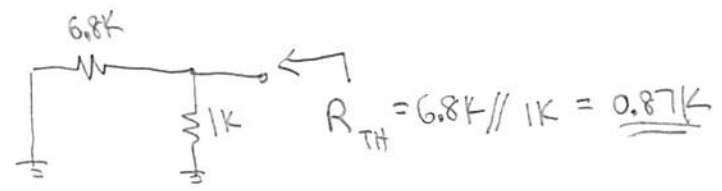

New circuit looks like:

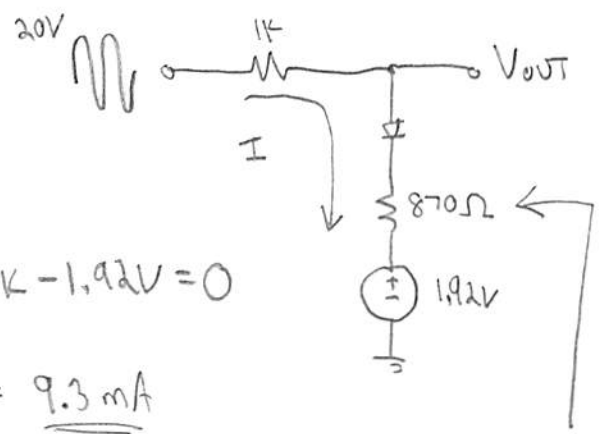

use KVL:

$$20V - I \times 1K - 0.7 - I \times 0.87K - 1.92V = 0$$

$$I = \frac{20 - 0.7 - 1.92V}{1.87K} = \underline{9.3mA}$$

$$V_{OUT,MAX} = 20V - (9.3mA)(1K)$$


$$= \boxed{10.7V}$$

This resistor causes \$V\_{OUT}\$ to NOT be clamped at  $1.92 + 0.7 = 2.62V!$

Max negative \$V\_{OUT}\$?

Diode is OFF
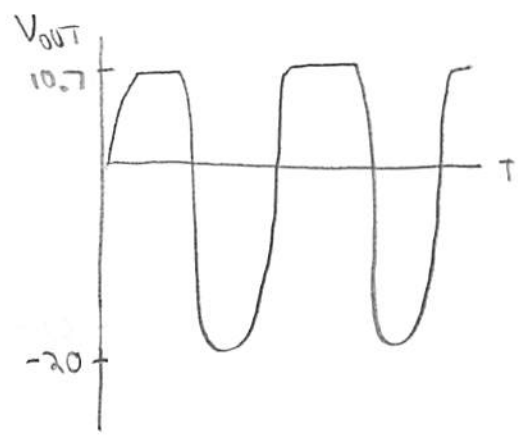
$$\rightarrow V_{OUT} = V_{IN} = \boxed{-20V}$$





4.38

+6

$$V_{MAX} = 2V_p - 0.7 = 30 - 0.7 = 29.3V$$

$$V_{MIN} = -0.7V$$

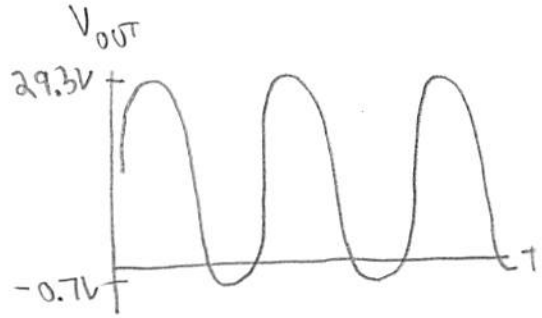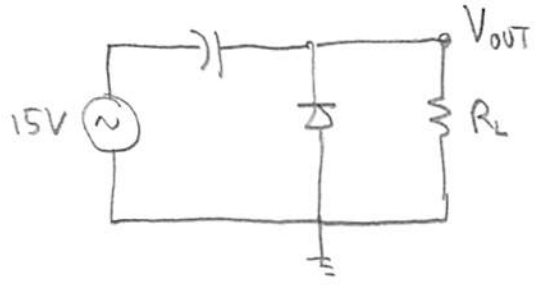



4.39

+6

This is a negative clamper!

$$V_{MAX} = +0.7V$$

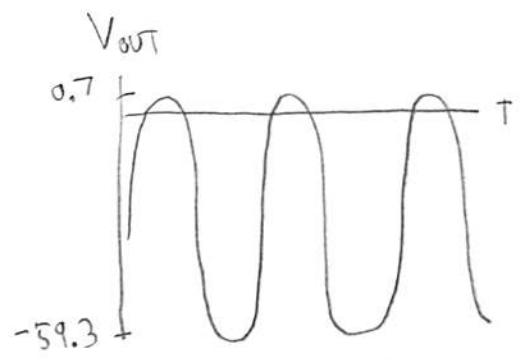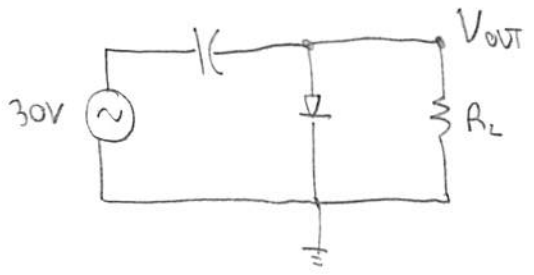
$$V_{MIN} = -(2V_p - 0.7) = -(60 - 0.7) = -59.3V$$



+6

4.40

• Ideal diodes have zero voltage drop

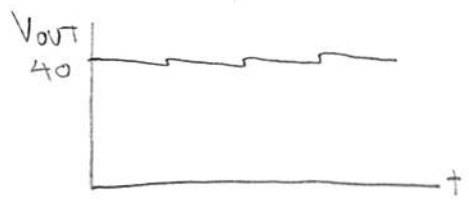

• second approx includes 0.7V drop

