

ECE 248  
HW 3 Solutions


Total = 100 pts

6.5

+7

$$I_B = \frac{10 - 0.7}{470K} = \boxed{.0198 \text{ mA}}$$

$$= 19.8 \mu\text{A}$$

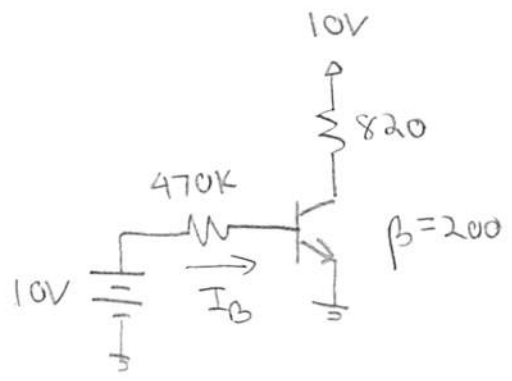

6.8


+7

$$V_{CE} = V_C - V_{E \rightarrow 0}$$

$$= V_C$$

$$= V_{CC} - I_C R_C$$
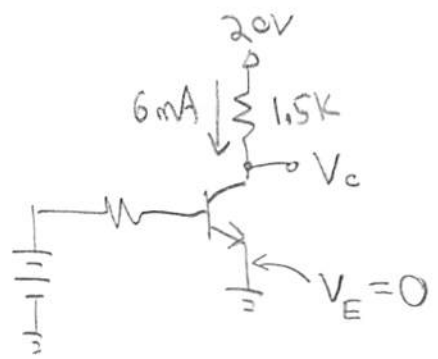
$$= 20 - (6 \text{ mA})(1.5K) = \boxed{11 \text{ V}}$$



6.30


+8

$$V_{CE} = V_C - V_{E \rightarrow 0}$$

$$= V_{CC} - I_C R_C$$

$$= V_{CC} - \beta I_B R_C$$
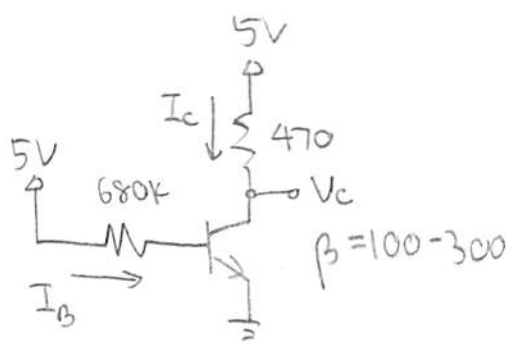
$$\uparrow I_B = \frac{5 - 0.7}{680K} = .0063 \text{ mA}$$



$$\beta = 100: V_{CE} = 5 - 100 \times .0063 \text{ mA} \times .47K = \boxed{4.7 \text{ V}}$$


$$\beta = 300: V_{CE} = 5 - 300 \times .0063 \text{ mA} \times .47K = \boxed{4.11 \text{ V}}$$

7.xx Need to find  $V_{CE}$

$$\begin{aligned} \textcircled{+7} \quad V_{CE} &= V_C - V_E \\ &= V_{CC} - I_C R_C \\ &= V_{CC} - \beta I_B R_C \end{aligned}$$

$$\uparrow \frac{9 - 0.7}{82K} = 0.101 \text{ mA}$$
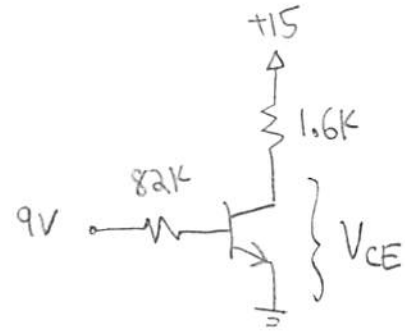
$$= 15 - 100 \times 0.1 \text{ mA} \times 1.6K = \underline{\underline{-1.2V}} < 0$$



NOT in active mode!


7.yy  $\textcircled{+16}$

a) stiff divider?

$$10K // 2.2K = 1.8K$$

$$\frac{200+1}{100} \times 1K = 2.01K$$

YES

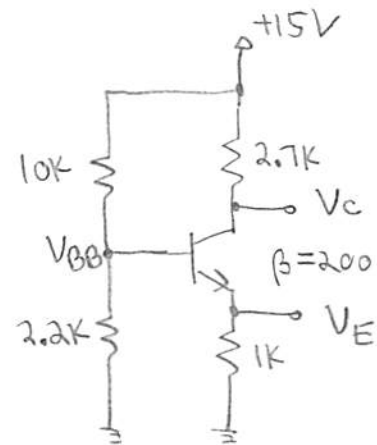

$$\textcircled{b} \quad V_{BB} = 15 \frac{2.2K}{2.2K + 10K} = \underline{\underline{2.7V}}$$

$$\alpha = \frac{200}{201} = 0.995$$

$$\textcircled{c} \quad V_{CQ} = V_{CC} - I_{CQ} R_C = V_{CC} - \alpha I_{EQ} R_C$$

$$\uparrow \frac{2.7 - 0.7}{1K} = 2 \text{ mA}$$

$$= 15 - 0.995 \times 2 \text{ mA} \times 2.7K$$

$$= \underline{\underline{9.63V}}$$

$$\textcircled{d} \quad V_{CEQ} = V_{CQ} - V_{EQ} = 9.63 - 2 = \underline{\underline{7.63V}}$$

$$\uparrow 2.7 - 0.7 = 2V$$

7.22 (+16)


(a) Thevenize the divider!

$$V_{TH} = 12 \cdot \frac{33K}{33K + 150K} = \boxed{2.16V}$$

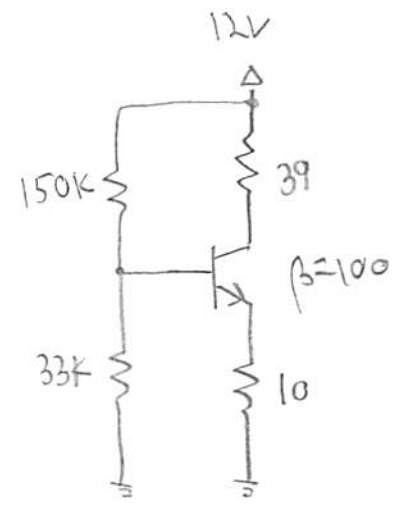(b)  $R_{TH} = 150K \parallel 33K = \underline{\underline{27K}}$

$$\frac{\beta + 1}{100} \cdot .010K = \frac{101}{100} \cdot .010K = \underline{\underline{.01K}}$$

27K > .01K! Divider is nowhere close to being stiff!




(c) KVL:

$$2.16 - I_B \cdot 27K - 0.7 - I_E \cdot 10 = 0$$

$\uparrow$   
 $(\beta + 1)I_B$

Method 1

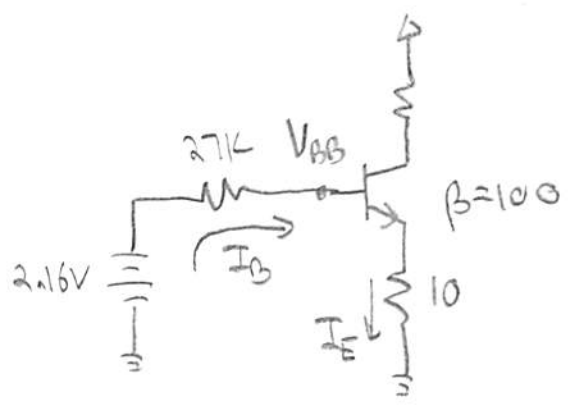

$$I_B = \frac{2.16 - 0.7}{27K + 101 \cdot .010K} = .052mA$$

$$V_{BB} = 2.16 - I_B \cdot 27K = 2.16 - .052mA \cdot 27K = \boxed{0.75V}$$

Base Current:

$$I_B = \frac{2.16 - V_{BB}}{27K} = \frac{1}{\beta + 1} I_E = \frac{V_{BB} - 0.7}{(101) \cdot .010K}$$


Method 2

$$.081 - .037V_{BB} = V_{BB} - 0.7$$
$$V_{BB} = \underline{\underline{0.75V}}$$

8.19

(16)

For AC equivalent circuit:

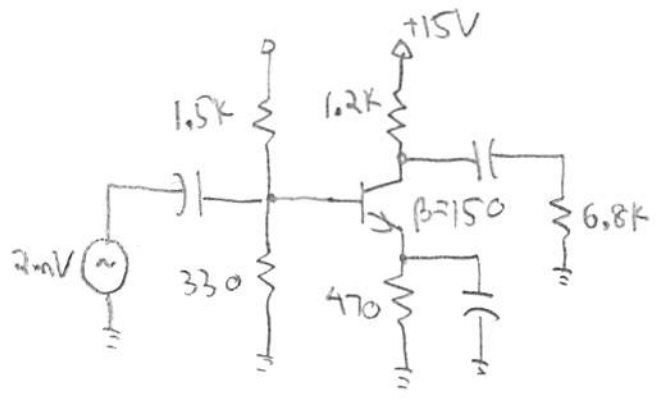

① All DC voltages become AC grounds

②  $R_c \parallel R_L = r_c = 1.2k \parallel 6.8k = \underline{\underline{1.02k}}$

$R_1 \parallel R_2 = 1.5k \parallel .33k = \underline{\underline{.271k}}$


③ Use T-model  $\leftarrow$  need  $r_e'$

Stiff divider?  $1.5k \parallel .33k = .271k$   
 $\frac{150+1}{100} \times .47k = .71k$  ] ✓

$\rightarrow V_{BB} = 15 \frac{330}{330+1500} = 2.71V$

$\Rightarrow I_{EQ} = \frac{2.71 - 0.7}{470} = .0043A \Rightarrow r_e' = \frac{.026}{.0043A} = \underline{\underline{6.1\Omega}}$

AC circuit

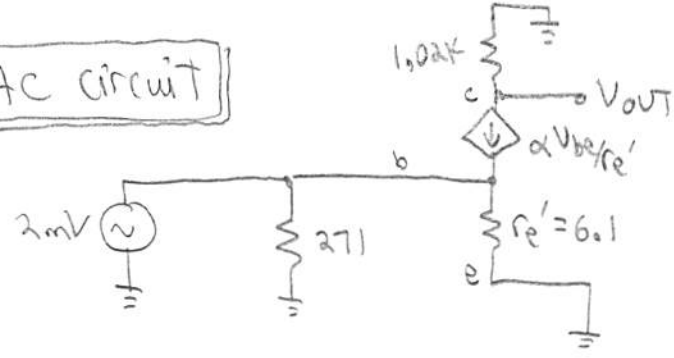

8.0XX

(17)

$\frac{V_{out}}{V_{in}} = -\alpha \frac{r_c}{r_e'} = -.995 \frac{1020}{6.1} = \underline{\underline{-166.4}}$

$\frac{200}{201} = .995$

8.44

+16

$$\textcircled{a} \bullet r_c = R_c // R_L$$

$$= 10\text{K} // 100\text{K} = \underline{\underline{9.1\text{K}}}$$


$$\bullet R_1 // R_2 = 10\text{K} // 1.2\text{K} = \underline{\underline{1.07\text{K}}}$$

$$\bullet \text{stiff divider? } \left. \begin{array}{l} 10\text{K} // 1.2\text{K} = 1.07\text{K} \\ \frac{201}{100} \cdot 1.5\text{K} = 3\text{K} \end{array} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{1.2\text{K}}{1.2\text{K} + 10\text{K}} = 1.61\text{V}$$

$$\Rightarrow I_{EQ} = \frac{1.61 - 0.7}{1.5\text{K}} = 0.61\text{mA} \Rightarrow r_e' = \frac{0.026}{0.61 \times 10^{-3}\text{A}} = \underline{\underline{42.6\Omega}}$$

AC circuit

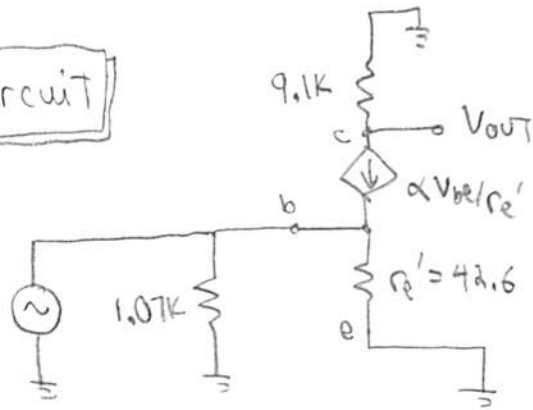

$$\textcircled{b} \frac{V_{OUT}}{V_{IN}} = -\alpha \frac{r_c}{r_e'} = -0.995 \frac{9.1\text{K}}{0.0426\text{K}} = \underline{\underline{-212.6}}$$

$$\textcircled{c} r_c = 10\text{K} // 1\text{K} = \underline{\underline{0.91\text{K}}}$$

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = -0.995 \frac{0.91\text{K}}{0.0426\text{K}} = \underline{\underline{-21.3}}$$

