

Union College
ECE 248
Spring 2018
Assignment 5

Due Wednesday June 6, 2018

Unless otherwise noted, all problems from Malvino & Bates (8th ed). Some problems have a “Multisim” label – ignore this and work out the calculations on paper.

A. Maximum undistorted output

- 8.w Compute the maximum peak (MP) output of the swamped common emitter in Fig. 8-36 (page 323). Draw the DC and AC load lines (see page 370 in the textbook and lab 7). Assume $\beta = 200$ (do not use 100). You should get an MP around 2.9 V.
- 9.x Compute the maximum peak (MP) output of the emitter follower in Fig. 9-28 (page 361). Draw the DC and AC load lines (see page 380 in the textbook). Assume $\beta = 150$. You should get an MP = 5.2V (approximately).
- 9.y For the same circuit as Problem 9.x, suppose the source V_g is a $14V_{PP}$ sine wave at 2 kHz. Using your results from Problem 9.x, sketch both V_g and V_{LOAD} over a 1 ms time interval. Label important features (e.g. amplitude and time)!
- 10.3 Assume $\beta = 200$ and remember MPP (max peak-to-peak) = $2MP$. You should get $MPP = 10.6V_{PP}$.
- 10.z For the same circuit as Problem 10.3, suppose the source V_g is a $10 mV_{PP}$ sine wave at 2 kHz. Using your results from Problem 10.3, sketch both V_g and V_{LOAD} over a 1 ms time interval. Label important features (e.g. amplitude and time)!

B. BJT switches

- 6.x Design a npn BJT driver for a white LED ($V_F = 3.5 \text{ V @ } 25 \text{ mA}$), as shown in Fig. 1a. Assume the control signal is 0 to +3.5V, and $V_{CC} = +5 \text{ V}$. Choose standard 5% resistor values (see course website for a table) for R and R_B . Choose R such that I_{LED} is NOT greater than 25 mA.
- 6.y You want to use a microcontroller (0 to +5V output signal) with an “internally driven” piezo buzzer (6 VDC @ 120 mA). Design a npn BJT driver powered by a 9V battery, as shown in Fig. 1b. Choose standard 5% resistor values. Make sure I_{PIEZO} is NOT $> 120 \text{ mA}$.

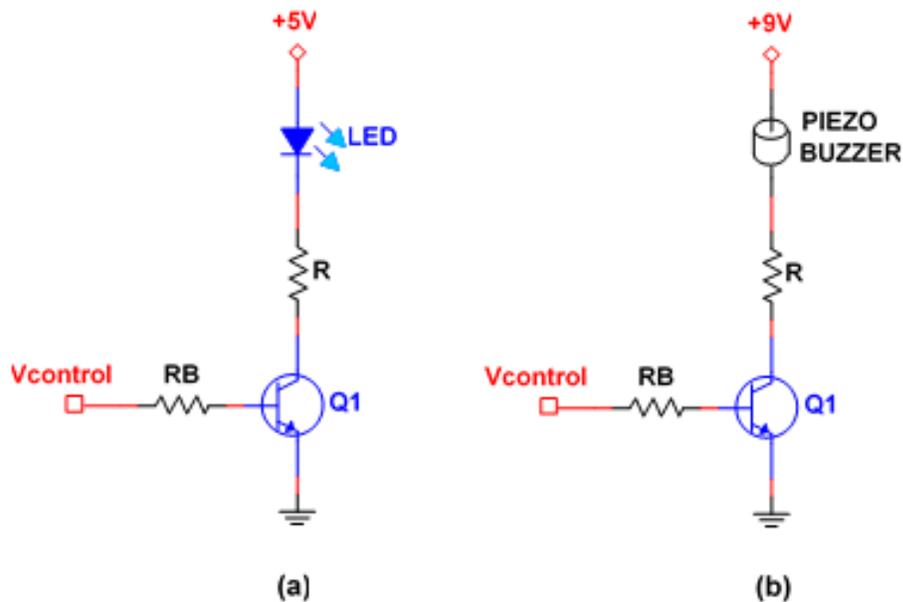


Fig. 1: (a) Circuit for Problem 6.x (b) Circuit for Problem 6.y

C. MOSFET ohmic region

- 12.11 Remember to check ohmic region!
- 12.14 Assume the LED has a forward voltage $V_F = 2V$. You should get $I_D = 27.8 \text{ mA}$. Check ohmic region!
- 12.15 Remember to check ohmic region!

D. Power FETs

- 12.27 Don't forget to check ohmic region!
- 12.34 Assume $I_{D,ON} = 5A$ when checking for ohmic region.

E. Frequency Response

- 14.33 "Base-coupling circuit" means C_{IN} . Your answer should be approximately 118 Hz (this assumes $r_e' = .026/I_{EQ}$)
- 14.34 "Collector coupling circuit" means C_{OUT} . Your answer should be approximately 2.5 Hz
- 14.35 "Emitter-bypass circuit" means C_E . Your answer should be approximately 273 Hz (this assumes $r_e' = .026/I_{EQ}$)