

ECE 248

HW2 Solutions

Total = 100 pts


4.9

$$V_{\text{upper}} = \frac{120}{4} \times \frac{1}{2} = 15 V_{\text{rms}}$$

+9

$$V_{\text{peak}} = 15 \sqrt{2} = 21.2 V_p$$
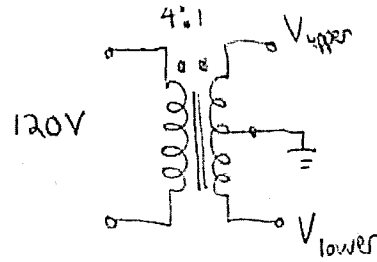
$$V_{\text{lower}} = \frac{120}{4} \times \frac{1}{2} = 15 V_{\text{rms}}$$





4.11 +9

$$\text{Peak } V_s = \frac{120V}{7} \times \frac{1}{2} \times \sqrt{2} = 12.1V$$

$$\text{Peak } V_{\text{out}} = 12.1 - 0.7 = 11.4 V_p$$
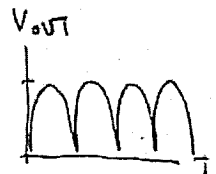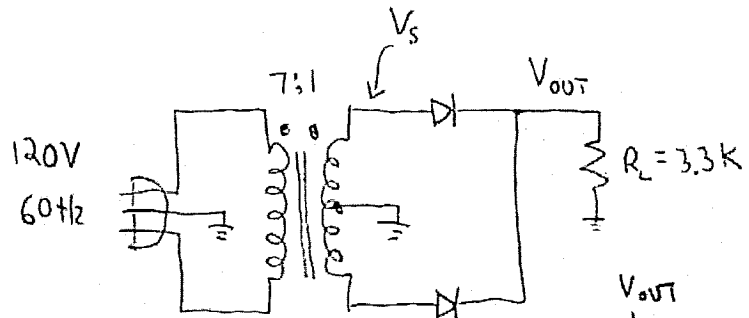
$$\text{Average value} = \text{DC Value} = 2 \times \frac{11.4}{\pi} = 7.3V$$




4.14 +9

Minimum DC  
output voltage

$$V_{\text{min}} = \left( \frac{105}{8} \times \sqrt{2} - 1.4 \right) \times \frac{2}{\pi} = 10.9V$$


Max DC  
output voltage
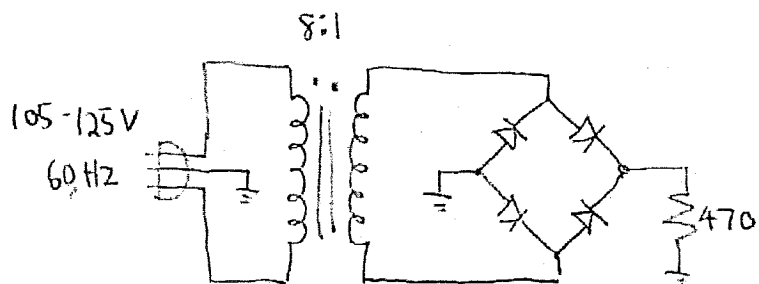
$$V_{\text{max}} = \left( \frac{125}{8} \times \sqrt{2} - 1.4 \right) \times \frac{2}{\pi} = 13.2V$$



A-xx

+5

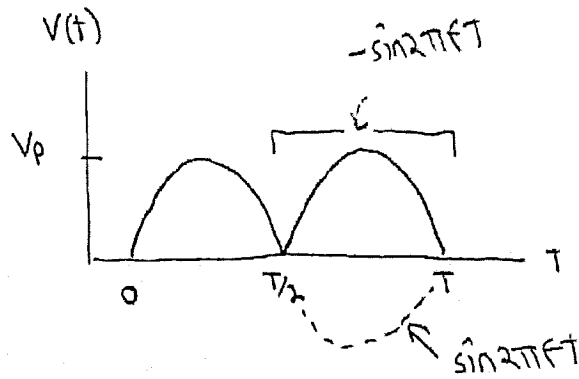

$$\langle V \rangle = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{T} \left[ \int_0^{T/2} V_p \sin 2\pi f t dt + \int_{T/2}^T V_p (-\sin 2\pi f t) dt \right]$$

$$= \frac{V_p}{T} \left[ \frac{-1}{2\pi f} \cos 2\pi f t \Big|_0^{T/2} + \frac{1}{2\pi f} \cos 2\pi f t \Big|_{T/2}^T \right]$$

$$= \frac{V_p}{2\pi f T} \left[ -(\underbrace{\cos \pi - \cos 0}_{-2}) + (\underbrace{\cos 2\pi - \cos \pi}_{2}) \right]$$

$$= \frac{4V_p}{2\pi} = \boxed{\frac{2V_p}{\pi}} \quad \checkmark$$


4.45 (+9)

$$V^+ = \left[ \frac{120}{8} \sqrt{2} \times \frac{1}{2} \right] - 0.7$$

$$= \boxed{9.9V}$$

$$V^- = - \left[ \frac{120}{8} \sqrt{2} \times \frac{1}{2} \right] + 0.7$$

$$= \boxed{-9.9V}$$

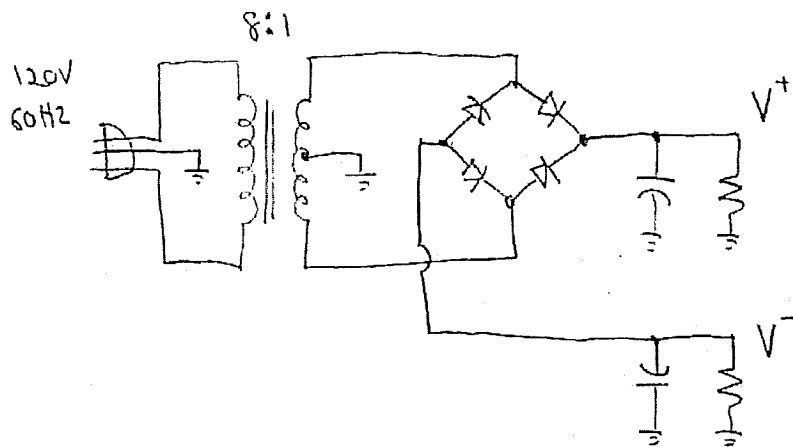


5.5 (+9)

$$I_s = \frac{24 - 15}{470} = \boxed{19.1 \text{ mA}}$$

$$I_L = \frac{15}{1.5K} = \boxed{10 \text{ mA}}$$
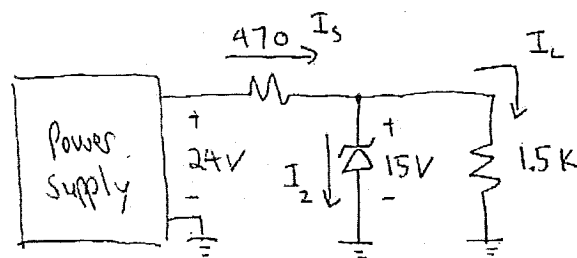
$$I_z = I_s - I_L = \boxed{9.1 \text{ mA}}$$



5.6 Max zener current involves lowest  $R_s$  and highest  $R_L$ .

$$I_{s, \max} = \frac{24 - 15}{.95 \times 470} = \underline{\underline{20.2 \text{ mA}}}$$

$$I_{L, \min} = \frac{15}{1.05 \times 1.5K} = \underline{\underline{9.5 \text{ mA}}}$$

$$I_{z, \max} = I_{s, \max} - I_{L, \min} = \boxed{10.7 \text{ mA}}$$

5.7 Max zener current involves highest supply


$$I_{s, \max} = \frac{40 - 15}{470} = \underline{\underline{53.2 \text{ mA}}}$$

$$I_L = \frac{15}{1.5K} = \underline{\underline{10 \text{ mA}}}$$

$$I_{z, \max} = I_{s, \max} - I_L = \boxed{43.2 \text{ mA}}$$

5.11

+9

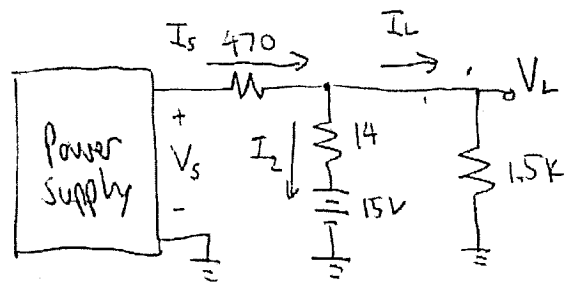

$$I_s = I_2 + I_L$$

$$\frac{V_s - V_L}{470} = \frac{V_L - 15}{14} + \frac{V_L}{1500}$$

$$\frac{V_s}{470} + \frac{15}{14} = \left( \frac{1}{470} + \frac{1}{14} + \frac{1}{1500} \right) V_L = .074 V_L$$

$$V_L = \frac{1}{.074} \left( \frac{V_s}{470} + \frac{15}{14} \right)$$

$$V_s = 21.5V \rightarrow V_L = \boxed{15.1V}$$

$$V_s = 25V \rightarrow V_L = \boxed{15.2V}$$

5.12

+5


Drop out occurs when  $I_2 = 0$

$$\rightarrow I_s = I_L$$

$$\frac{V_s - 15}{470} = \frac{15}{1500}$$

$$V_s = \left( \frac{15}{1500} + \frac{15}{470} \right) 470 = \boxed{19.7V}$$

← Voltage regulation is completely gone.

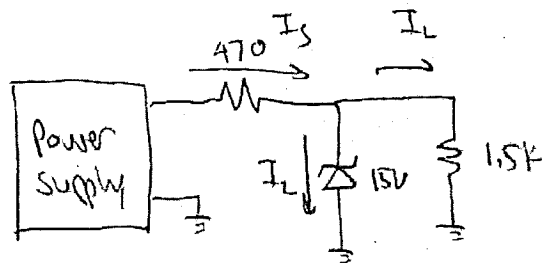

Note: Regulation becomes poor when  $I_2 \leq 10 \text{ mA}$

5.13 (+9)


worst case scenario:

$$I_z = I_s - I_L$$

$$= \frac{20-15}{470} - \frac{15}{500}$$

$$= 10.6 \text{ mA} - 30 \text{ mA} = -19.4 \text{ mA} < 0 \text{!}$$

YES, the zener regulator will fail. :(

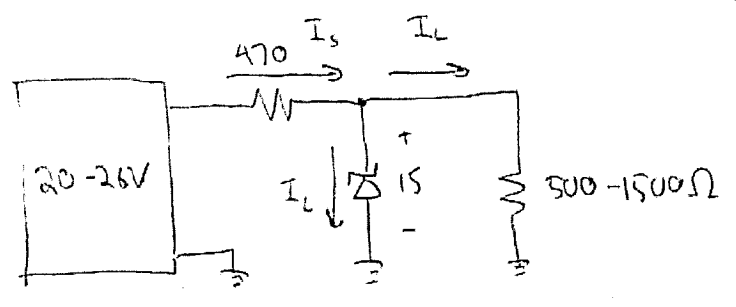

worst  $I_{z,min} = 0 = \frac{20-15}{R_{s,max}} - \frac{15}{500}$

$$R_{s,max} = (20-15) \frac{500}{15} = 167 \Omega$$

NOTE: In practice, \$R\_s\$ should be lower than this to keep \$I\_z > 10 \text{ mA}\$.

5.14 (+9)


worst case scenario:

$$I_z = I_s - I_L$$

$$= \frac{18-15}{470} - 25 \text{ mA}$$

$$= -18.6 \text{ mA} < 0 \text{!}$$

YES, the zener will fail. :(

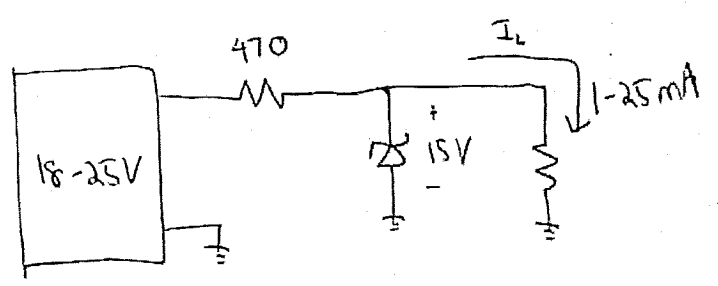

worst  $I_{z,min} = 0 = \frac{18-15}{R_{s,max}} - 25 \text{ mA}$

$$R_{s,max} = \frac{3}{25 \text{ mA}} = 0.12 \text{ k} = 120 \Omega$$

NOTE: In practice, \$R\_s\$ should be lower than this to keep \$I\_z > 10 \text{ mA}\$.

D. 4-yy Diode datasheets

4-yy Suppose that the lab you are doing specifies that you use a 1N4002 diode but you only have 1N4003 diodes. Use the datasheet on the WEB site to determine if the 1N4003 diodes will work. Explain your answer.

See pages 110 to 113 in your textbook

The difference between the 1N4002 and the 1N4003 is that the 1N4002 has a PIV of 100 V and the 1N4003 has a PIV of 200V

Section 4-7 defines PIV as:

The maximum voltage across the reverse biased diode. This voltage must be below the specified PIV for the diode or the diode will be destroyed.

In the circuit in lab 1 has a  $V_{pk}$  of less than 5 Vpk and in lab 2 a  $V_{pk}$  of less than 20 Vpk so either the 1N4002 or 1n4003 will work.