

8.17 $R_{base} = (\beta + 1) r_e'$

(+8)


Stiff divider?

$$\left. \begin{aligned} 1.5K // .33K &= 0.27K \\ \frac{201}{100} \cdot .94K &= 1.89K \end{aligned} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{.33K}{.33K + 1.5K} = 2.7V$$

$$\Rightarrow I_{EQ} = \frac{2.7 - 0.7}{.94K} = 2.1mA \Rightarrow r_e' = \frac{.026}{.0021A} = 12.4\Omega$$
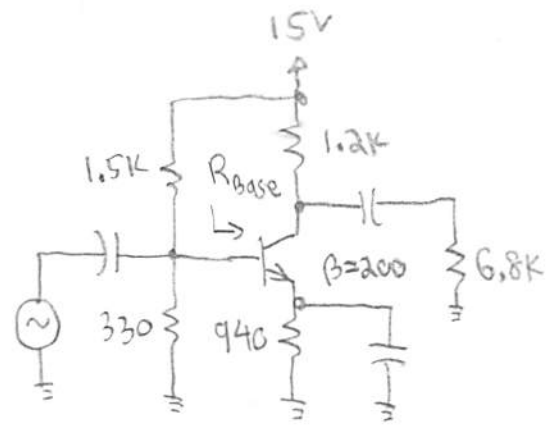
$$R_{base} = (201)(12.4\Omega) = 2492\Omega$$



8.18

(+8)

$R_{base} = (\beta + 1) r_e'$


Stiff divider?

$$\left. \begin{aligned} 1.5K // .33K &= 0.27K \\ \text{vs.} \\ \frac{201}{100} \cdot .47K &= 0.94K \end{aligned} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{.33K}{.33K + 1.5K} = 2.7V$$

$$\Rightarrow I_{EQ} = \frac{2.7 - 0.7}{.470} = 4.26 \times 10^{-3} A \Rightarrow r_e' = \frac{.026}{.00426} = 6.1\Omega$$


$$R_{base} = (201)(6.1) = 1226\Omega$$

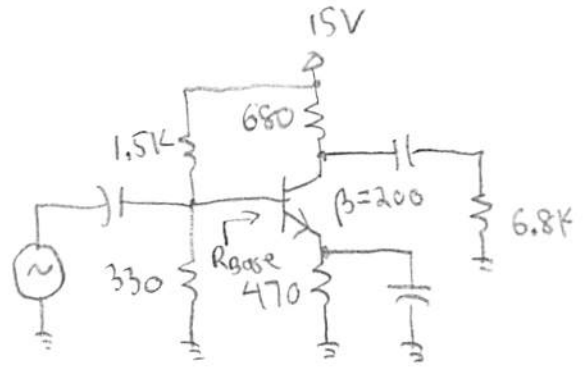

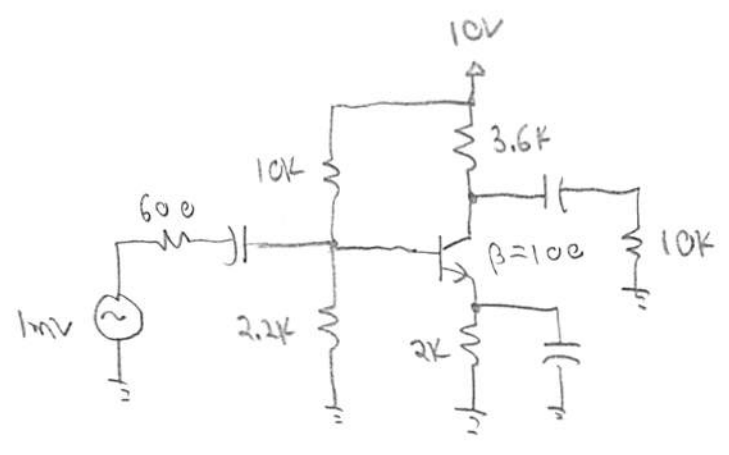8.27 (+10)

$$\frac{V_{OUT}}{V_S} = \frac{Z_{IN}}{Z_{IN} + R_S} \cdot \frac{V_{OUT}}{V_{IN}}$$

$(10k // 2.2k) // (\beta + 1)r_{e'}$ $-\alpha \frac{r_c}{r_{e'}}$



Need to find $r_{e'}$!

• Stiff divider? $10k // 2.2k = 1.8k$ vs. $\frac{101}{100} 2k = 2.02k$ ✓

$$\Rightarrow V_{BB} = 10 \frac{2.2k}{10k + 2.2k} = 1.8V$$

$$\Rightarrow I_{EQ} = \frac{1.8 - 0.7}{2k} = 0.55mA \Rightarrow r_{e'} = \frac{.026}{.55 \times 10^{-3}A} = \underline{\underline{47.3\Omega}}$$

$$\bullet r_c = R_C // R_L = 3.6k // 10k = 2.65k$$

$$\alpha = \frac{100}{101} = 0.99$$

$$\frac{V_{OUT}}{V_{IN}} = -0.99 \frac{2.65k}{.0473k} = \underline{\underline{-55.5}}$$

$$Z_{in} = (10k // 2.2k) // 101(.0473k) = \underline{\underline{1.31k}}$$

$$\Rightarrow \frac{V_{OUT}}{V_S} = \frac{1.31k}{1.31k + .6k} \cdot (-55.5) = -38.1$$

$$V_{OUT} = \left(\frac{V_{OUT}}{V_S} \right) \cdot V_S = (-38.1)(1mV) = \boxed{-38.1mV}$$


9.8

+10

Emitter follower!

$$\frac{V_{OUT}}{V_s} = \frac{Z_{IN}}{Z_{IN} + R_s} \cdot \frac{V_{OUT}}{V_{IN}}$$

$$\frac{r_e}{r_e + r_e'}$$

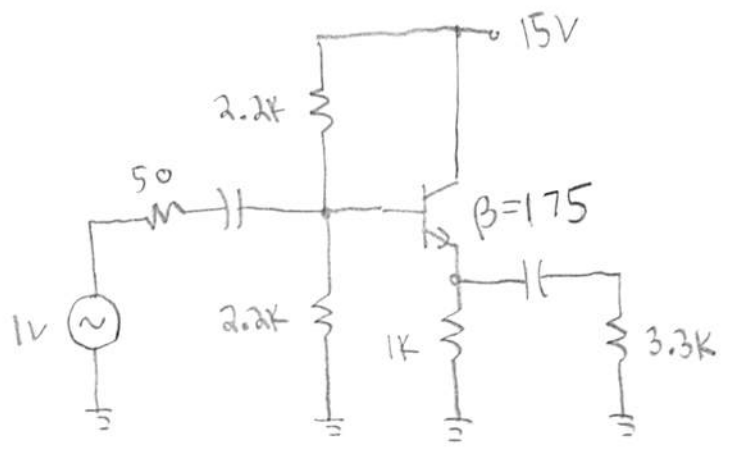

$$r_e = 1000 // 3300 = \underline{767.4}$$

$$\rightarrow V_{BB} = 15 \cdot \frac{2.2k}{4.4k} = 7.5V$$

$$r_e' \text{? stiff divider? } \left. \begin{array}{l} 2.2k // 2.2k = 1.1k \\ \frac{176}{100} \cdot 1k = 1.76k \end{array} \right\} \checkmark$$

$$I_{EQ} = \frac{7.5 - 0.7}{1k} = \underline{6.8mA}$$

$$r_e' = \frac{.026}{6.8 \times 10^{-3}} = \underline{3.82 \Omega}$$

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{767.4}{767.4 + 3.82} = \underline{0.995}$$

$$Z_{IN} = \underbrace{(2.2k // 2.2k)}_{1.1k} // \underbrace{\left[176(3.82 + 767.4) \right]}_{135.7k} = \underline{1.09k}$$


$$\Rightarrow \frac{V_{OUT}}{V_s} = \frac{1090}{1090 + 50} \cdot .995 = \boxed{0.95}$$

9.13 (+12)

$$\frac{V_{out}}{V_s} = \frac{Z_{in}}{Z_{in} + R_s} \times \frac{r_e}{r_e + r_e'}$$

$$r_e = 30 // 10 = \underline{7.5}$$

$r_e' ?$

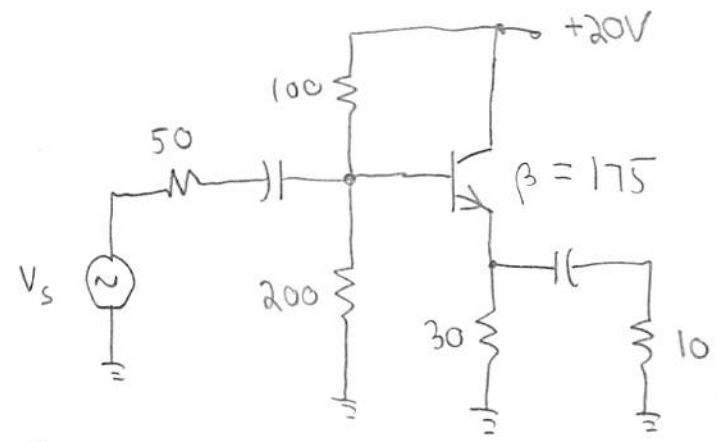

Stiff divider? $100 // 200 = 67$ } NOT stiff, but close enough $\rightarrow V_{BB} = 20 \frac{200}{300} = \underline{13.33}$
 $\frac{176}{100} 30 = 52.8$

$$I_{EQ} = \frac{13.33 - 0.7}{30} = 0.42A$$

$$Z_{in} = \underbrace{(100 // 200)}_{67} // \left[176 (.062 + 7.5) \right]_{1331}$$

$$= \underline{63.8 \Omega}$$

$$r_e' = \frac{.026V}{.42A} = \underline{.062 \Omega}$$


$$\Rightarrow \frac{V_{out}}{V_s} = \frac{63.8}{63.8 + 50} \times \frac{7.5}{7.5 + .062} = \boxed{0.556}$$

9.x For Darlington.

(+12) $R_{base} = (150 \times 150 + 1) (r_e' + r_e)$

? \uparrow \uparrow
 $10 // 8 = 4.44$

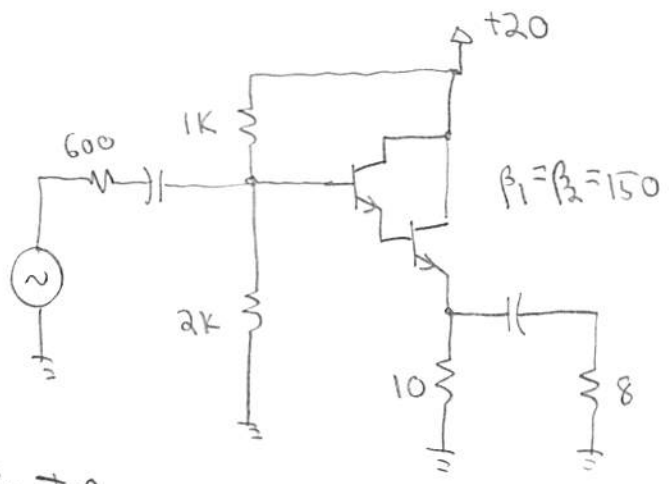Stiff divider? $1k // 2k = 667$ } ✓
 $\frac{(22501)}{100} 10 = 2250$



$$V_{BB} = 20 \frac{2k}{3k} = 13.33V$$

For Darlington,

$$I_{EQ} = \frac{13.33 - 1.4}{10} = 1.19A \Rightarrow r_e' = 2 \frac{.026}{1.19A} = \underline{.044 \Omega}$$

$$R_{base} = 22501 (.044 + 4.44) = \boxed{100.4k}$$

$$\frac{V_{OUT}}{V_s} = \frac{Z_{IN}}{Z_{IN} + R_s} \cdot \frac{r_e}{r_e + r_e'}$$

$$\frac{4.44}{4.44 + 0.044} = \underline{\underline{0.99}}$$

$$\uparrow$$

$$\underbrace{(1K // 2K)}_{.667K} // \underbrace{R_{base}}_{100.4K} = \underline{\underline{0.663K}}$$

$$= \frac{663}{663 + 600} \times .99 = \boxed{0.52}$$

9.24

78

$$V_{OUT} = V_Z - 0.7$$


$$= \boxed{6.8V}$$

$$I_2 = I_s - I_B$$

$$= \frac{15 - 7.5}{1K} - \frac{1}{151} \times \frac{6.8V}{.033K}$$

$$\frac{7.5mA}{1.36mA}$$

$$= \boxed{6.14mA}$$

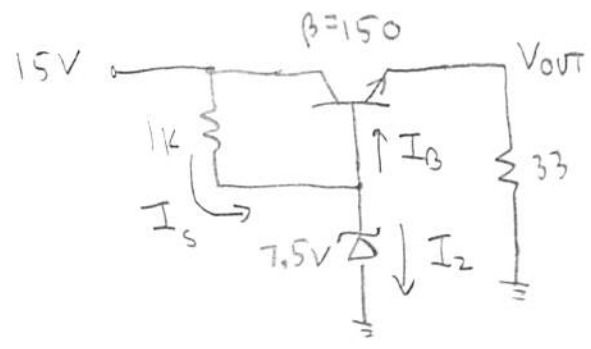

$$\alpha = \frac{150}{151} = .993$$

9.33

78

$$P = I_B V_{BE} + I_C V_{CE}$$


$$I_E = \frac{7.5 - 0.7}{33} = \underline{\underline{0.21A}}$$

$$V_{CE} = V_C - V_E = 15 - (7.5 - 0.7) = \underline{\underline{8.2V}}$$

$$I_B = \frac{.21A}{151} = \underline{\underline{.0014A}}$$

$$P = (.0014A)(0.7V) + (.21A)(8.2V)$$

$$= \boxed{1.723W}$$

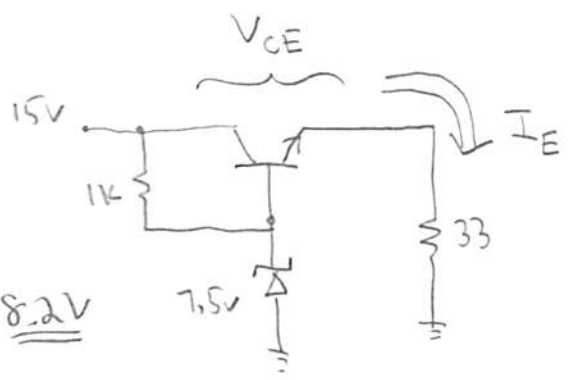

9.4 (+12)

→ start with A_2

• stiff divider?

$$3.3k \parallel 1.2k = 0.88k$$

$$\frac{201}{100} \cdot 47k = 0.94k$$

$$V_{BB} = 12 \frac{1.2k}{1.2k + 3.3k} = 3.2V$$

$$I_{EQ} = \frac{3.2 - 0.7}{47k} = 5.32mA$$

$$r_{e2}' = \frac{0.026V}{5.32mA} = 0.0049k$$

$$r_c = 1.2k \parallel 1k = 0.545k$$

$$A_2 = - \frac{200}{201} \frac{0.545k}{0.0049k} = -110.7$$

→ compute A_1

• stiff divider?

$$3.3k \parallel 5.6k = 2.08k$$


$$\frac{201}{100} \cdot 1.9k = 3.82k$$

$$V_{BB} = 12 \frac{5.6k}{5.6k + 3.3k} = 7.55V \rightarrow I_{EQ} = \frac{7.55 - 0.7}{1.9k} = 3.61mA$$

$$r_{e1}' = \frac{0.026V}{3.61mA} = 0.0072k$$

$$r_c = 1.2k \parallel 0.465k = 0.335k$$
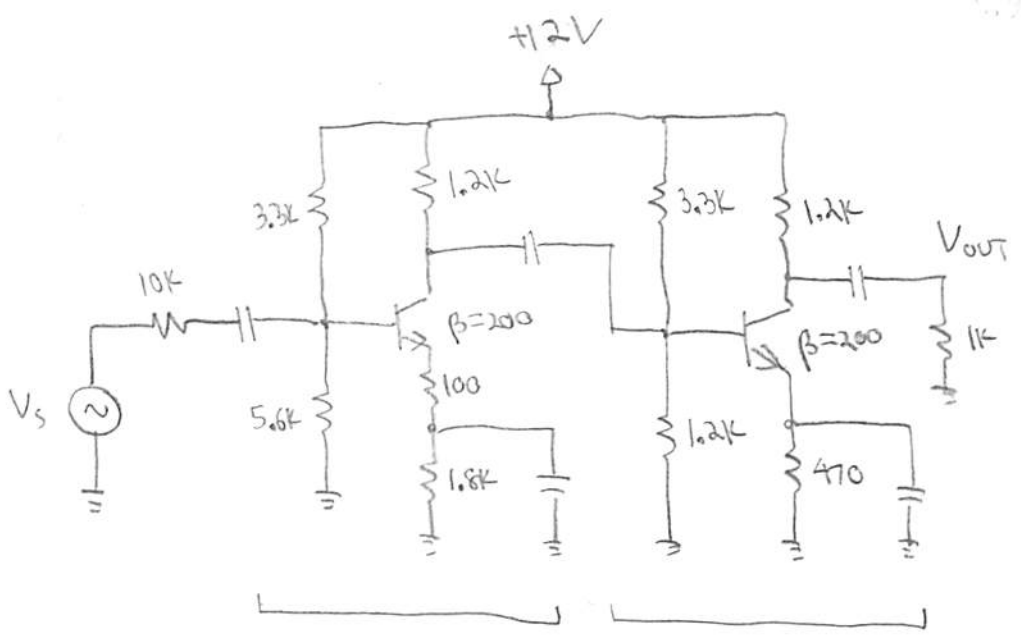
$$A_1 = - \frac{200}{201} \frac{0.335k}{0.0072k + 0.1k} = -3.1$$



$$A_1 = -\alpha \frac{R_c \parallel R_{in2}}{r_{e1}' + R_e}$$

$$A_2 = -\alpha \frac{R_c \parallel R_c}{r_{e2}'}$$

$$Z_{in2} = (3.3k \parallel 1.2k) \parallel (201)(0.0049k)$$

$$= 0.465k$$

$$Z_{in} = (3.3k \parallel 5.6k) \parallel 201(0.0072k + 0.1k)$$

$$= 1.89k$$


$$\Rightarrow \frac{V_{out}}{V_s} = \frac{Z_{in}}{Z_{in} + R_s} A_1 A_2 = \frac{1.89 \text{ k}}{1.89 + 10 \text{ k}} (-3.1)(-110.7) = \boxed{54.5}$$

9.2 (+12)

• stiff divider?

$$10 \text{ k} \parallel 2.2 \text{ k} = 1.8 \text{ k}$$
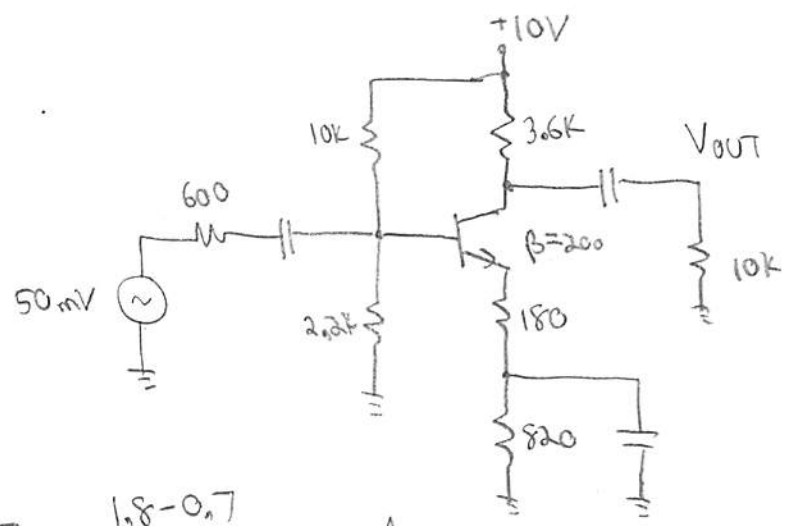
$$\frac{201}{100} \cdot 1 \text{ k} = 2.01 \text{ k}$$



$$V_{BB} = 10 \frac{2.2 \text{ k}}{2.2 \text{ k} + 10 \text{ k}} = 1.8 \text{ V} \Rightarrow I_{EQ} = \frac{1.8 - 0.7}{1 \text{ k}} = \underline{\underline{1.1 \text{ mA}}}$$

$$r_e = \frac{0.026 \text{ V}}{1.1 \text{ mA}} = \underline{\underline{0.0236 \text{ k}}}$$

$$\alpha = \frac{200}{201} = 0.995$$

$$r_c = 3.6 \text{ k} \parallel 10 \text{ k} = 2.65 \text{ k}$$

$$A = -\alpha \frac{r_c}{r_e + R_e} = -0.995 \frac{2.65 \text{ k}}{(0.0236 \text{ k} + 0.18 \text{ k})} = \underline{\underline{-12.95}}$$

$$Z_{in} = (10 \text{ k} \parallel 2.2 \text{ k}) \parallel \underbrace{201(0.0236 \text{ k} + 0.18 \text{ k})}_{40.9 \text{ k}} = \underline{\underline{1.73 \text{ k}}}$$

$$\Rightarrow V_{out} = 50 \text{ mV} \frac{1.73 \text{ k}}{1.73 \text{ k} + 0.6 \text{ k}} \times (-12.95) = \boxed{-481 \text{ mV}}$$