

8.W (16)

ECE 248 Assignment 5 solution

1

STEP 1 Q-Point

Stiff divider: $10K // 2.2K = 1.8K$

$\frac{201}{100} \cdot 1K = 2.01K$

$V_{BB} = 10 \frac{2.2K}{2.2K + 10K} = 1.8V$

$I_{EQ} = \frac{1.8 - 0.7}{1K} = 1.1mA$

$V_C = 10 - 0.995 (1.1mA) (3.6K) = 6.06V$

$I_{CQ} = \frac{10 - 6.06}{2.6} = 1.094mA$

$V_{CEQ} = 6.06 - 1.1V = 4.96V$

STEP 2 AC analysis

$r_c = 3.6K // 10K = 2.65K$

$v_{out} = -i_c r_c = -\alpha i_e r_c$

$i_e = -\frac{v_{out}}{\alpha r_c}$

$v_{ce} = v_c - v_e = v_{out} - i_e R_e = v_{out} - \left(\frac{-v_{out}}{\alpha r_c} \right) R_e = v_{out} \left(1 + \frac{R_e}{\alpha r_c} \right)$



STEP 3 Cut-off vs. Saturation

cut-off: $i_e = -I_{EQ} \Rightarrow \frac{-v_{out}}{\alpha r_c} = -I_{EQ} \Rightarrow v_{out} = \alpha I_{EQ} r_c = 0.995 (1.1mA) (2.65K) = 2.9V$

saturation: $v_{ce} = -V_{CEQ} \Rightarrow v_{out} \left(1 + \frac{R_e}{\alpha r_c} \right) = -V_{CEQ}$


$v_{out} = \frac{-4.96V}{1 + \frac{1.8K}{0.995 \cdot 2.65K}} = -4.64V$

MP = 2.9V
Due to cut-off on (+) side

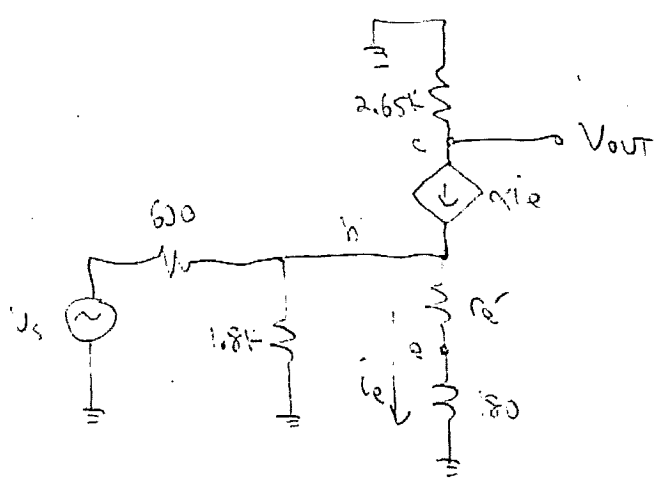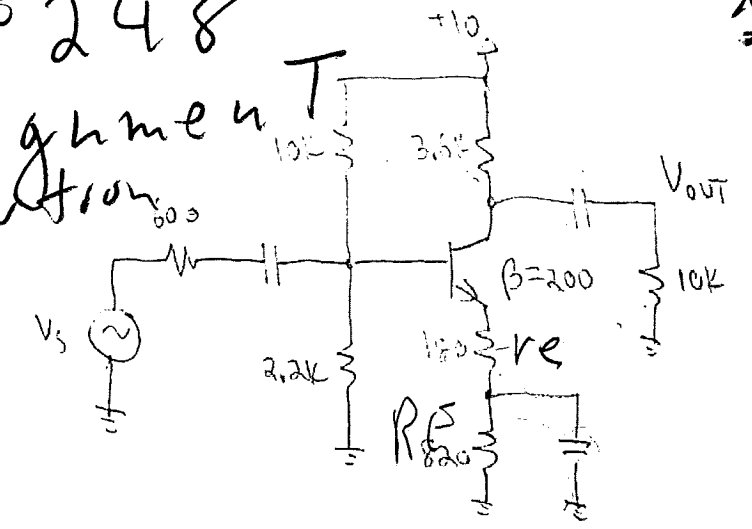

Load lines for Problem 8W

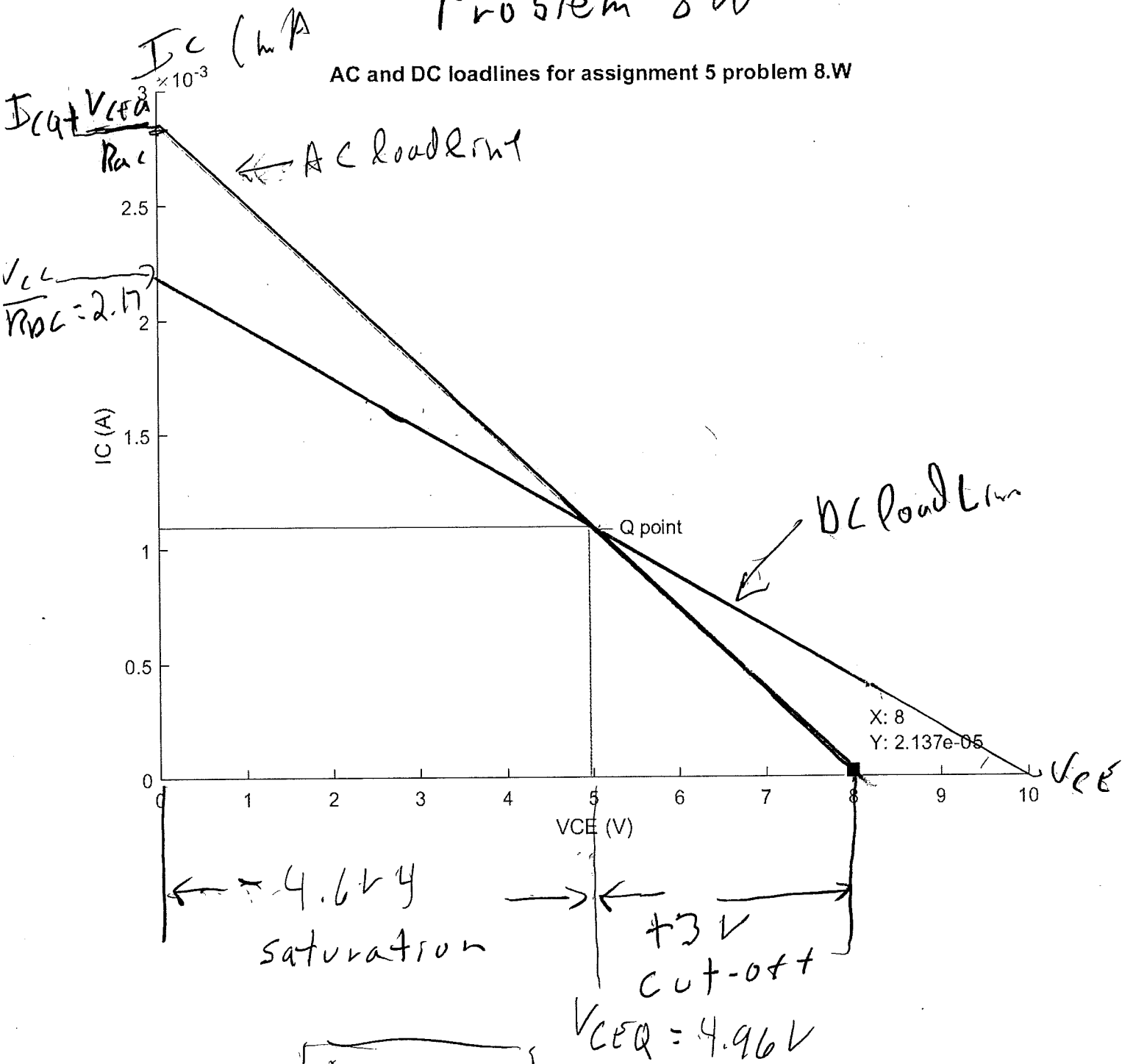AC and DC loadlines for assignment 5 problem 8.W




$V_P = 3V$

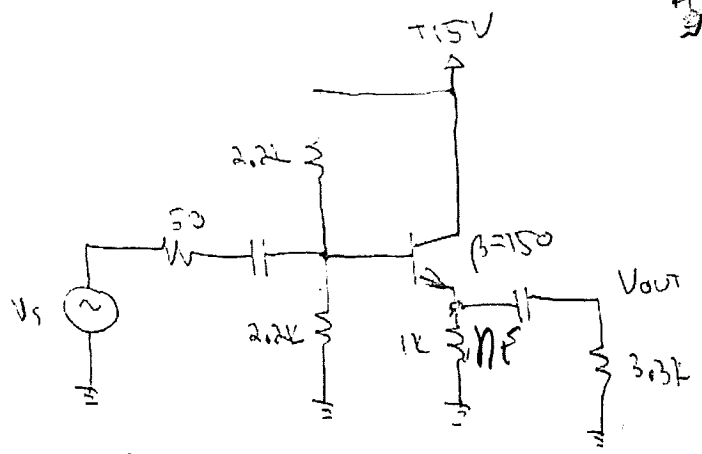9.X +16

STEP 1 Q-Point

• stiff divider? $2.2k // 2.2k = 1.1k$
 $\frac{15}{100} \times 1k = 1.51k$



• $V_{BB} = 15 \times \frac{2.2k}{2.2k + 2.2k} = 7.5V \rightarrow I_{EQ} = \frac{7.5 - 0.7}{1k} = 6.8mA$



• $V_{CEQ} = V_C - V_E = 15 - 6.8V = 8.2V$

STEP 2 AC analysis

$r_e = 1k // 3.3k = 0.77k$

• $V_{out} = i_e r_e \rightarrow i_e = \frac{V_{out}}{r_e}$

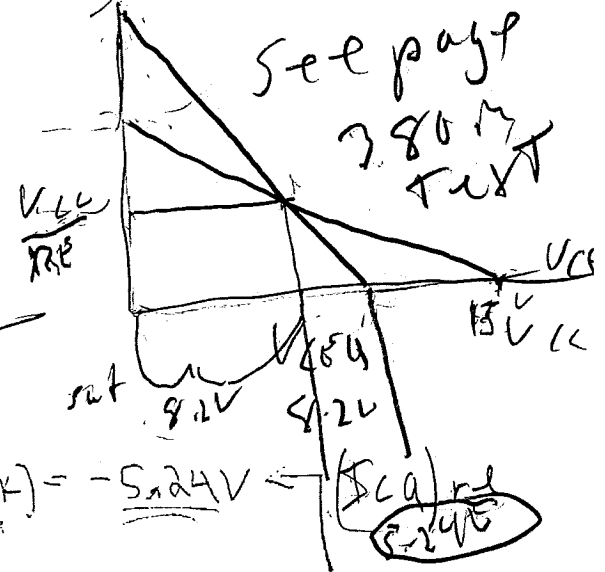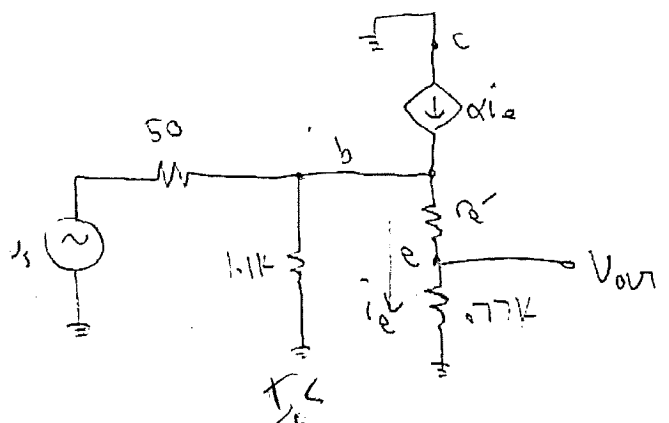• $V_{ce} = V_C - V_e = 0 - V_{out} = -V_{out}$



STEP 3 cut-off vs. saturation

cut-off: $i_e = -I_{EQ} \Rightarrow \frac{V_{out}}{r_e} = -I_{EQ}$

Max $V_{out} = -(6.8mA)(0.77k) = -5.24V$

saturation: $V_{ce} = -V_{CEQ} \Rightarrow -V_{out} = -V_{CEQ}$

Max $V_{out} = 8.2V$

MP = 5.24V

Due to cut-off on (-) side

9.4

(10)

$$r_e' = \frac{.026}{6.8 \text{ mA}} = .0038 \text{ K}$$



$$V_{\text{LOAD}} = V_G \frac{Z_W}{Z_W + Z_S} A$$

$$\frac{r_e}{r_e + r_e'} = \frac{.77 \text{ K}}{.77 \text{ K} + .0038 \text{ K}} = 0.995$$

$$Z_W = 2.2 \text{ K} // 2.2 \text{ K} // (151)(.0038 \text{ K} + .77 \text{ K}) = \underline{\underline{1.09 \text{ K}}}$$

$$V_{\text{LOAD}} = (7 V_p) \frac{1.09 \text{ K}}{1.09 \text{ K} + .050 \text{ K}} \times .995 = \underline{\underline{6.66 V_p}}$$
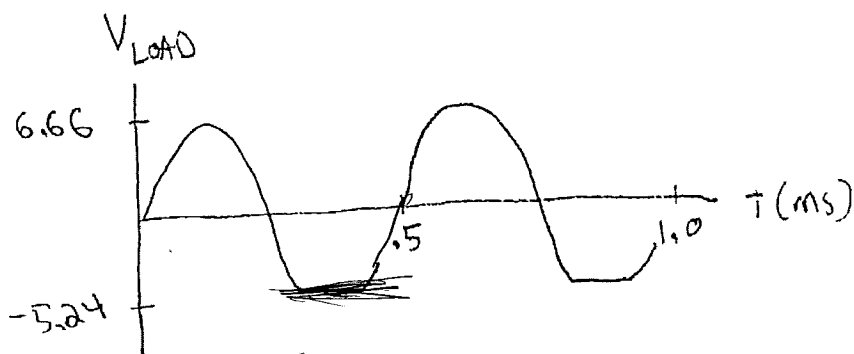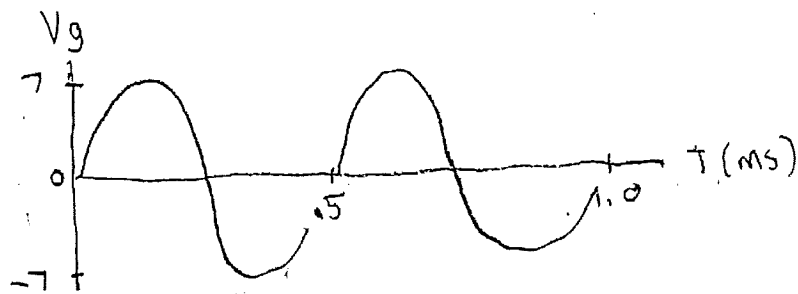
$$2 \text{ KHz} \Rightarrow T_{\text{cycle}} = .5 \text{ ms}$$



10.3 +16

5

STEP 1 Q-Point

• stiff divider: $2k // 47k = 0.38k$
 $\frac{201}{100} \cdot 22k = 0.44k$

• $V_{BB} = 15 \frac{0.47k}{0.47k + 2k} = 2.85V$


$\rightarrow I_{EQ} = \frac{2.85 - 0.7}{220} = 0.0098A$

$\alpha = \frac{200}{201} = 0.995$

• $V_c = 15 - 0.995 (0.0098A) (680\Omega) = 8.37V$

$V_E = 2.15V$

$V_{CEQ} = 8.37 - 2.15 = 6.22V$

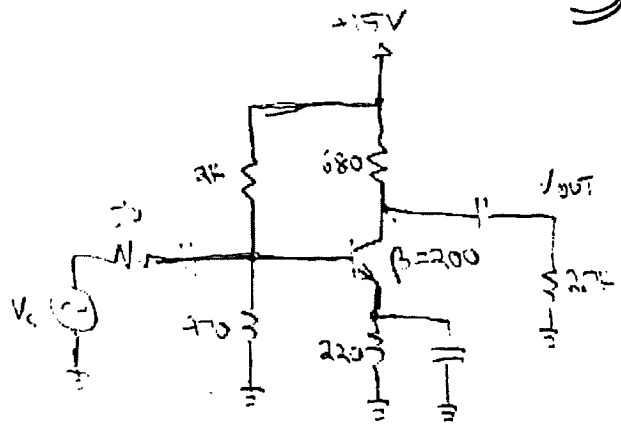


STEP 2 AC analysis

$r_c = 680 // 2700 = 543\Omega$

• $V_{OUT} = -i_c r_c = -\alpha i_e r_c$

$i_e = -\frac{V_{OUT}}{\alpha r_c}$

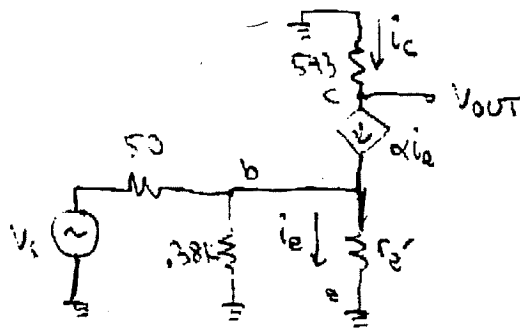• $V_{ce} = V_c - V_e = V_{OUT} - 0 = V_{OUT}$



STEP 3 Cut-off vs Saturation

Cut-off: $i_e = -I_{EQ} \rightarrow -\frac{V_{OUT}}{\alpha r_c} = -I_{EQ} \rightarrow \text{Max } V_{OUT} = \alpha I_{EQ} r_c$
 $= 0.995 (0.0098A) (543\Omega)$
 $= 5.3V \leftarrow MP$

Saturation: $V_{ce} = -V_{CEQ} \rightarrow V_{OUT} = -V_{CEQ} \rightarrow \text{Max } V_{OUT} = -6.22V$
MPP = 10.6V_{pp} cut-off on (+) side

10.2

+10

$$V_{out} = V_g \frac{Z_{in}}{Z_{in} + Z_s} A \quad \leftarrow \quad A = -\alpha \frac{R_c / R_e}{r_e'}$$

$$\alpha = \frac{200}{201} = .995$$

$$680 // 2700 = 543.2 \Omega$$


$$\rightarrow A = -.995 \frac{543.2}{2.65} = \underline{\underline{-204}}$$

$$r_e' = \frac{.026V}{.0098A} = 2.65 \Omega$$


$$Z_{in} = 2000 // 470 // (201)(2.65) = \underline{\underline{222 \Omega}}$$

$$\text{So, } V_{out} = (.005V_p) \frac{222}{222 + 50} (-204) = \underline{\underline{-0.83V_p}} \quad \leftarrow$$

less than MPV

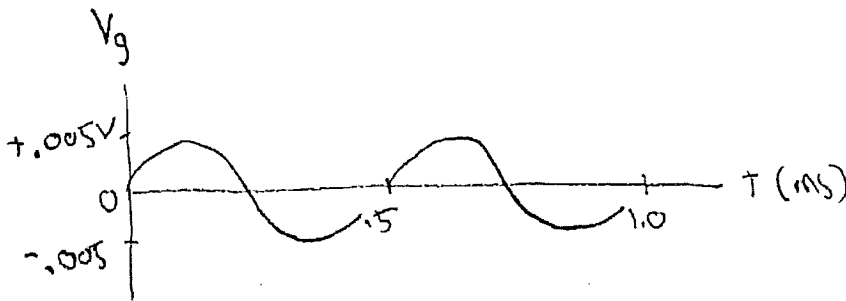


2kHz \rightarrow .5ms per cycle

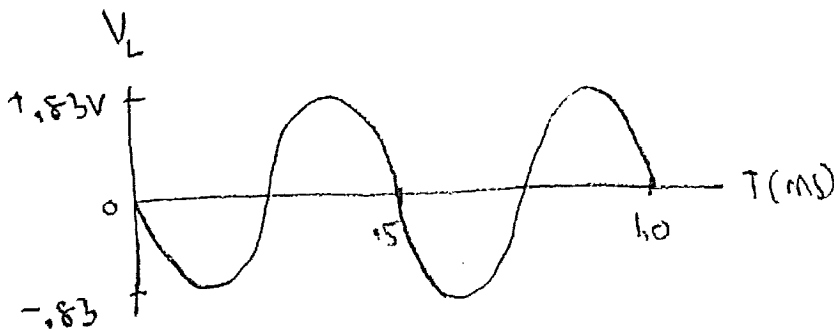

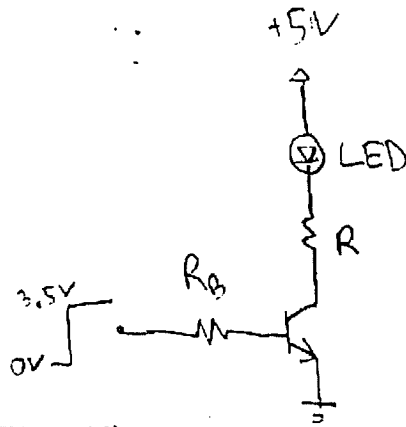6.x (+8)

- Load properties: LED has $V_F = 3.5V$ @ $25mA$



- Saturated BJT: $5 - V_{LED} - I_{LED} R - V_{CE,sat} = 0$
 \uparrow \uparrow \uparrow
 $3.5V$ $.025A$ $0V$

$$\Rightarrow R = \frac{5 - 3.5V}{.025A} = 60\Omega$$

For $I_{LED} < 25mA$, choose

$$R = 62\Omega$$

[62Ω is probably safer, but 60Ω is OK]

- Base current: $I_B \sim \frac{I_C}{10}$ (Hard saturation)

$$I_{LED} = \frac{5 - 3.5V}{62\Omega} = \underline{\underline{24.2mA}}$$

$$\frac{3.5 - 0.7}{R_B} \sim 2.42mA$$

$$\Rightarrow R_B = \frac{3.5 - 0.7V}{.00242A} = 1157\Omega$$

$$\text{Choose } R_B = 1.2K$$

(1.1K also OK)

6.y (+8)


- Load: $V_L = 6V$ @ $120mA$

- Saturated BJT:

$$9 - V_{Load} - I_{Load} R - V_{CE,sat} = 0$$

$$\uparrow \quad \uparrow \quad \uparrow$$

$$6V \quad .12A \quad 0V$$

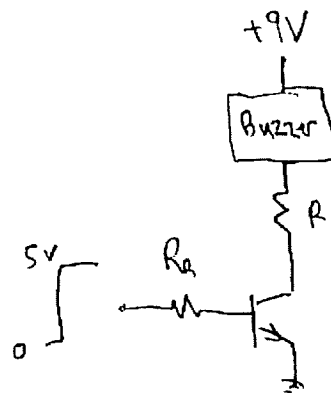

$$R = \frac{9-6}{0.12A} = 25\Omega \Rightarrow \text{Choose } R = 27\Omega$$

$$I = \frac{9-6}{27\Omega} = 0.11A$$

Base current: $I_B \sim \frac{I_C}{10}$ (Hard saturation)

$$\frac{5-0.7}{R_B} \sim 0.11A \Rightarrow R_B = 39\Omega \quad \text{Choose } R_B = 390\Omega$$

12.11 According to Table 12-1, BS107 has


+8 $V_{GS,ON} = 2.6V, R_{DS,ON} = 28\Omega, I_{D,ON} = 20mA$

$V_{GS} = 3-0=3V > V_{GS,ON} \Rightarrow$ MOSFET is ON.

$$I_D = \frac{15-0V}{1800 + 28\Omega} = 0.0082A = 8.2mA < 20mA$$


$$\Rightarrow V_D = I_D R_{DS,ON} = (0.0082A)(28\Omega) = 0.23V$$

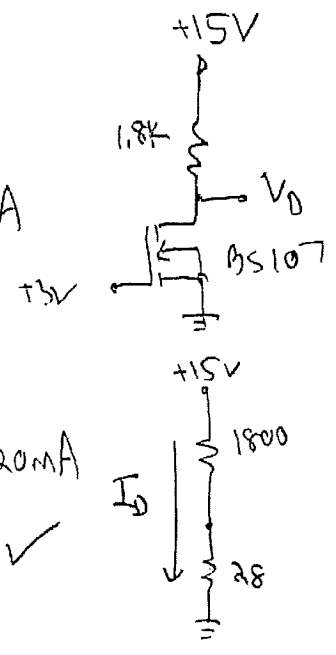OR $= 15 - I_D(1800) = 0.24V$
 Discrepancy due to rounding error



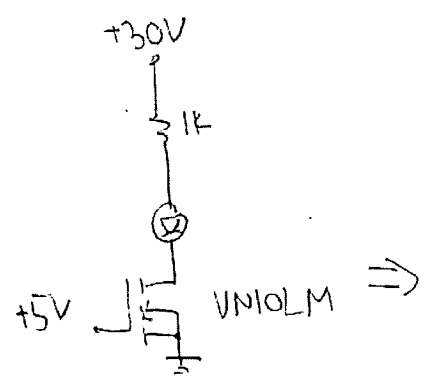12.14 MOSFET is ON since +5V = $V_{GS,ON}$

+8 $V_{GS,ON} = 5V$
 $R_{DS,ON} = 7.5\Omega$
 $I_{D,ON} = 200mA$




$$I_D = \frac{30-2V}{1000 + 7.5} = 0.0278A = 27.8mA < 200mA \quad \text{Ohmic}$$

12.15 When MOSFET is ON,

+8
$$I_D = \frac{20 - 0V}{1000 + 28\Omega}$$

=
$$\boxed{19.5mA} < 20mA$$

ohmic ✓

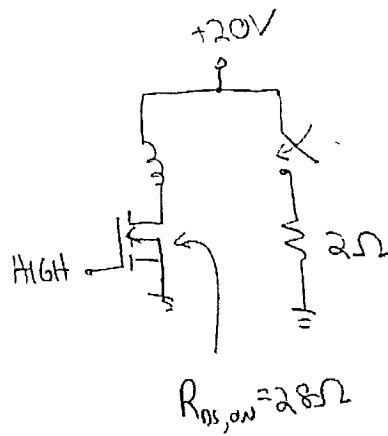


Load current =
$$\frac{20V}{2\Omega} = \boxed{10A} \leftarrow \text{HUGE!}$$

12.27

+8 DARK \rightarrow photodiode is OFF
 \Rightarrow AETs like open circuit

$$V_{Gate} = 15 \frac{2M}{2M + 1M} = \underline{10V} = V_{GS,ON}$$

\Rightarrow MOSFET is ON

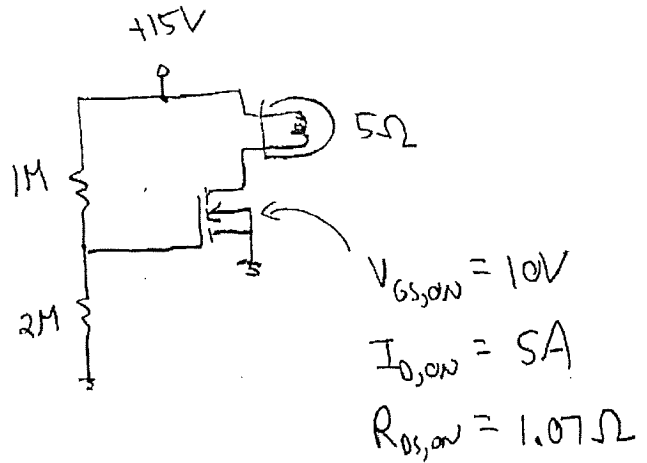


$$I_D = \frac{15 - 0V}{5 + 1.07} = 2.47A < 5A \quad \text{ohmic } \checkmark$$

Lamp power =
$$I_D^2 R = (2.47A)^2 (5\Omega) = \boxed{30.5W}$$

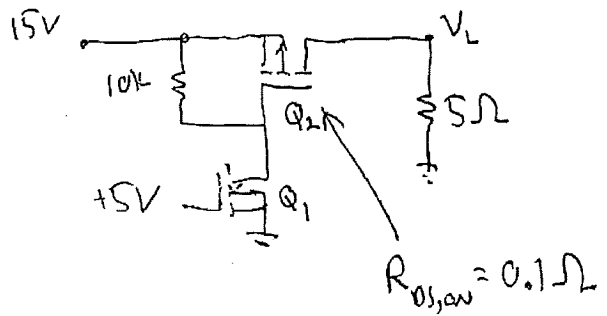12.34


+8 When Q_1 ON, Q_2 's $V_G \approx 0V$
 $V_{GS} \approx -15V$
 $\Rightarrow Q_2$ is OFF



12-24 continued

$$I_0 = \frac{15V}{.1 + 5\Omega} = 2.94A < 5A$$

ohmic ✓

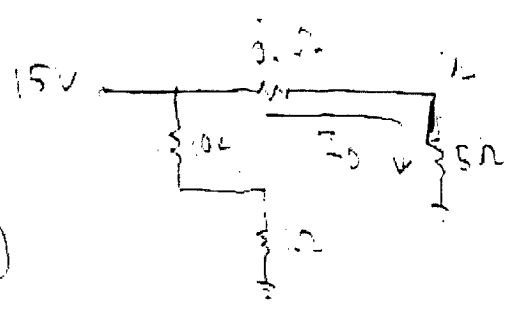

$$P_2 = I_0^2 R_{os,sw} = (2.94A)^2 (0.1\Omega)$$


$$= \boxed{0.864W}$$

$$P_L = I_0^2 R_L = (2.94A)^2 (5\Omega) = \boxed{43.2W}$$

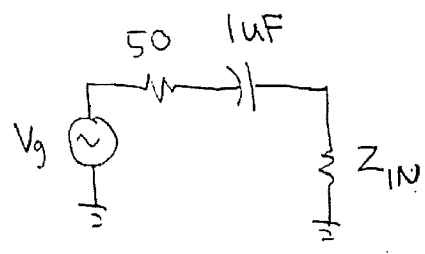14.33

+6

$$f_1 = \frac{1}{2\pi(50 + R_w)(1 \times 10^{-6} \text{F})}$$



$$Z_w = (10\text{K} // 2.2\text{K}) // 201 r_e'$$

• Stiff divider? $10\text{K} // 2.2\text{K} = 1.8\text{K}$
 $\frac{201}{100} 1\text{K} = 2.01\text{K}$

$$I_{EQ} = \frac{10 \frac{2.2\text{K}}{12.2\text{K}} - 0.7}{1\text{K}} = 1.1\text{mA} \Rightarrow r_e' = \frac{0.026\text{V}}{0.0011\text{A}} = \underline{23.6\Omega}$$


$$\Rightarrow Z_w = 10000 // 2200 // 201(23.6) = \underline{1307\Omega}$$

$$\Rightarrow f_1 = \frac{1}{2\pi(50 + 1307)(10^{-6})} = \boxed{117.3\text{Hz}}$$

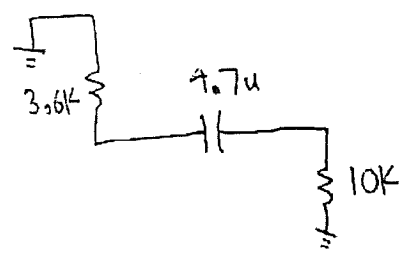14.34

+3


$$f_1 = \frac{1}{2\pi(3600 + 10000)(4.7 \times 10^{-6})} = \boxed{2.49\text{Hz}}$$



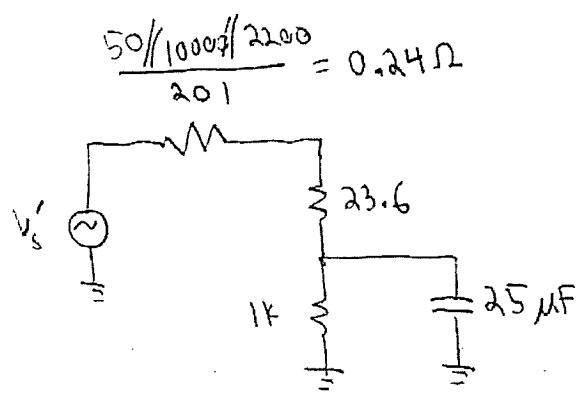14.35

+3

$$f_1 = \frac{1}{2\pi \left[1000 // (23.6 + 0.24) \right] (25 \times 10^{-6})} = \boxed{273.4\text{Hz}}$$



$$\frac{50 // 1000 // 2200}{201} = 0.24\Omega$$