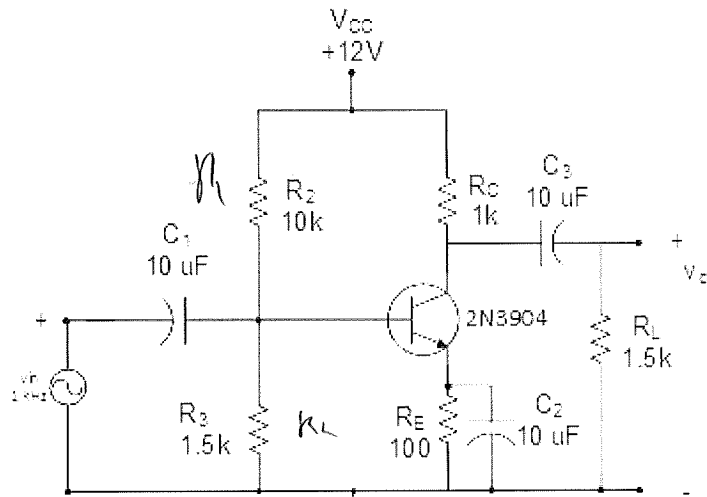


1

Union College
ECE248
Lab 07 Solution

See page
370 in the
text book



Case 1 MSS

Find the value of R_3 for MSS

a) find I_{CQ} and V_{CEQ}

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} \quad R_{ac} = R_c \parallel R_L$$

$$R_{ac} = 1k \parallel 1.5k = 600 \Omega$$

$$R_{dc} = R_c + R_E = 1k + 100 \Omega = 1.1k \Omega$$

$$I_{CQ} = \frac{12}{1.1k + .6k} = 7.06 \text{ mA}$$


$$V_{CEQ} = V_{CC} - I_{CQ}(R_c + R_E) = 12 - (7.06(1 + .1)) = 4.3V$$

2

b) Find value for R_3

"Thevenin" voltage divider

Find V_{BB}

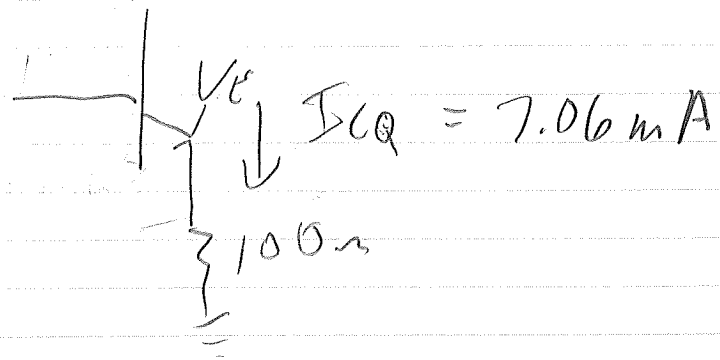

$$V_E = (7.06\ \text{mA})(100\ \Omega) = .706\ \text{V}$$

$$V_{BB} = V_E + 0.7 = 1.406$$


Find R_3 to give 1.406 V

$$1.406 = \frac{12R_3}{R_3 + 10k}$$

$$R_3 = 1.335\ \text{k}\Omega$$

nearest 5% value = $1.5\ \text{k}\Omega$

Draw load line

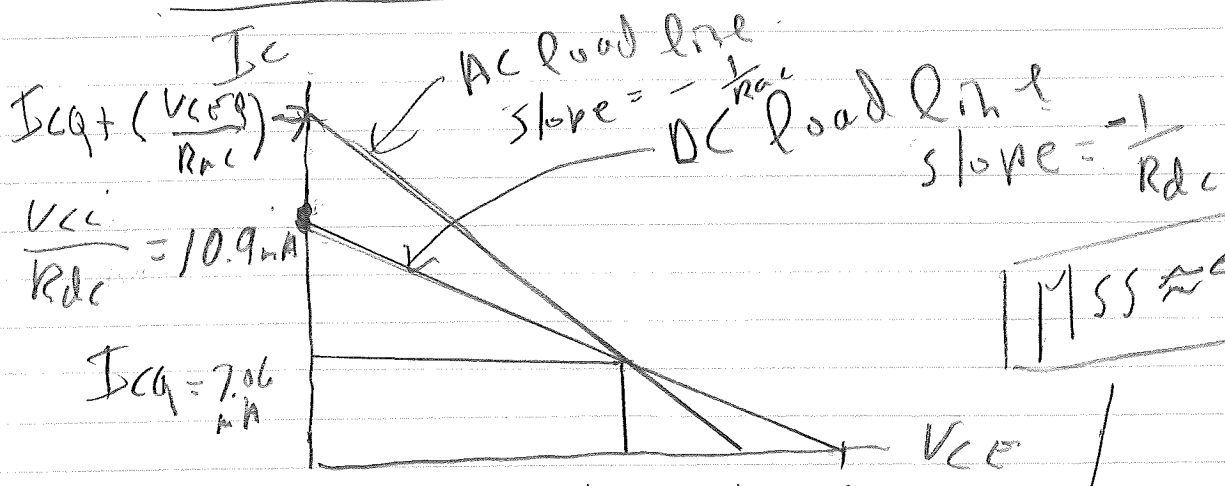


$$V_{CEQ} \approx 8.4\ \text{V}_{\text{pu-pb}}$$

$$V_{CEQ} = 4.3\ \text{V}$$

$$I_{CQ}(R_{ac}) = 4.2\ \text{V}$$

3

Simulate in Multisim

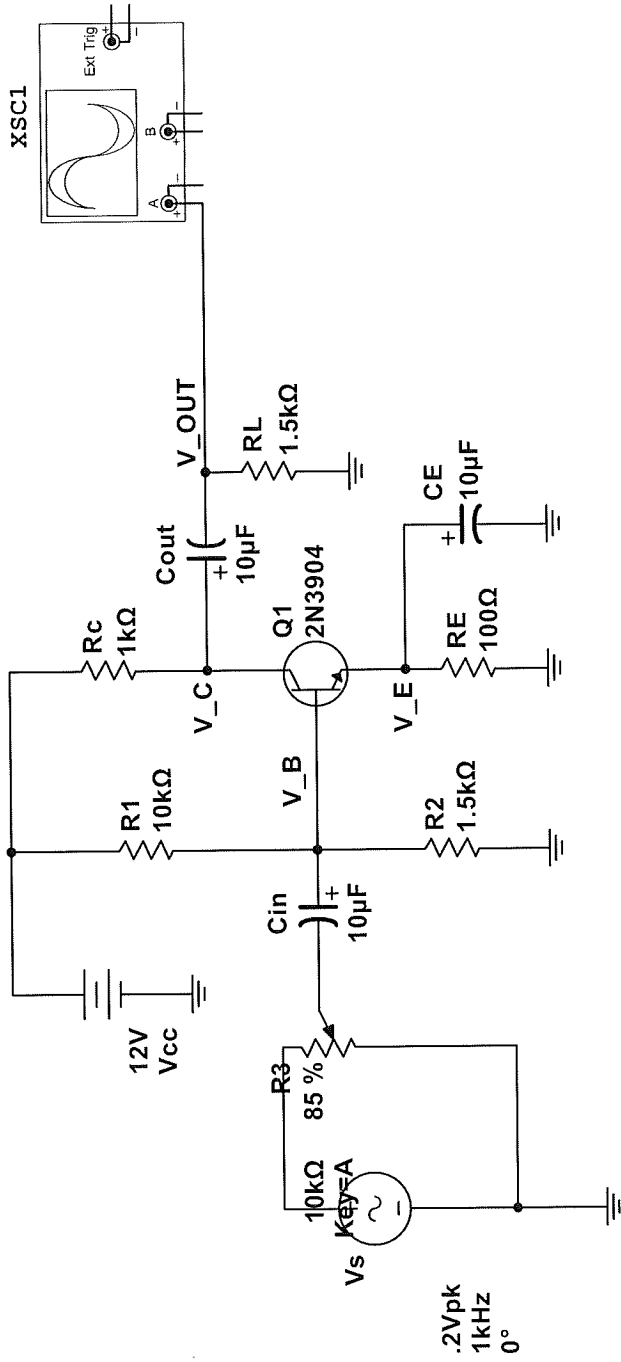

0 1 2 3 4 5 6 7 8

A B C D E F G

0 1 2 3 4 5 6 7 8

5


simulate in Multisim

DC Operating Point Analysis

	Variable	Operating point value
1	V(v_b)	1.50363
2	V(v_c)	4.21784
3	V(v_c)-V(v_e)	3.43491
4	V(v_e)	782.93716 m
5	I(Q1[IB])	47.21579 u
6	I(Q1[IC])	7.78216 m
7	I(Q1[IE])	-7.82937 m

← designed for $V_{CEQ} = 4.2V$

← designed for $I_{CQ} = 7.06mA$

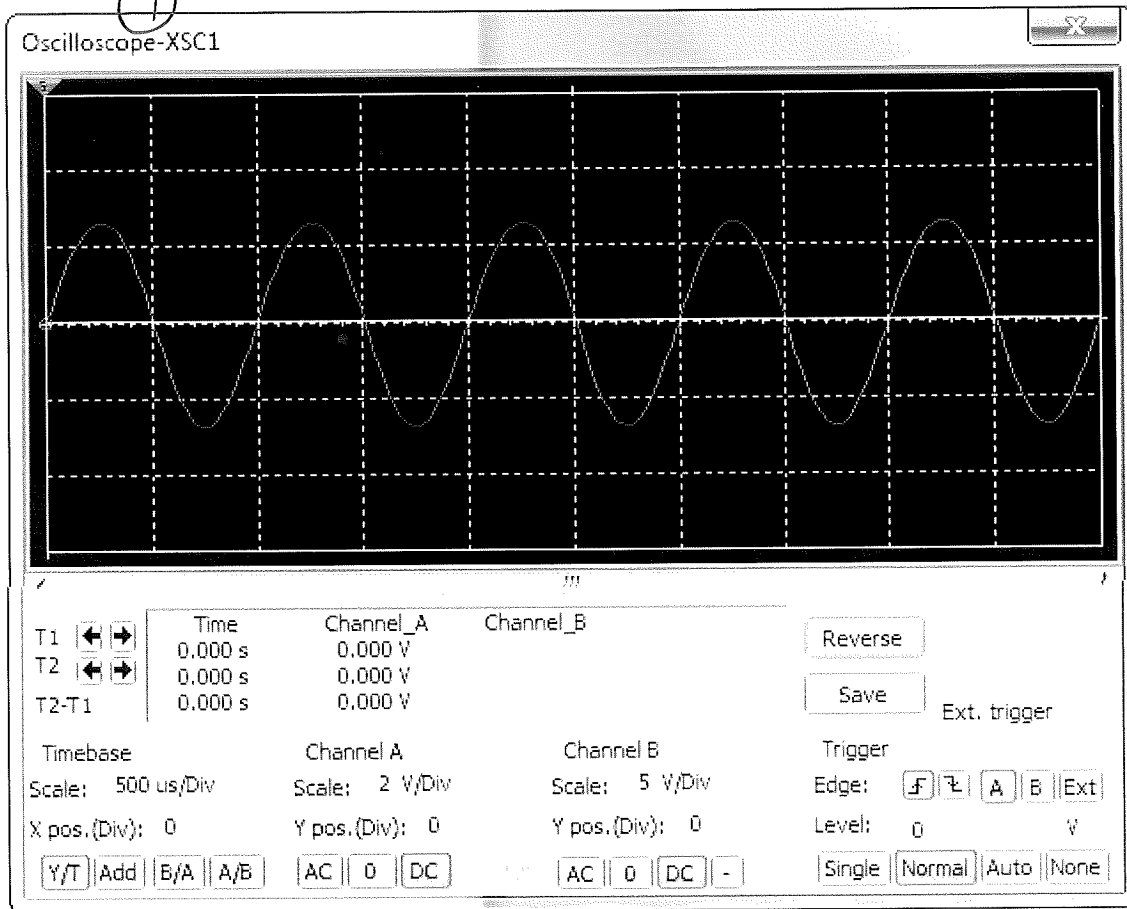

Simulate in Multisim


LoadLinesR3_1.5k

Printing Time: Friday, May 25, 2018, 10:15:41 AM

Simulate in Multisim

6

Transient

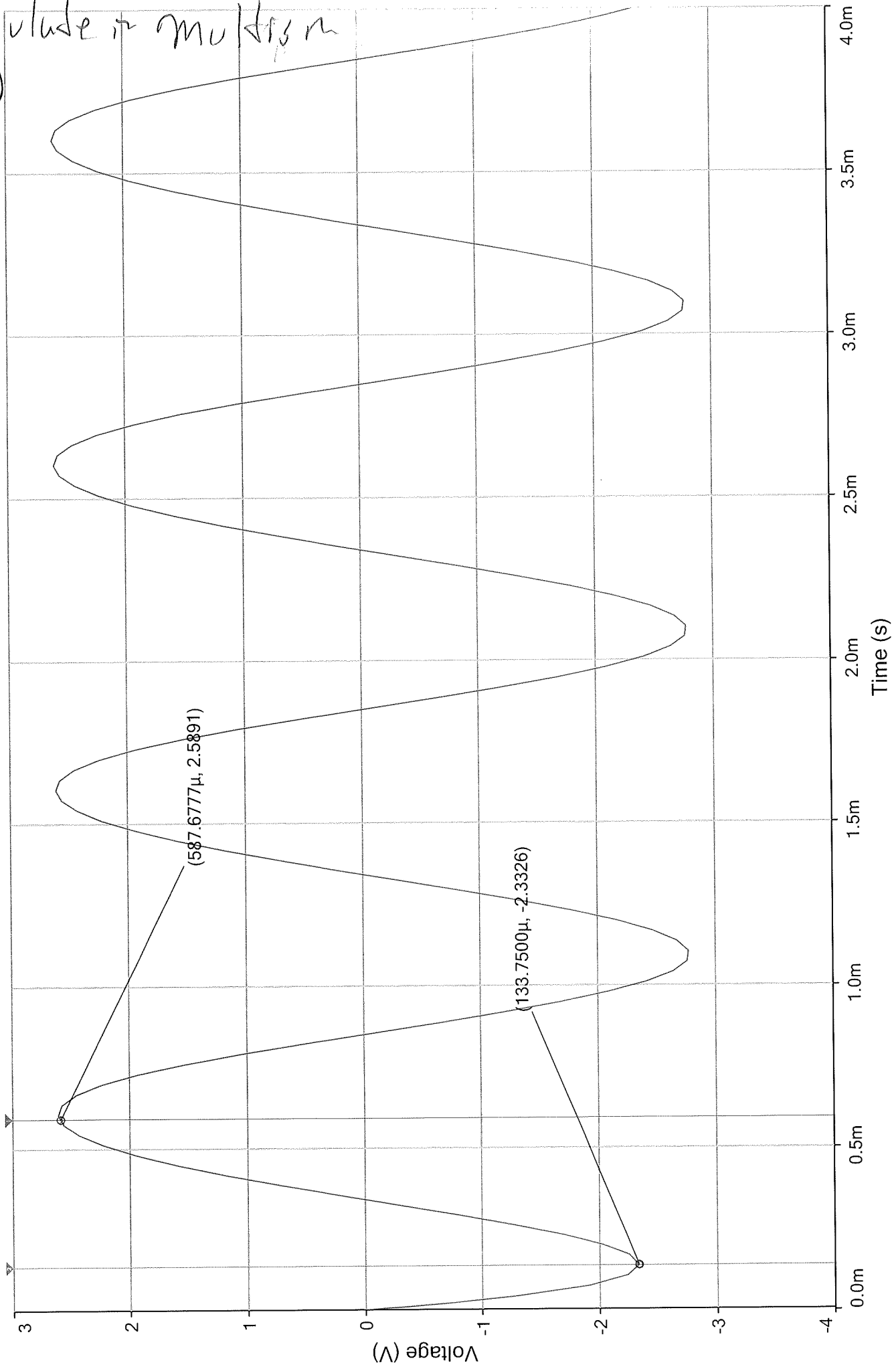

V(v_out)

V(v_out):	x1	y1	x2	y2	dx	dy	dv/dx	1/dx
	587.6777 μ	2.5891	133.7500 μ	-2.3326	-453.9277 μ	-4.9217	10.8424k	-2.2030k

```
% Generate the DC and AC load lines for R3 = 1.5k
% this will give the MSS
```

```
clear
clf
```

```
k = 10^3;
VCC = 12;
RC = 1*k;
RE = 100;
RL = 1.5*k;
RDC = RC + RE
Rac = (RC*RL)/(RC + RL)
```

```
% calculate ICQ for MSS
```

```
ICQ = VCC/(Rac + RDC)
VCEQ = VCC - (ICQ*(RC + RE))
```

```
Vpk = ICQ * Rac
```

```
x = 0:.1: VCC;
ydc = (-1/RDC)*x + (VCC/RDC);
```

```
yac = (-1/Rac)*x + (ICQ + (VCEQ/Rac));
```

```
for i = 1: length(yac)
    if yac(i) <= 0
        yac(i) = 0;
    end
end
```

```
hold
```

```
plot(x,ydc, x, yac)
```

```
plot([0, VCEQ], [ICQ, ICQ] , 'r')
```


```
plot([VCEQ, VCEQ] , [ICQ,0], 'r')
```

```
Qpt = ' \leftarrow Q point';
text(VCEQ, ICQ, Qpt)
grid
xlabel('VCE (V)')
ylabel('IC (A)')
title(' AC and DC loadlines with R3 = 1.5k')
hold off
```

Use Matlab to
Plot Theoretical
Load Lines

8

Matlab

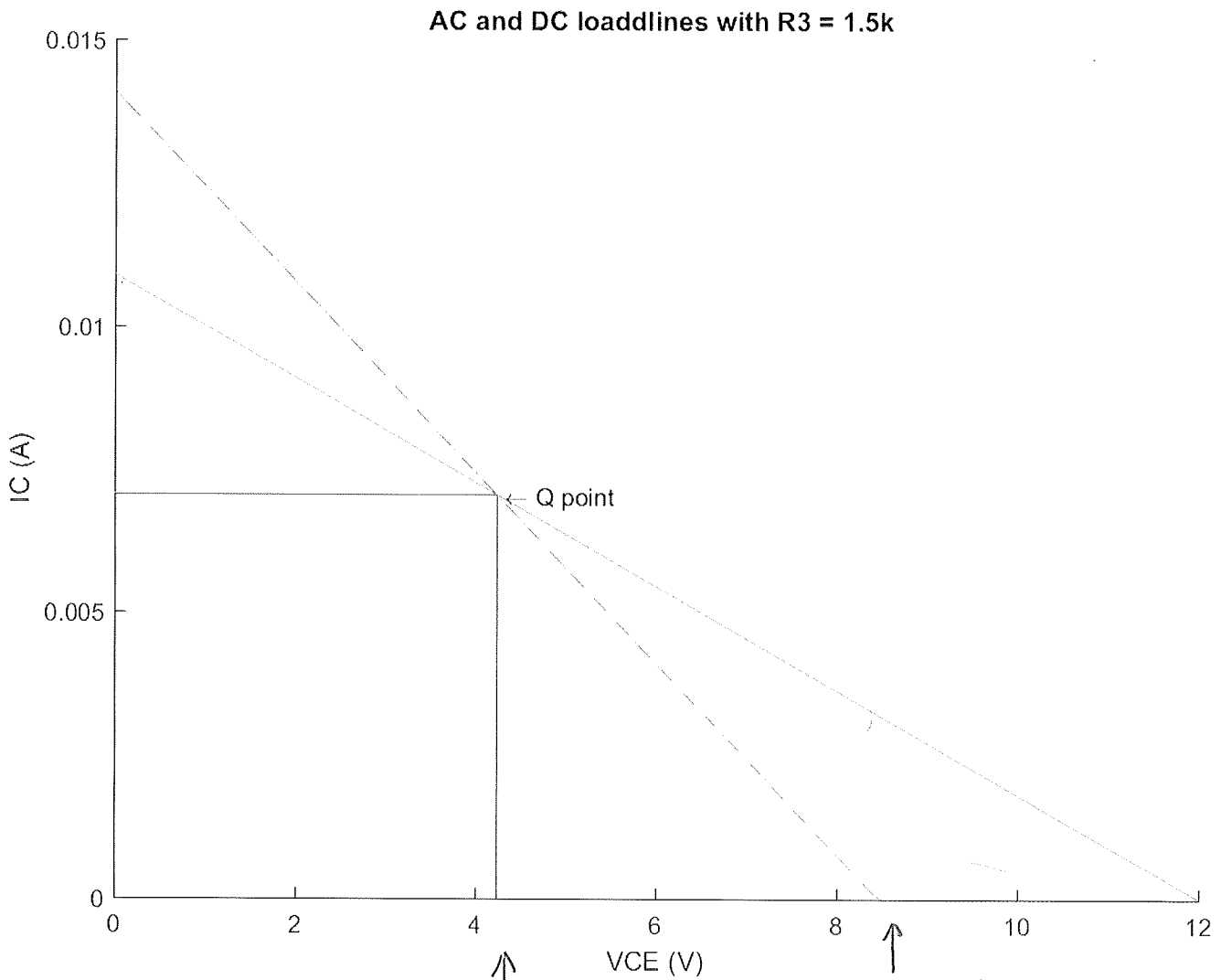

↑
4.225V

↑
8.4V

↑ ← 4.165V → ↑

absolutely max $V_{CE} = 8.22$ p-p

AC and DC loadlines for $R_3 = 2k$

Using calculated $I_{CQ} = 10.2 \text{ mA}$

