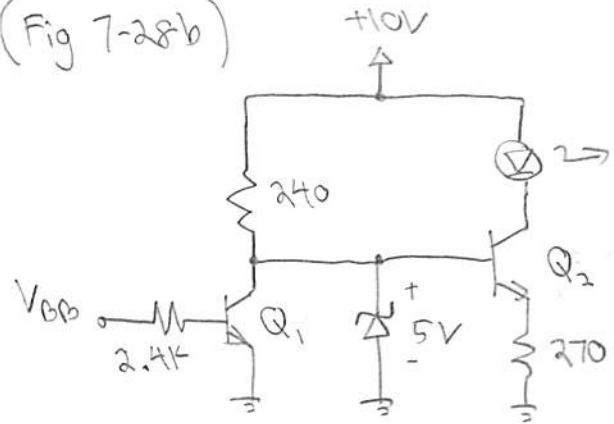


7.48 (+8)

(Fig 7-28b)



• If $V_{BB} = 0$, then Q_1 is OFF

$\rightarrow I_{c1} = 0$

\Rightarrow Zener is ON

$(I_z \approx \frac{10-5}{240} = 20.8 \text{ mA})$

$\Rightarrow I_{E2} = \frac{5-0.7}{270\Omega} = \underline{15.9 \text{ mA}}$

$\Rightarrow I_{LED} = \frac{100}{101} \times 15.9 \text{ mA} = \boxed{15.7 \text{ mA}}$

• If $V_{BB} = 10\text{V}$, then Q_1 is ON

$\rightarrow I_{B1} = \frac{10-0.7}{2.4\text{k}} = \underline{3.875 \text{ mA}}$

\Rightarrow What is I_{c1} ? let $I_{c1} = \beta I_{B1} = 100 \times 3.875 \text{ mA} = 387.5 \text{ mA}$

This not possible, because $V_{CE1} = 10 - (387.5)(240) - 0 = \underline{-83\text{V}}$!


So, Q_1 is saturated $\rightarrow V_{c1} = 0\text{V} \rightarrow V_{B2} = 0\text{V} \Rightarrow Q_2$ is OFF and therefore $I_{LED} = 0$

Zener is OFF

7.x (+8)

STEP 1 Load properties

$V_F = 3.5\text{V} @ 25\text{mA}$

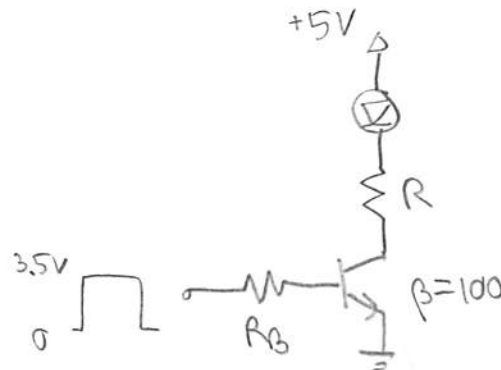

STEP 2 Saturated BJT

$$\text{KVL: } 5 - \boxed{V_F} - \boxed{I_C} R - \boxed{V_{CE}} = 0 \Rightarrow R = \frac{5 - 3.5}{0.025 \text{ A}} = 60 \Omega$$

3.5V 25mA 0V

Choose $\boxed{56 \Omega} = R$

STEP 3 Base current drive

$$I_B = \frac{1}{\beta} I_C = \frac{25 \text{ mA}}{10} = 2.5 \text{ mA} \Rightarrow R_B = \frac{3.5 - 0.7}{2.5 \text{ mA}}$$

= 1.12k


Choose $\boxed{R_B = 1.1 \text{ k}}$

1.2k is also OK

7.4 (18)

STEP 1 Load properties

$$V_L = 6 \text{ V @ } 120 \text{ mA}$$

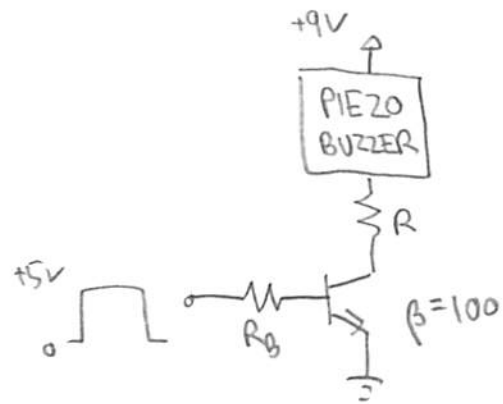

STEP 2 Saturated BJT

$$\text{KVL: } 9 - \boxed{V_{\text{LOAD}}} - \boxed{I_C} R - \boxed{V_{CE}} = 0 \Rightarrow R = \frac{9 - 6}{0.12 \text{ A}} = 25 \Omega$$

6V 120mA 0V

Choose $\boxed{R = 24 \Omega}$

STEP 3 Base current drive

$$I_B = \frac{1}{\beta} I_C = \frac{120 \text{ mA}}{10} = 12 \text{ mA} \Rightarrow R_B = \frac{5 - 0.7}{12 \text{ mA}}$$

Choose $\boxed{R_B = 330 \Omega}$

360Ω is also OK



14.11 According to Table 14-1, BS107 has

(+8) $V_{GS,ON} = 2.6V, R_{DS,ON} = 28\Omega, I_{D,ON} = 20mA$

MOSFET is ON because $+3V > 2.6V$

Ohmic region: $I_D = \frac{15V}{1.8k + 0.028k} = 8.2mA < 20mA \checkmark$

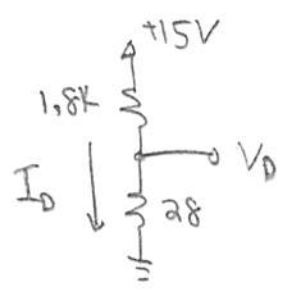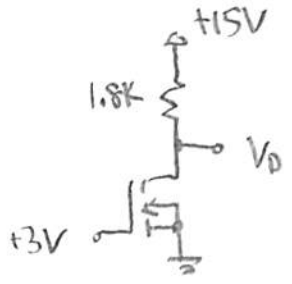$\Rightarrow V_D = I_D \times 28 = (8.2mA)(0.028k) = 0.23V$





14.14

(+8) MOSFET is ON since $+5V = V_{GS,ON}$

Assume $V_F = 2V$

Compute I_D using KVL:

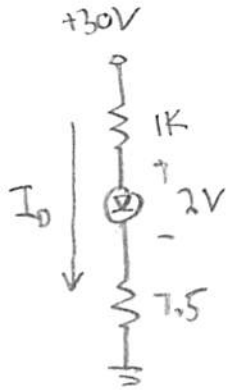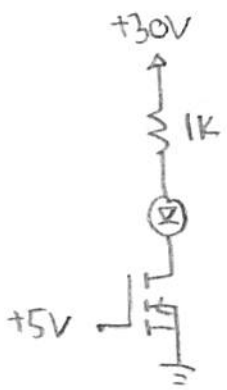

$30 - I_D(1000) - 2 - I_D(7.5) = 0$


$I_D = \frac{30-2}{1000+7.5} = 0.0278A = 27.8mA < 200mA$ Ohmic region \checkmark

14.15

When MOSFET is ON,

(+8) $R_{DS,ON} = 28\Omega$

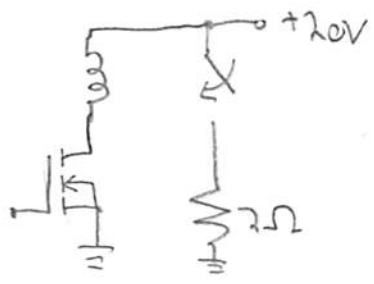$I_D = \frac{20V}{1k + 0.028k} = 19.5mA < 20mA$ HIGH Ohmic region \checkmark



Load current = $\frac{20V}{2\Omega} = 10A \leftarrow$ Large!


14.27

(+8) DARK → Photodiode is OFF

$$V_{GATE} = 15 \frac{2M}{2M+1M} = \underline{10V} = V_{GS,ON}$$

⇒ MOSFET is ON
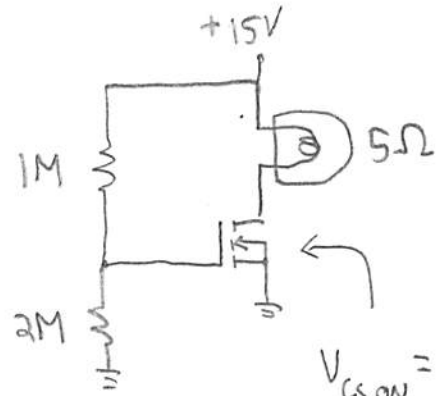
$$I_D = \frac{15}{5 + 1.07} = 2.47A < \overbrace{5A}^{I_{D,ON}} \quad \text{ohmic region} \checkmark$$



$$V_{GS,ON} = 10V$$

$$I_{D,ON} = 5A$$


$$R_{DS,ON} = 1.07\Omega$$

$$\text{Lamp power} = I^2 R = (2.47A)^2 (5\Omega) = \boxed{30.5W}$$

14.2

When CONTROL = 12V

$Q_3 = \text{OFF}$	$Q_4 = \text{ON}$
$Q_1 = \text{ON}$	$Q_2 = \text{OFF}$

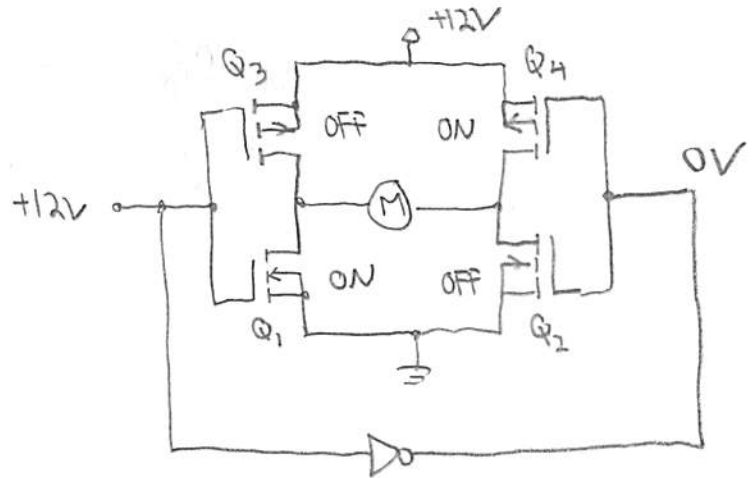


Motor equivalent resistance²

12V rating @ 500mA

$$\rightarrow R_M = \frac{12V}{.5A} = \underline{24\Omega}$$
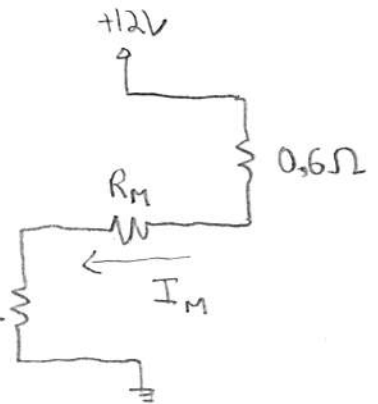
$$I_M = \frac{12}{0.6 + 24 + 0.27} = \boxed{0.483A} < 5A \quad \text{ohmic region} \checkmark$$



$$V_M = I_M R_M = (.483A)(24\Omega) = \boxed{11.6V}$$

$$P_M = I_M V_M = (.483A)(11.6V) = \boxed{5.6W}$$

16.33

+4


$$f_1 = \frac{1}{2\pi(50 + R_{in})(10^{-6}F)}$$

↑
(10k // 2.2k) // 201 r_e'

• Stiff divider? $10k // 2.2k = 1.8k$
 $\frac{201}{100} \times 1k = 2.01k$ ✓

$$\Rightarrow R_{in} = 1800 // [201(23.6)] = \underline{\underline{1305\Omega}}$$
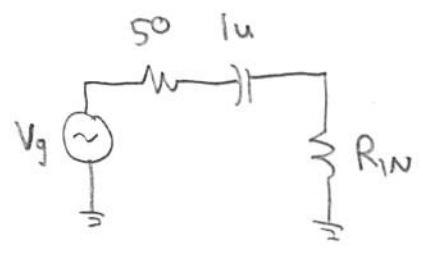
$$\Rightarrow f_1 = \frac{1}{2\pi(50 + 1305)(10^{-6})} = \boxed{117.5 \text{ Hz}}$$



$$V_{BB} = 10 \frac{2.2k}{2.2k + 10k} = 1.8V$$


$$I_{EQ} = \frac{1.8 - 0.7}{1k} = 1.1 \text{ mA}$$

$$r_e' = \frac{0.026}{0.0011A} = \underline{\underline{23.6\Omega}}$$

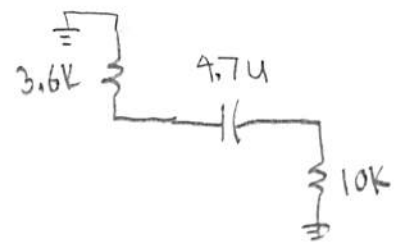16.34

+4

$$f_1 = \frac{1}{2\pi(3600 + 10000)(4.7 \times 10^{-6})} = \boxed{2.49 \text{ Hz}}$$




16.35

+4

$$f_1 = \frac{1}{2\pi \left[1000 // \left(23.6 + \frac{50/1800}{201} \right) \right] (25 \times 10^{-6})}$$


$$= \boxed{273.4 \text{ Hz}}$$

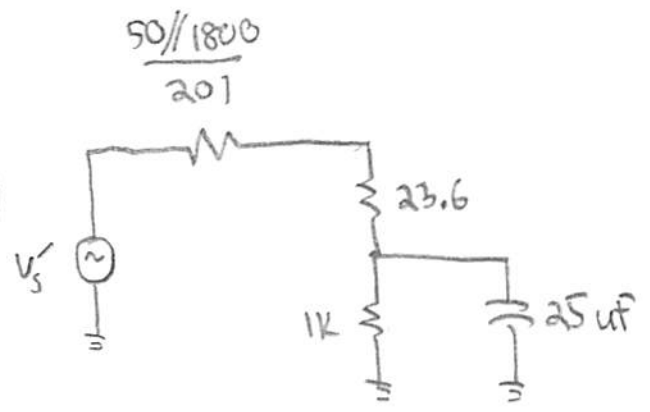

16.x +12

$C_{IN}: f_1 = \frac{1}{2\pi(R_S + R_{IN})C_{IN}}$

\uparrow 680Ω \uparrow ? \uparrow 1μ

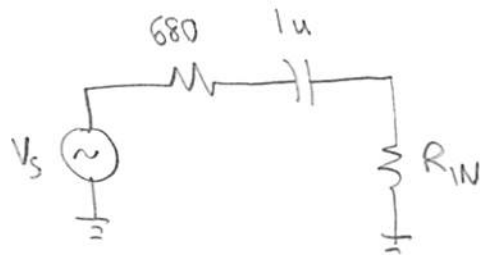

$R_{IN} = (6.8k \parallel 4.7k) \parallel 201(r_e' + 220)$

? \uparrow

$V_{BB} = 12 \frac{4.7k}{4.7k + 6.8k} = 4.9V$

Stiff divider? $6.8k \parallel 4.7k = 2.78k$

$\frac{201}{100}(1.2k + .22k) = 2.85k$

$I_{EQ} = \frac{4.9 - 0.7}{.22k + 1.2k} = 2.96mA$

$r_e' = \frac{.026V}{2.96mA} = .0088k$

$= \underline{\underline{8.8\Omega}}$


$\rightarrow R_{IN} = 2.78k \parallel 201(8.8 + 220) = \underline{\underline{2.62k}}$

46k

$\Rightarrow f_1 = \frac{1}{2\pi(680 + 2620)(10^{-6})} = \boxed{48.2Hz}$

$C_{OUT}: f_1 = \frac{1}{2\pi(2700 + 3300)(100 \times 10^{-9})}$


$= \boxed{265.3Hz}$

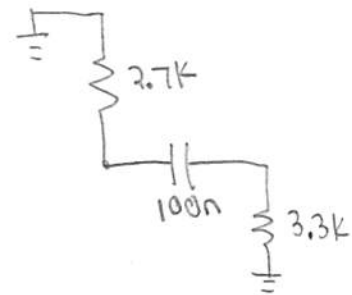

$C_E:$

$f_1 = \frac{1}{2\pi \left[1200 \parallel \left(220 + 8.8 + \frac{680 \parallel 2780}{201} \right) \right] (100 \times 10^{-6})}$

$= \boxed{8.2Hz}$

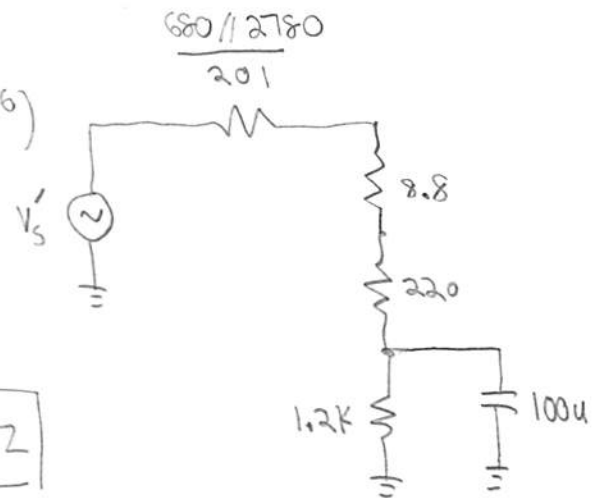


➔ Dominant low cut-off freq = $\boxed{265.3Hz}$

\uparrow Due to C_{OUT}

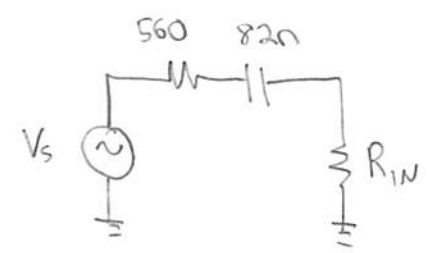16.4 (12)

• $C_{IN}: f_1 = \frac{1}{2\pi (560 + R_{IN}) (82 \times 10^{-9})}$



$R_{IN} = (12K // 15K) // 2501 (r_e' + 330 // 150)$

• Stiff divider? $12K // 15K = 6.67K$
 $\frac{2501}{100} \cdot 33K = 8.25K$] YES

$V_{BB} = 10 \frac{15K}{15K + 12K} = 5.56V$

$I_{EQ} = \frac{5.56 - 1.4}{330} = .0126A$


$r_e' = \frac{.026}{.0126A} = \underline{\underline{2.1\Omega}}$

$\rightarrow R_{IN} = 6.67K // 2501 (2.1 + 103.1) = \underline{\underline{6.505K}}$
263K

$\Rightarrow f_1 = \frac{1}{2\pi (560 + 6505) (82 \times 10^{-9})} = \boxed{274.7 \text{ Hz}}$

• $C_{OUT}: f_1 =$

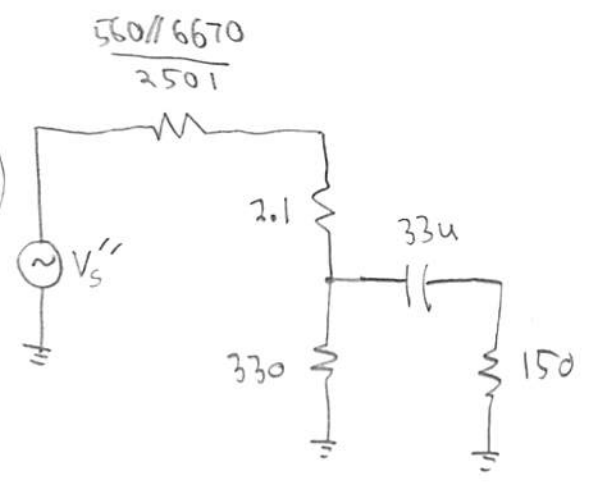$f_1 = \frac{1}{2\pi [150 + 330 // (2.1 + \frac{560 // 6670}{2501})] (33 \times 10^{-6})}$
2.31
 $= \boxed{31.7 \text{ Hz}}$



\Rightarrow Dominant low cut-off freq = $\boxed{274.7 \text{ Hz}}$ ← Due to C_{IN}