


Union College
ECE 248
Spring 2015
Homework #3

Due Thursday April 28, 2015

Unless otherwise noted, all problems from Malvino & Bates (7th ed)

A. BJT Basics (Read Textbook Ch 6.3 - 6.5)

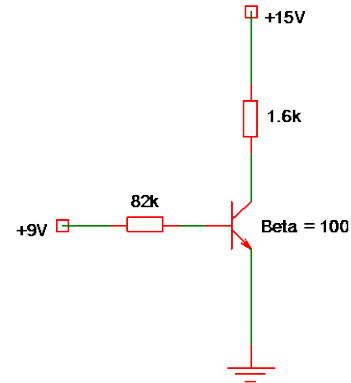
- 6.5 You should get $I_B = 0.02 \text{ mA}$.
 6.8 You should get $V_{CE} = 11\text{V}$.
 7.14 You should get $V_{CE,MIN} = 4.11\text{V}$ and $V_{CE,MAX} = 4.70\text{V}$.
 7.xx For the figure to the right, determine if the transistor is in active mode.



Hint: You should find that $V_{CE} = -1.2\text{V}$, which means the transistor is NOT in active mode.


B. Voltage Divider Biasing (Read Textbook Ch 8.1, 8.2)

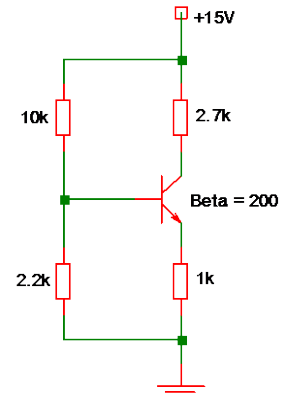- 8.xx (Based on Problem 8.2 in textbook)
 (a) Show that the voltage divider is stiff.
 (b) Show that $V_{BB} = 2.7 \text{ V}$.
 (c) Show that $V_{CQ} = 9.6 \text{ V}$.
 (d) Show that $V_{CEQ} = 7.6\text{V}$.



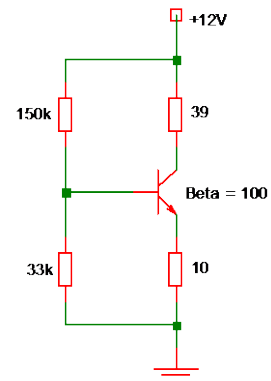- 8.yy (Based on Problem 8.24 in textbook)
 (a) Show that the biasing voltage divider has $V_{TH} = 2.16\text{V}$.
 (b) Show that the voltage divider is NOT stiff.
 (c) Show that the base voltage is actually $V_{BB} = 0.75\text{V}$, which is much less than $V_{TH} = 2.16\text{V}$!

Hint: Using the Thevenized voltage divider, use KVL to determine the base current I_B . Once you know I_B you can compute the base voltage V_{BB} .



NOTE: This problem should highlight why a stiff divider makes it much easier to determine V_{BB} !

C. Amplifier Gain (Read Textbook Ch 9.3 - 9.7, 10.1)

9.19 Use the T-model for the AC circuit. You should $R_1//R_2 = 271 \text{ ohm}$, $R_C//R_L = 1.02 \text{ kohm}$, and $r_e' = 6.1 \text{ ohm}$.

9.xx Compute the small signal voltage gain of the amplifier in Problem 9-19. Use $\beta = 200$. Your answer should be $V_{OUT}/V_{IN} = -166$.

9.yy


(a) Draw the AC equivalent circuit using the T-model. You should get $r_e' = 42.6 \text{ ohm}$.

(b) Compute the small signal voltage gain of the amplifier. Assume $\beta = 200$.

You should get $V_{OUT}/V_{IN} = -212$.

(c) What is the gain if the 100 kohm load resistor is replaced with a 1 kohm load resistor?

You should get $V_{OUT}/V_{IN} = -21$.

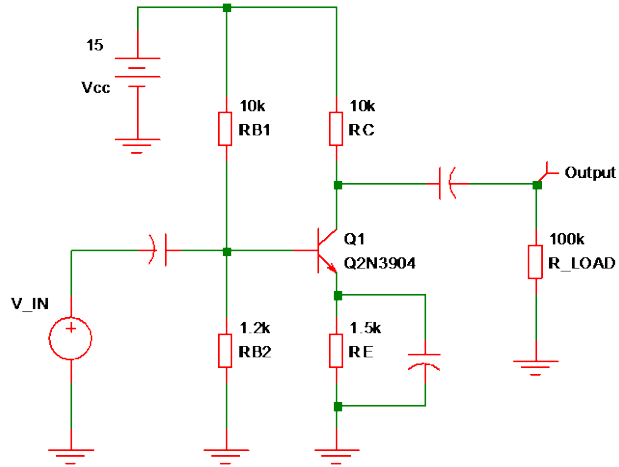

10.xx

(a) What is the value of r_e' in Fig. 10-13 of the textbook? Use $V_T = 26 \text{ mV}$. You should get $r_e' = 23.6 \text{ ohm}$.

(b) Draw the AC equivalent circuit of Fig. 10-13.

(c) Compute the AC output voltage for $V_{IN} = 2 \text{ mV}$. Assume $\beta = 200$. Your answer should be $V_{OUT} = -223 \text{ mV}$.

D. Base and Input Impedance (Read Textbook Ch 10.2)

9.17 You should get $R_{BASE} = 2.49 \text{ kohm}$

9.18 You should get $R_{BASE} = 1.23 \text{ kohm}$

10.5 You should get $r_e' = 47.3 \text{ ohm}$, $R_{IN} = 1.31 \text{ kohm}$, and $V_{OUT} = -38 \text{ mV}$

10.6 You should get $r_e' = 23.6 \text{ ohm}$, $R_{IN} = 1.03 \text{ kohm}$, and $V_{OUT} = -86 \text{ mV}$

Spring 2015