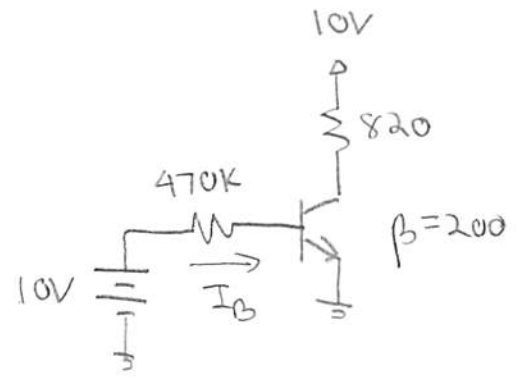


ECE 248
HW 3 Solutions

Total = 100 pts

6.5


$$I_B = \frac{10 - 0.7}{470K} = 0.02 \text{ mA}$$



+5

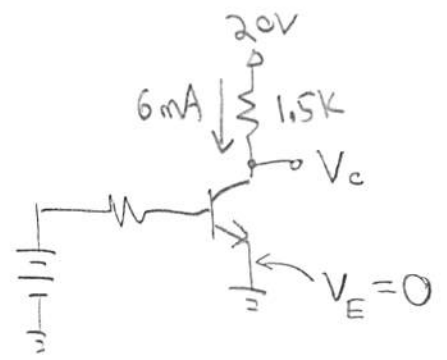6.8


$$\begin{aligned} V_{CE} &= V_C - V_{E \rightarrow 0} \\ &= V_C \\ &= V_{CC} - I_C R_C \\ &= 20 - (6 \text{ mA})(1.5K) = 11 \text{ V} \end{aligned}$$



+5

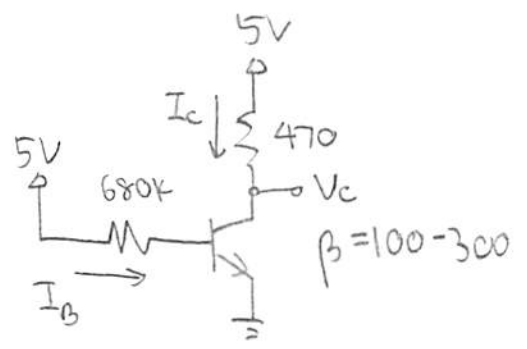7.14

$$\begin{aligned} V_{CE} &= V_C - V_{E \rightarrow 0} \\ &= V_{CC} - I_C R_C \\ &= V_{CC} - \beta I_B R_C \end{aligned}$$
$$I_B = \frac{5 - 0.7}{680K} = 0.0063 \text{ mA}$$




+8

$$\beta = 100: V_{CE} = 5 - 100 \times 0.0063 \text{ mA} \times 470K = 4.7 \text{ V}$$

$$\beta = 300: V_{CE} = 5 - 300 \times 0.0063 \text{ mA} \times 470K = 4.11 \text{ V}$$

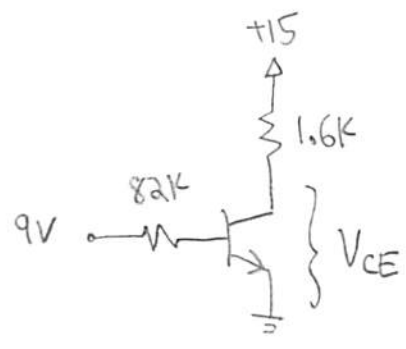7.xx Need to find V_{CE}

(+5) $V_{CE} = V_C - V_E$
 $= V_{CC} - I_C R_C$
 $= V_{CC} - \beta I_B R_C$



$\frac{9 - 0.7}{82k} = 0.101mA$

$= 15 - 100 \times 0.1mA \times 1.6k = -1.2V < 0$


NOT in active mode!

8.xx

(+8) a) stiff divider?

$10k // 2.2k = 1.8k$
 $\frac{200+1}{100} \times 1k = 2.01k$

YES

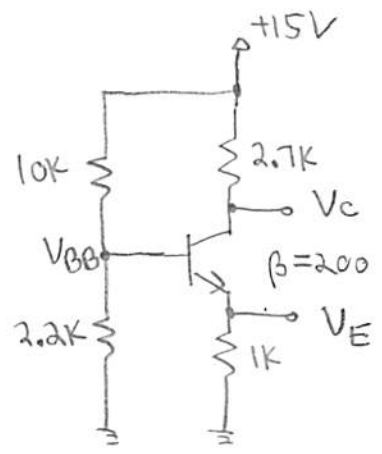

b) $V_{BB} = 15 \frac{2.2k}{2.2k + 10k} = 2.7V$

$\alpha = \frac{200}{201} = .995$

c) $V_{CQ} = V_{CC} - I_{CQ} R_C = V_{CC} - \alpha I_{EQ} R_C$

$\frac{2.7 - 0.7}{1k} = 2mA$

$= 15 - .995 \times 2mA \times 2.7k$

$= 9.63V$

d) $V_{CEQ} = V_{CQ} - V_{EQ} = 9.63 - 2 = 7.63V$

$\frac{2.7 - 0.7}{1k} = 2V$

8.44

78


(a) Thevenize the divider!

$$V_{TH} = 12 \cdot \frac{33K}{33K + 150K} = \boxed{2.16V}$$

$$(b) R_{TH} = 150K \parallel 33K = \underline{\underline{27K}}$$

$$\frac{\beta + 1}{100} \times .010K = \frac{201}{100} \times .010K = \underline{\underline{.02K}}$$

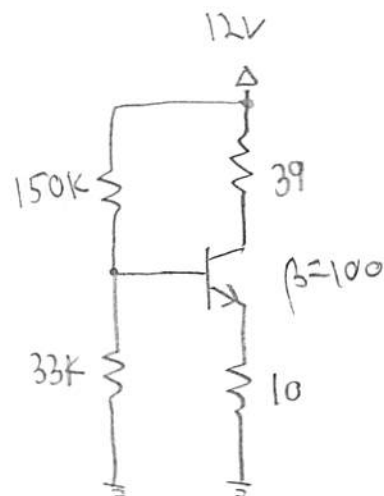
$27K > .02K$! Divider is nowhere close to being stiff!



(c) KVL:

$$2.16 - I_B \times 27K - 0.7 - I_E \times 10 = 0$$

\uparrow
 $(\beta + 1)I_B$

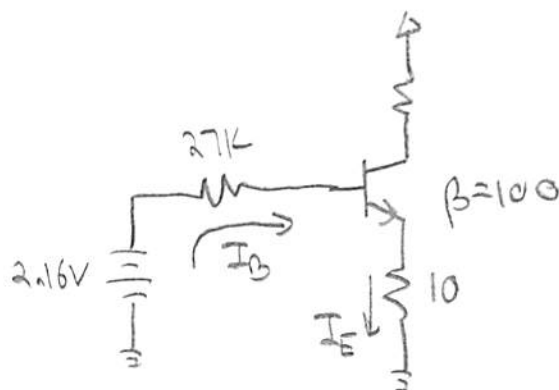


$$I_B = \frac{2.16 - 0.7}{27K + 101 \times .010K} = .052mA$$

$$V_{BB} = 2.16 - I_B \times 27K = 2.16 - .052mA \times 27K = \boxed{0.75V}$$

9.19

For AC equivalent circuit:

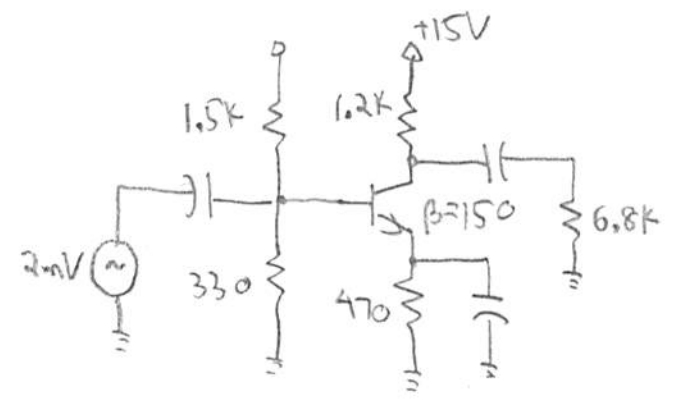

① All DC voltages become AC grounds

② $R_c \parallel R_L = r_c = 1.2K \parallel 6.8K = \underline{\underline{1.02K}}$


$R_1 \parallel R_2 = 1.5K \parallel .33K = \underline{\underline{.271K}}$

③ Use T-model \leftarrow need r_e'

Stiff divider? $1.5K \parallel .33K = .271K$
 $\frac{150+1}{100} \times .47K = .71K$ ✓

$\rightarrow V_{BB} = 15 \frac{.330}{.330 + 1500} = 2.71V$

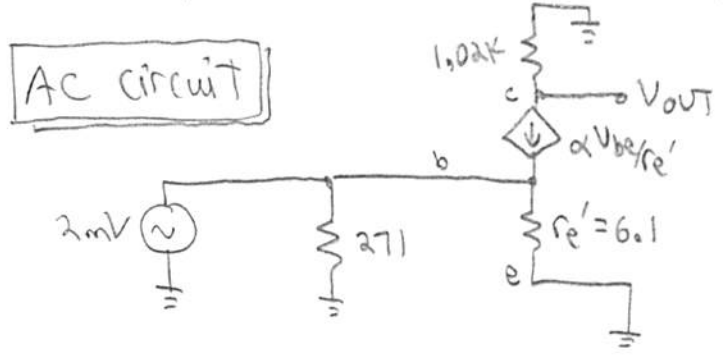$\Rightarrow I_{EQ} = \frac{2.71 - 0.7}{470} = .0043 A \Rightarrow r_e' = \frac{.026}{.0043 A} = \underline{\underline{6.1 \Omega}}$



9.XX

$\frac{V_{OUT}}{V_{IN}} = -\alpha \frac{r_c}{r_e'} = -.995 \frac{1020}{6.1} = \underline{\underline{-166.4}}$

9.5


$\frac{200}{201} = .995$

9.44 (78)

$$\textcircled{a} \bullet r_c = R_c // R_L$$

$$= 10\text{K} // 100\text{K} = \underline{\underline{9.1\text{K}}}$$

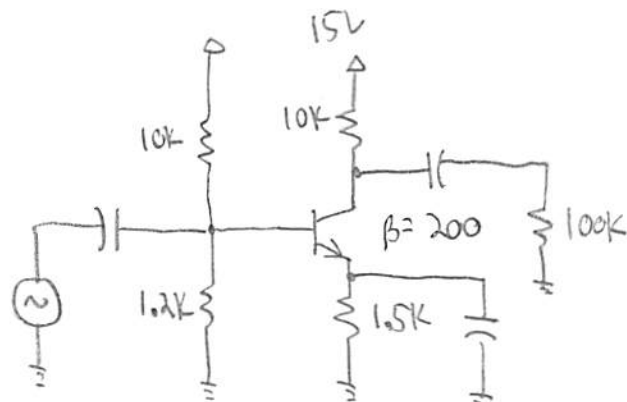
$$\bullet R_1 // R_2 = 10\text{K} // 1.2\text{K} = \underline{\underline{1.07\text{K}}}$$



$$\bullet \text{stiff divider? } \left. \begin{array}{l} 10\text{K} // 1.2\text{K} = 1.07\text{K} \\ \frac{201}{100} \cdot 1.5\text{K} = 3\text{K} \end{array} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{1.2\text{K}}{1.2\text{K} + 10\text{K}} = 1.61\text{V}$$
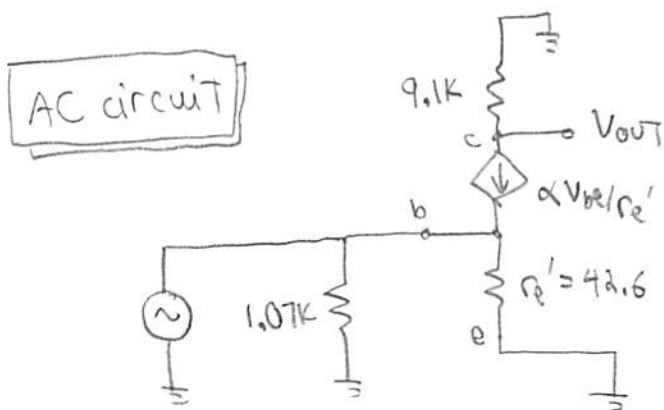
$$\Rightarrow I_{EQ} = \frac{1.61 - 0.7}{1.5\text{K}} = 0.61\text{mA} \Rightarrow r_e' = \frac{0.026}{0.61 \times 10^{-3}\text{A}} = \underline{\underline{42.6\Omega}}$$



$$\textcircled{b} \frac{V_{OUT}}{V_{IN}} = -\alpha \frac{r_c}{r_e'} = -0.995 \frac{9.1\text{K}}{0.0426\text{K}} = \boxed{-212.6}$$

$$\textcircled{c} r_c = 10\text{K} // 1\text{K} = \underline{\underline{0.91\text{K}}}$$

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = -0.995 \frac{0.91\text{K}}{0.0426\text{K}} = \boxed{-21.3}$$

10.xx (18)


a) stiff divider?

$$10k // 2.2k = 1.8k$$


$$\frac{10}{100} \cdot 1k = 2.01k$$

$$\rightarrow V_{BB} = 10 \frac{2.2k}{2.2k + 10k} = 1.8V$$
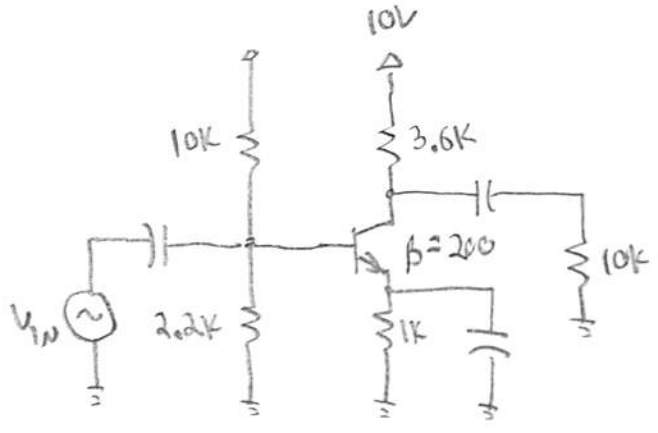
$$\Rightarrow I_{EQ} = \frac{1.8 - 0.7}{1k} = 1.1mA \Rightarrow r_e' = \frac{0.026}{0.0011} = 23.6\Omega$$



b) $r_c = 3.6k // 10k = 2.65k$

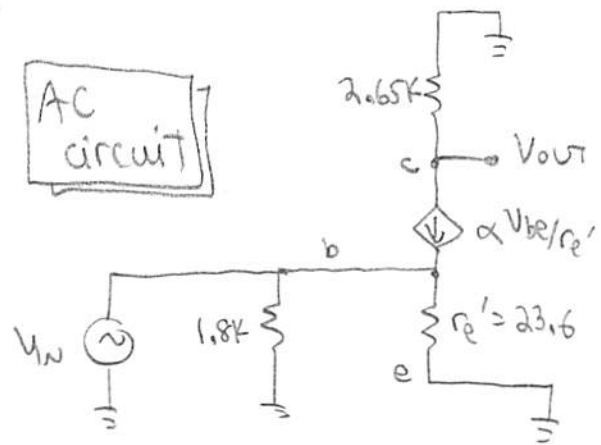

$$c) V_{out} = \left(\frac{V_{out}}{V_{in}} \right) \cdot 2mV = \left(-\alpha \frac{r_c}{r_e'} \right) 2mV = \left(-0.995 \frac{2.65k}{0.0236k} \right) \cdot 2mV$$

$$= -223.5mV$$

9.17

+8

$$R_{base} = (\beta + 1) r_e'$$


Stiff divider?

$$\left. \begin{aligned} 1.5K // .33K &= 0.27K \\ \frac{201}{100} \cdot .94K &= 1.89K \end{aligned} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{.33K}{.33K + 1.5K} = 2.7V$$

$$\Rightarrow I_{EQ} = \frac{2.7 - 0.7}{.94K} = 2.1mA \Rightarrow r_e' = \frac{.026}{.0021A} = \underline{12.4\Omega}$$
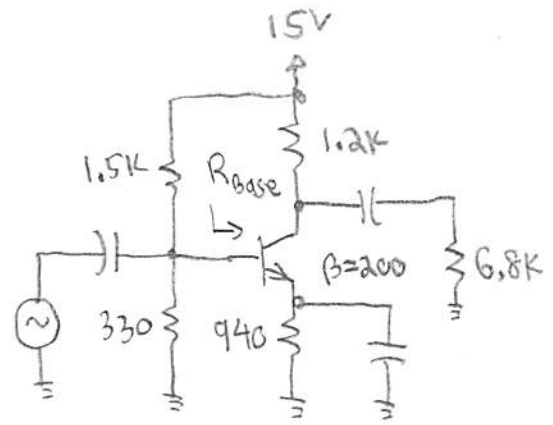
$$R_{base} = (201)(12.4\Omega) = \boxed{2492\Omega}$$



9.18

+8

$$R_{base} = (\beta + 1) r_e'$$


Stiff divider?

$$\left. \begin{aligned} 1.5K // .33K &= 0.27K \\ \text{vs.} \\ \frac{201}{100} \cdot .47K &= 0.94K \end{aligned} \right\} \checkmark$$

$$\Rightarrow V_{BB} = 15 \frac{.33K}{.33K + 1.5K} = 2.7V$$

$$\Rightarrow I_{EQ} = \frac{2.7 - 0.7}{470} = 4.26 \times 10^{-3} A \Rightarrow r_e' = \frac{.026}{.00426} = \underline{6.1\Omega}$$
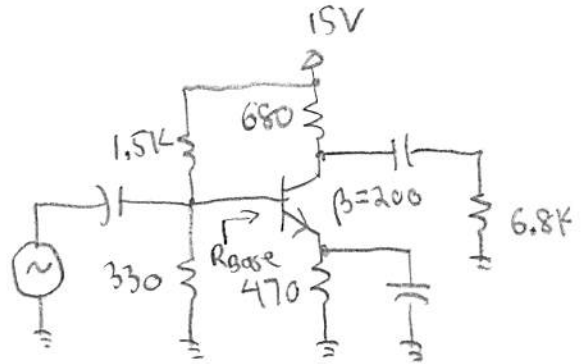
$$R_{base} = (201)(6.1) = \boxed{1226\Omega}$$




10.5

+8

$$\frac{V_{OUT}}{V_S} = \frac{R_{IN}}{R_{IN} + R_S} \cdot \frac{V_{OUT}}{V_{IN}}$$

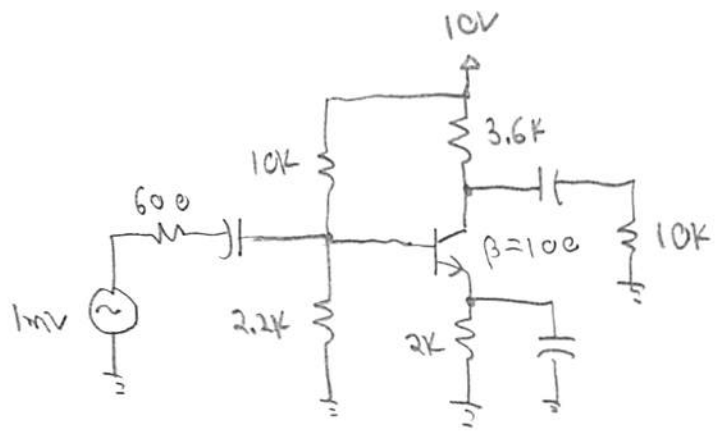\uparrow $(10k // 2.2k) // (\beta + 1)r_{e'}$ \uparrow $-\alpha \frac{r_c}{r_{e'}}$



Need to find $r_{e'}$!

- Stiff divider? $10k // 2.2k = 1.8k$ vs. $\frac{101}{100} 2k = 2.02k$ ✓

$$\Rightarrow V_{BB} = 10 \frac{2.2k}{10k + 2.2k} = 1.8V$$

$$\Rightarrow I_{EQ} = \frac{1.8 - 0.7}{2k} = 0.55mA \Rightarrow r_{e'} = \frac{.026}{.55 \times 10^{-3}A} = \underline{\underline{47.3\Omega}}$$

- $r_c = R_C // R_L = 3.6k // 10k = 2.65k$

$$\frac{V_{OUT}}{V_{IN}} = -0.99 \frac{2.65k}{.0473k} = \underline{\underline{-55.5}}$$

$$\alpha = \frac{100}{101} = 0.99$$

$$R_{IN} = (10k // 2.2k) // 101(.0473k) = \underline{\underline{1.31k}}$$

$$\Rightarrow \frac{V_{OUT}}{V_S} = \frac{1.31k}{1.31k + .6k} \times (-55.5) = -38.1$$

$$V_{OUT} = \left(\frac{V_{OUT}}{V_S} \right) \times V_S = (-38.1)(1mV) = \boxed{-38.1mV}$$


10.6 (48)

$$V_{out} = \left(\frac{V_{out}}{V_s} \right) \times V_s$$

$$= \frac{R_{in}}{R_{in} + R_s} \left(\frac{V_{out}}{V_{in}} \right) \times V_s$$

↑

$$- \alpha \frac{r_c}{r_e'}$$

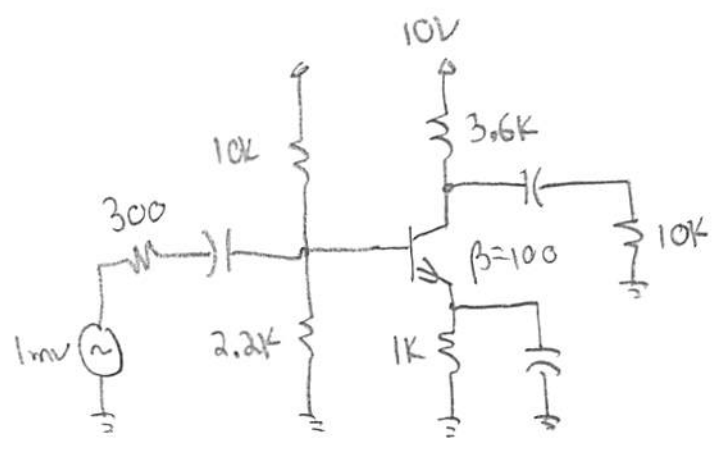

Find r_e' !

• Stiff divider? $10K \parallel 2.2K = 1.8K$
 vs.
 $\frac{10V}{100} \times 1K = 1.01K$

oops! Not stiff, but OK to ignore for this problem. (sorry about that...)

$$V_{BB} = 10 \frac{2.2K}{2.2K + 10K} = 1.8V$$

$$\rightarrow I_{EQ} = \frac{1.8V - 0.7V}{1K} = 1.1mA \Rightarrow r_e' = \frac{0.026}{1.1 \times 10^{-3}A} = 23.6\Omega$$

• $r_c = 3.6K \parallel 10K = 2.65K$

$$\frac{V_{out}}{V_{in}} = -\alpha \frac{r_c}{r_e'} = -0.99 \frac{2.65K}{0.0236K} = -111.2$$

$$R_{in} = (10K \parallel 2.2K) \parallel 101(0.0236K) = 1.026K$$

$$\frac{V_{out}}{V_s} = \frac{1.026K}{1.026K + 300} (-111.2) = -86$$

$$V_{out} = (-86) \times 1mV = \boxed{-86mV}$$