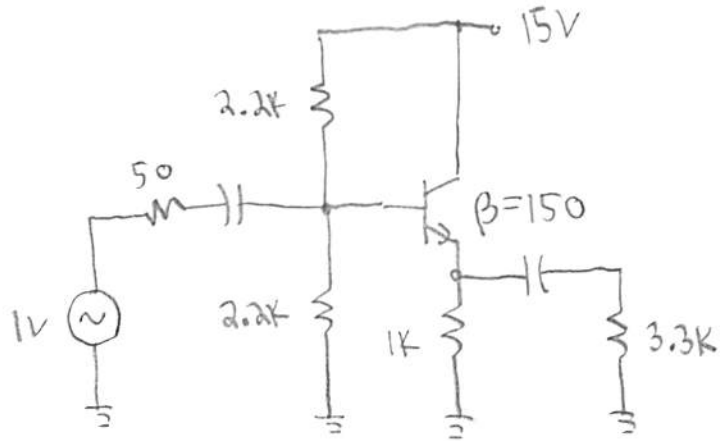


11.3 Emitter follower!

(+9)
$$\frac{V_{OUT}}{V_S} = \frac{R_{IN}}{R_{IN} + R_S}$$

$\frac{V_{OUT}}{V_{IN}}$
 \uparrow
 $\frac{r_e}{r_e + r_e'}$



$r_e = 1000 // 3300 = \underline{767.4}$

$\Rightarrow V_{BB} = 15 \frac{2.2k}{4.4k} = 7.5V$

$r_e' ?$ Stiff divider? $2.2k // 2.2k = 1.1k$
 $\frac{151}{100} \times 1k = 1.51k$

$I_{EQ} = \frac{7.5 - 0.7}{1k} = \underline{6.8mA}$

$r_e' = \frac{0.026}{6.8 \times 10^{-3}} = \underline{3.82 \Omega}$

$\Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{767.4}{767.4 + 3.82} = \underline{0.995}$

$R_{IN} = \underbrace{(2.2k // 2.2k)}_{1.1k} // \left[\underbrace{151 (3.82 + 767.4)}_{116.5k} \right] = \underline{1.09k}$

$\Rightarrow \frac{V_{OUT}}{V_S} = \frac{1090}{1090 + 50} \times 0.995 = \boxed{0.95}$

11.8 (+9)

$$\frac{V_{out}}{V_s} = \frac{R_{in}}{R_{in} + R_s} \times \frac{r_e}{r_e + r_e'}$$

$$r_e = 30 // 10 = \underline{7.5}$$

$r_e' ?$

Stiff divider? $100 // 200 = 67$
 $\frac{176}{100} 30 = 52.8$

Not stiff, but close enough

$$V_{BB} = 20 \frac{200}{300} = \underline{13.33}$$


$$I_{EQ} = \frac{13.33 - 0.7}{30} = 0.42 A$$

$$R_{in} = \underbrace{(100 // 200)}_{67} // \left[\underbrace{176}_{1331} (.062 + 7.5) \right]$$

$$r_e' = \frac{.026 V}{.42 A} = \underline{1062 \Omega}$$

$$= \underline{63.8 \Omega}$$
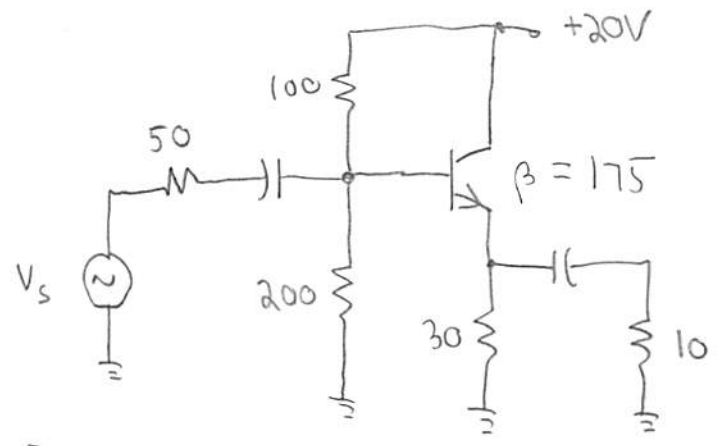
$$\Rightarrow \frac{V_{out}}{V_s} = \frac{63.8}{63.8 + 50} \times \frac{7.5}{7.5 + .062} = \boxed{0.556}$$




11.17 (+9)

$$R_{base} = (150 \times 150 + 1)(r_e' + r_e)$$

? \uparrow
 $10 // 8 = 4.44$

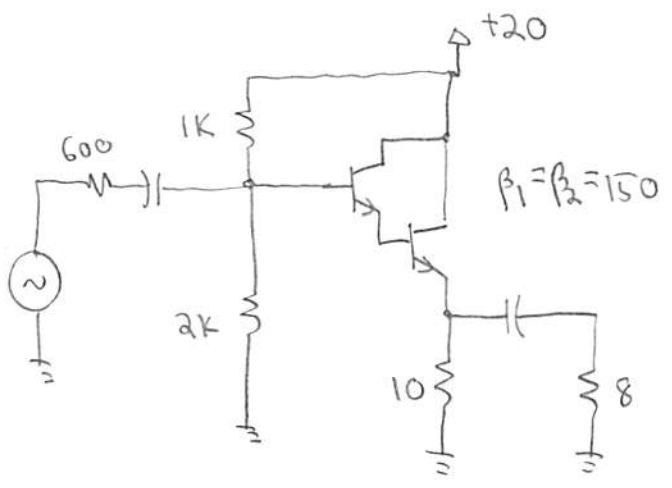Stiff divider? $1K // 2K = 667$
 $\frac{(22501)}{100} 10 = 2250$ ✓



$$V_{BB} = 20 \frac{2K}{3K} = 13.33 V$$

$$I_{EQ} = \frac{13.33 - 1.4}{10} = 1.19 A \Rightarrow r_e' = \frac{.026}{1.19} A = \underline{.022 \Omega}$$

$$R_{base} = 22501 (.022 + 4.44) = \boxed{100.4 K}$$

11.22

For previous problem,

$$\frac{4.44}{4.44 + 0.022} = \underline{\underline{0.995}}$$

+9

$$\frac{V_{OUT}}{V_S} = \frac{R_{IN}}{R_{IN} + R_S} \left[\frac{r_e}{r_e + r_e'} \right]$$

$$\uparrow \quad \quad \quad \uparrow$$
$$\left(\underbrace{1K // 2K}_{.667K} \right) // \underbrace{R_{base}}_{100.4K} = \underline{\underline{0.663K}}$$


$$= \frac{663}{663 + 600} \times .995 = \boxed{0.52}$$

11.19

+5

$$V_{OUT} = V_Z - 0.7$$
$$= \boxed{6.8V}$$
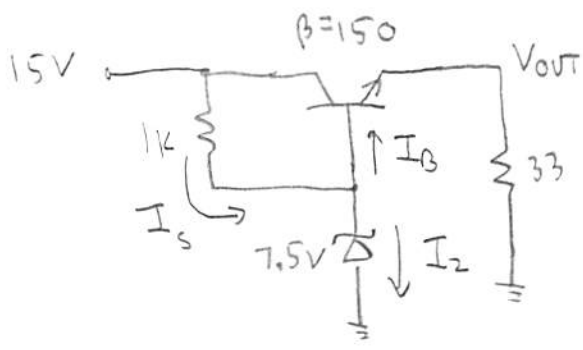
$$I_2 = I_S - I_B$$
$$= \frac{15 - 7.5}{1K} - \frac{1}{151} \times \frac{6.8V}{.033K}$$
$$= \underline{\underline{6.14 mA}}$$



11.28


+5

$$P = I_E V_{CE}$$

$$I_E = \frac{7.5 - 0.7}{33} = \underline{\underline{0.21A}}$$

$$V_{CE} = V_C - V_E = 15 - (7.5 - 0.7) = \underline{\underline{8.2V}}$$

$$P = (0.21A)(8.2V) = \boxed{1.72W}$$

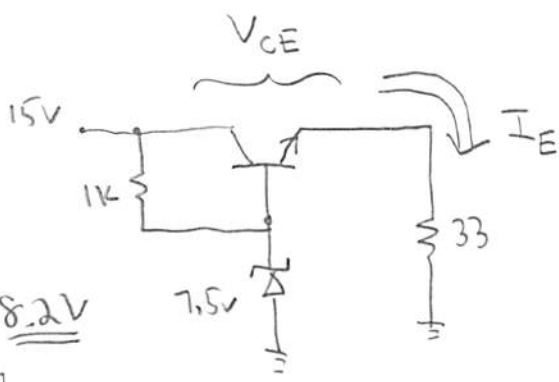


← Gets pretty warm!

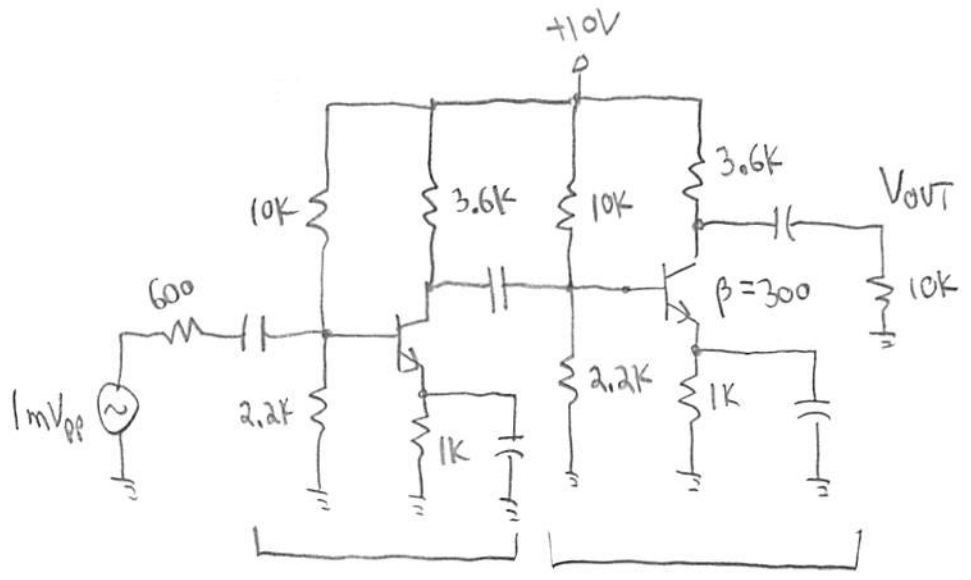10.9 (+9)

$$V_{out} = \frac{V_{out}}{V_s} V_s$$

$$= \frac{R_{in}}{R_{in} + R_s} A_1 A_2 V_s$$



Start with A_2 ?

stiff divider? $10k // 2.2k = 1.8k$
 $\frac{301}{100} \times 1k = 3.01k$ ✓

$$A_1 = -\alpha \frac{R_c // R_{in2}}{r_{e1}}$$

$$A_2 = -\alpha \frac{R_c // R_L}{r_{e2}}$$

$$\rightarrow V_{BB} = 10 \frac{2.2k}{12.2k} = 1.8V \Rightarrow I_{EQ} = \frac{1.8 - 0.7}{1k} = \underline{1.1mA} \Rightarrow r_{e2}' = \frac{0.026}{1.1mA} = \underline{0.0236k}$$

$$\rightarrow r_{c2} = 3.6k // 10k = \underline{2.65k}$$

$$\Rightarrow A_2 = -\frac{300}{301} \times \frac{2.65k}{0.0236k} = \underline{-111.9}$$

$$R_{in2} = (10k // 2.2k) // 301(0.0236k) = \underline{1.44k}$$

Now compute A_1 ?

stiff divider? YES (same circuit as A_2)

$$\rightarrow r_{e1}' = r_{e2}' = \underline{0.0236k}$$

$$\rightarrow r_{c1} = 3.6k // 1.44k = \underline{1.03k}$$

$$\Rightarrow A_1 = -\frac{300}{301} \frac{1.03k}{0.0236k} = \underline{-43.5}$$

$$R_{in1} = R_{in2} = \underline{1.44k} \text{ (same circuit)}$$

$$SO, V_{out} = \frac{1.44k}{1.44k + 0.6k} (-43.5)(-111.9) \cdot 1mV_{pp} = 3436mV_{pp}$$

$$= \boxed{3.44V_{pp}}$$

10.XX (+9)

→ start with A_2

• stiff divider?

$$\left. \begin{aligned} 3.3k \parallel 1.2k &= 0.88k \\ \frac{201}{100} \cdot 4.7k &= 0.94k \end{aligned} \right\} \checkmark$$

• $V_{BB} = 12 \frac{1.2k}{1.2k + 3.3k} = 3.2V$

$I_{EQ} = \frac{3.2 - 0.7}{4.7k} = 5.32mA$

$r_{e2}' = \frac{0.026V}{5.32mA} = 0.0049k$

• $r_c = 1.2k \parallel 1k = 0.545k$

• $A_2 = - \frac{200}{201} \frac{0.545k}{0.0049k} = -110.7$

→ compute A_1

• stiff divider?


$$\left. \begin{aligned} 3.3k \parallel 5.6k &= 2.08k \\ \frac{201}{100} \cdot 1.9k &= 3.82k \end{aligned} \right\} \checkmark$$

• $V_{BB} = 12 \frac{5.6k}{5.6k + 3.3k} = 7.55V \rightarrow I_{EQ} = \frac{7.55 - 0.7}{1.9k} = 3.61mA$

$r_{e1}' = \frac{0.026V}{3.61mA} = 0.0072k$

• $r_c = 1.2k \parallel 0.465k = 0.335k$

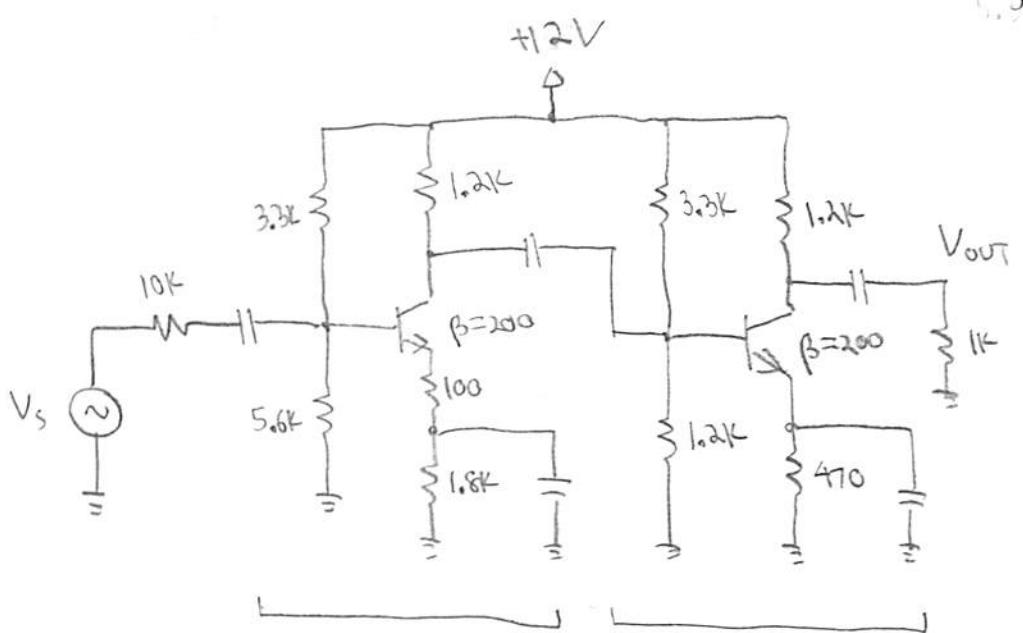• $A_1 = - \frac{200}{201} \frac{0.335k}{0.0072k + 0.1k} = -3.1$



$$A_1 = -\alpha \frac{R_c \parallel R_{w2}}{r_{e1}' + R_e} \quad A_2 = -\alpha \frac{R_c \parallel R_c}{r_{e2}'}$$

$$R_{w2} = (3.3k \parallel 1.2k) \parallel (201)(0.0049k) = 0.465k$$

$$R_{w1} = (3.3k \parallel 5.6k) \parallel 201(0.0072k + 0.1k) = 1.89k$$


$$\Rightarrow \frac{V_{OUT}}{V_S} = \frac{R_{IN}}{R_{IN} + R_S} A_1 A_2 = \frac{1.89 \text{ k}}{1.89 + 10 \text{ k}} (-3.1)(-110.7) = \boxed{54.5}$$

10.9 (19)

• stiff divider?

$$10 \text{ k} \parallel 2.2 \text{ k} = 1.8 \text{ k}$$
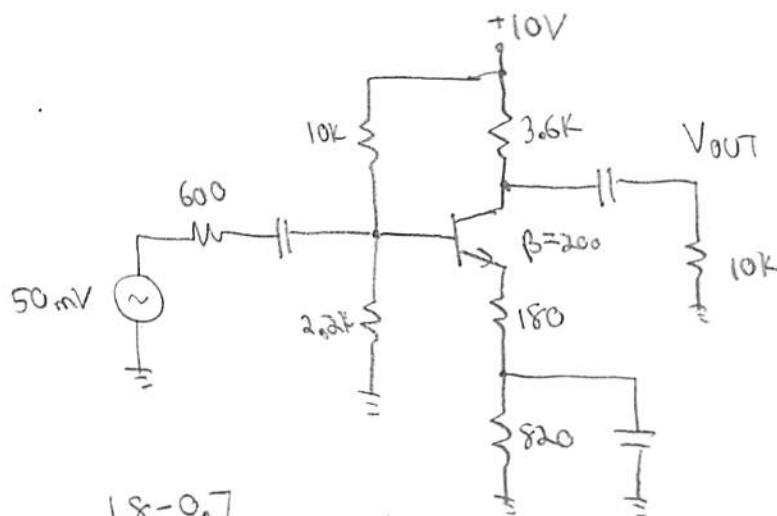
$$\frac{201}{100} \cdot 1 \text{ k} = 2.01 \text{ k}$$



$$\bullet V_{BB} = 10 \frac{2.2 \text{ k}}{2.2 \text{ k} + 10 \text{ k}} = 1.8 \text{ V} \Rightarrow I_{EQ} = \frac{1.8 - 0.7}{1 \text{ k}} = \underline{\underline{1.1 \text{ mA}}}$$

$$r_e^- = \frac{0.026 \text{ V}}{1.1 \text{ mA}} = \underline{\underline{0.0236 \text{ k}}}$$

$$\alpha = \frac{200}{201} = 0.995$$

$$\bullet r_c = 3.6 \text{ k} \parallel 10 \text{ k} = 2.65 \text{ k}$$

$$\bullet A = -\alpha \frac{r_c}{r_e^- + R_e} = -0.995 \frac{2.65 \text{ k}}{(0.0236 \text{ k} + 0.18 \text{ k})} = \underline{\underline{-12.95}}$$

$$\bullet R_{IN} = (10 \text{ k} \parallel 2.2 \text{ k}) \parallel \underbrace{201(0.0236 \text{ k} + 0.18 \text{ k})}_{40.9 \text{ k}} = \underline{\underline{1.73 \text{ k}}}$$

$$\Rightarrow V_{OUT} = 50 \text{ mV} \frac{1.73 \text{ k}}{1.73 \text{ k} + 0.6 \text{ k}} \cdot (-12.95) = \boxed{-481 \text{ mV}}$$

12.3 (19)

STEP 1 Q-Point

• stiff divider? $2k // 47k = 0.38k$
 $\frac{201}{100} \cdot 22k = 0.44k$ ✓


• $V_{BB} = 15 \frac{47k}{47k + 2k} = 2.85V$

→ $I_{EQ} = \frac{2.85 - 0.7}{220} = \underline{0.0098A}$

$\alpha = \frac{200}{201} = 0.995$

• $V_C = 15 - 0.995 (0.0098A)(680\Omega) = 8.37V$
 $V_E = 2.15V$

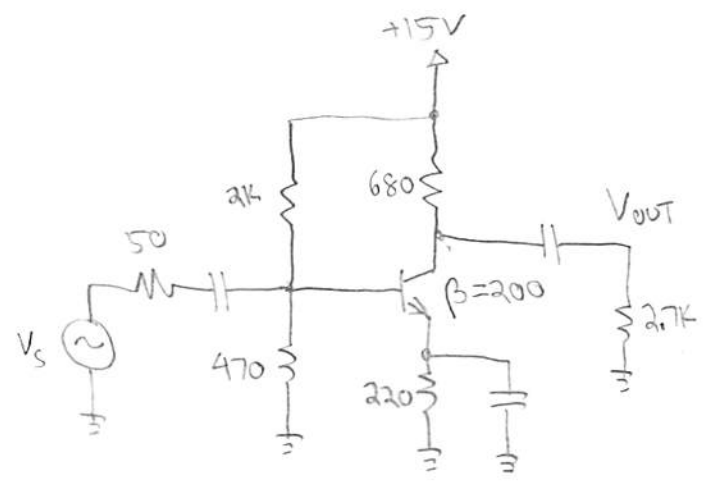$V_{CEQ} = 8.37 - 2.15 = \underline{6.22V}$




STEP 2 AC analysis

$r_c = 680 // 2700 = \underline{543\Omega}$

• $V_{OUT} = -i_c r_c = -\alpha i_e r_c$

$i_e = -\frac{V_{OUT}}{\alpha r_c}$

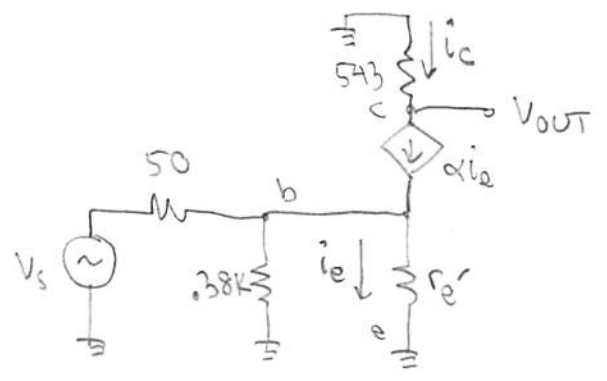• $V_{ce} = V_c - V_e = V_{OUT} - 0 = \underline{V_{OUT}}$



STEP 3 Cut-off vs Saturation

Cut-off: $i_e = -I_{EQ} \rightarrow -\frac{V_{OUT}}{\alpha r_c} = -I_{EQ} \rightarrow \text{Max } V_{OUT} = \alpha I_{EQ} r_c$
 $= 0.995 (0.0098A)(543\Omega)$
 $= \underline{5.3V} \leftarrow MP$

Saturation: $V_{ce} = -V_{CEQ} \rightarrow V_{OUT} = -V_{CEQ} \rightarrow \text{Max } V_{OUT} = \underline{-6.22V}$ $MPP = 10.6V_{PP}$

10.2 (+9)

STEP 1 Q-Point


Stiff divider: $10k // 2.2k = 1.8k$
 $\frac{201}{100} \times 1k = 2.01k$

$V_{BB} = 10 \frac{2.2k}{2.2k + 10k} = 1.8V$

$I_{EQ} = \frac{1.8 - 0.7}{1k} = 1.1mA$

$V_C = 10 - 0.995 (1.1mA) (3.6k) = 6.06V$

$V_{CEQ} = 6.06 - 1.1V = 4.96V$

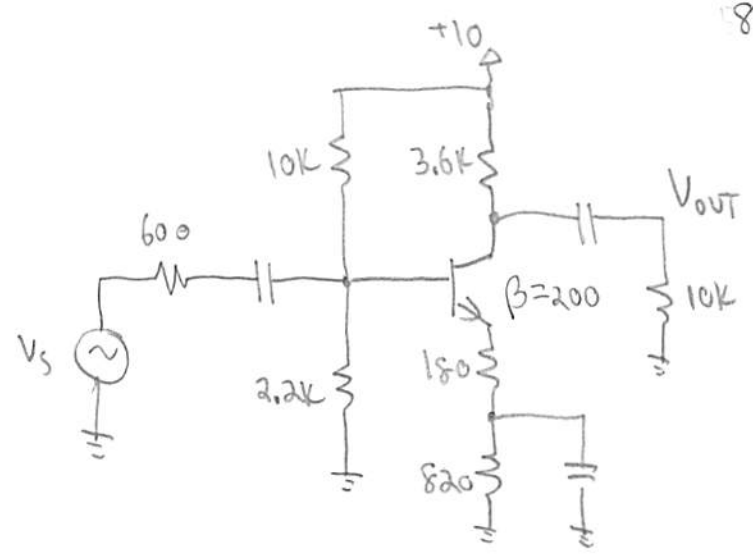


$\alpha = \frac{200}{201} = 0.995$

STEP 2 AC analysis

$r_c = 3.6k // 10k = 2.65k$

$v_{out} = -a_c r_c = -\alpha i_e r_c$

$i_e = -\frac{v_{out}}{\alpha r_c}$

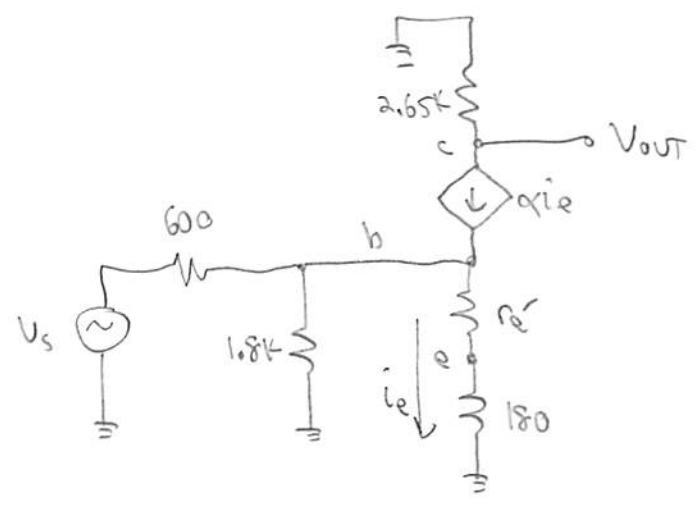

$v_{ce} = v_c - v_e = v_{out} - i_e R_e = v_{out} - \left(-\frac{v_{out}}{\alpha r_c} \right) R_e = v_{out} \left(1 + \frac{R_e}{\alpha r_c} \right)$

STEP 3 Cut-off vs. Saturation

cut-off: $i_e = -I_{EQ} \Rightarrow \frac{-v_{out}}{\alpha r_c} = -I_{EQ} \Rightarrow v_{out} = \alpha I_{EQ} r_c = 0.995 (1.1mA) (2.65k) = 2.9V$


saturation: $v_{ce} = -V_{CEQ} \Rightarrow v_{out} \left(1 + \frac{R_e}{\alpha r_c} \right) = -V_{CEQ}$

$v_{out} = \frac{-4.96V}{1 + \frac{180}{0.995 \times 2.65k}} = -4.64V$

MP = 2.9V

STEP 1 Q-Point

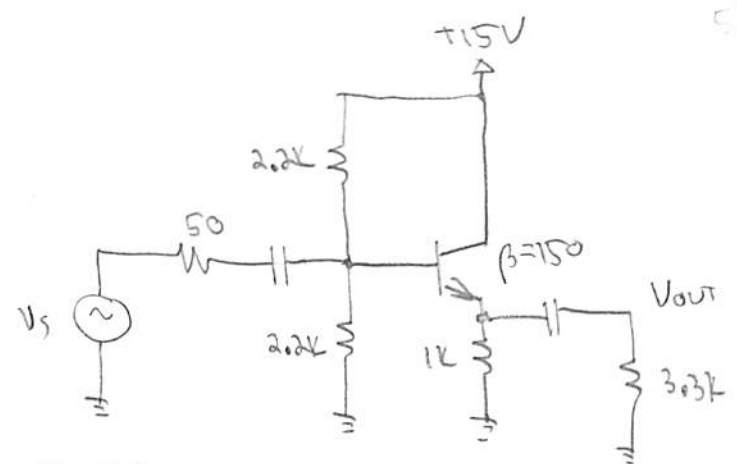- stiff divider? $2.2k // 2.2k = 1.1k$
 $\frac{15}{100} \times 1k = 1.51k$




• $V_{BB} = 15 \times \frac{2.2k}{2.2k + 2.2k} = 7.5V \rightarrow I_{EQ} = \frac{7.5 - 0.7}{1k} = 6.8mA$

• $V_{CEQ} = V_C - V_E = 15 - 6.8V = 8.2V$

STEP 2 AC analysis

$r_e = 1k // 3.3k = 0.77k$

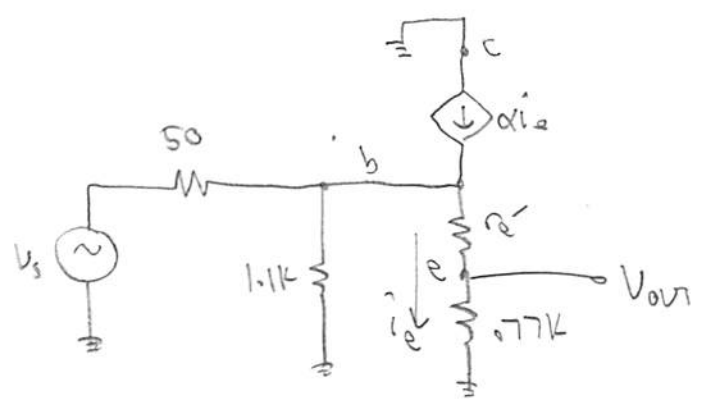

• $V_{out} = i_e r_e \rightarrow i_e = \frac{V_{out}}{r_e}$

• $V_{ce} = V_c - V_e = 0 - V_{out} = -V_{out}$

STEP 3 cut-off vs. saturation

cut-off: $i_e = -I_{EQ} \Rightarrow \frac{V_{out}}{r_e} = -I_{EQ}$

Max $V_{out} = -(6.8mA)(0.77k) = -5.24V$

saturation: $V_{ce} = -V_{CEQ} \Rightarrow -V_{out} = -V_{CEQ}$

Max $V_{out} = 8.2V$

MP = 5.24V