

Solution

Union College
 ECE248 Semiconductor Devices and Circuits
 Spring 2015
 In-Class-Exercise – Common Emitter Voltage Amplifier

Use the circuit in figure 1 below and, $V_T = 26\text{mV}$, to make the following calculations:

- Determine if the bias voltage divider is "stiff".
- Compute the quiescent emitter current I_{EQ} .
- Draw the AC small signal equivalent circuit and make sure to label the value of r_e .
- Compute the voltage gain V_{out}/V_{in} .
- Compute the input impedance R_{in} .
- Compute V_{out} when the AC signal source is $V_s = 8\text{mV}$.

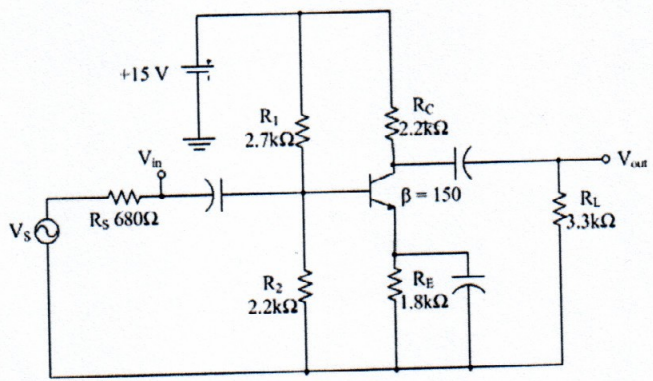



Figure 1 Common Emitter Voltage Amplifier

a. $R_1 || R_2 < \frac{1}{100} (\beta + 1) R_E$
 $2.7k || 2.2k = 1.2k$
 $\frac{151}{100} \cdot 1.8k = 2.7k$] **Yes**

b. $V_{BB} = 15 \left(\frac{2.2k}{2.2k + 2.7k} \right) = 6.735\text{V}$
 $V_E = V_{BB} - 0.7 = 6.035\text{V}$

$I_{EQ} = \frac{6.035\text{V}}{1.8k} = \mathbf{3.35\text{mA}}$

(Extra sheet for work)

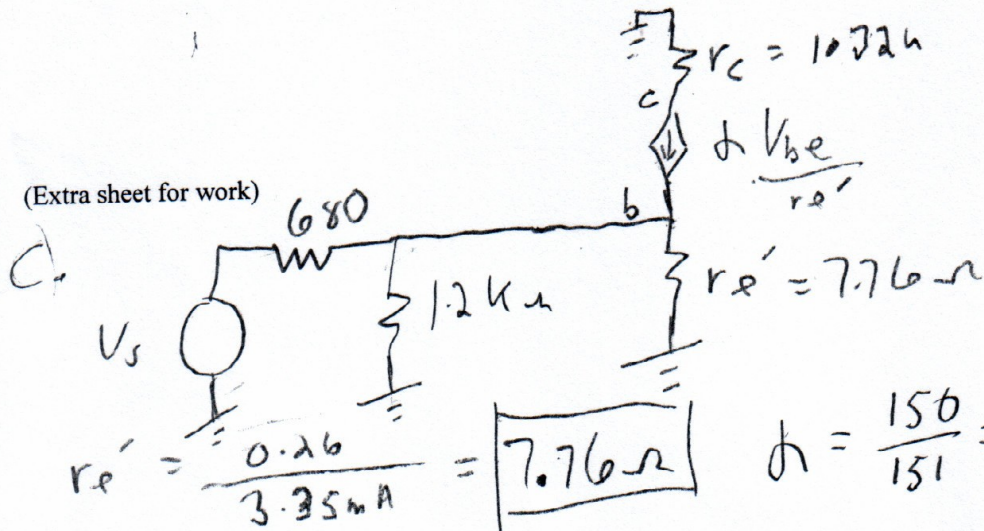

d.
$$\frac{V_{out}}{V_{in}} = -\beta \frac{r_c}{r_{e'}} = -0.993 \frac{1320}{7.76} = -168.9$$

e.
$$R_{in} = R_1 \parallel R_2 \parallel (\beta + 1)r_{e'}$$

$$R_{in} = 1200 \parallel \underbrace{(151)(7.76)}_{1171.8 \Omega} = 592.9 \Omega \approx 593 \Omega$$

f.
$$V_{out} = \left(\frac{V_{out}}{V_s} \right) \cdot V_s = \left(\frac{R_{in}}{R_{in} + R_s} \right) \left(\frac{V_{out}}{V_{in}} \right) \cdot V_s$$

$$\left(\frac{593}{593 + 680} \right) (-168.9) (8 \mu\text{V}) = -629 \text{ mV}$$