

Union College
ECE318/CSC318
Assignment 6
Due Date: March 5th

Note: submit both the code and the simulation output for each problem requiring simulation.

Problem 1 Design an 8-bit dedicated datapath for the following algorithm and write the control words for it. Use only one adder-subtractor unit for all of the addition and subtraction operations. Label clearly all of the control and status signals

```
W=0
X=0
Y=0
INPUT Z
WHILE (Z /= 0) {
    W = W - 2
    IF (Z is an odd number) THEN
        X = X + 2
    ELSE
        Y = Y + 1
    END IF
    Z = Z - 1
}
```

Problem 2 A digital system has an 8-bit input, X, and an 11-bit output, Z, which is computed from X by the equation:

$$Z = 2X + 4(X-1) + 2(X-2)$$

NOTE: (X-1) is the 8-bit value of X of the PREVIOUS CLOCK CYCLE. (X-2) is the 8-bit value of X of TWO CLOCK CYCLES AGO. A new X input is applied at every clock cycle, and after 2 clock cycles, a new Z output is generated every clock cycle.

a. If the X input sequence is the simple incrementing sequence shown below, give the Z output for each of the first 10 clock cycles. We assume the initial values of X-1 and X-2 are 0, and the first two are done for you.

clock cycle	X(binary)	Z(decimal)
1	00000001	$2 + 0 + 0 = 2$
2	00000010	$4 + 4 + 0 = 8$
3	00000011	
4	00000100	
5	00000101	
6	00000110	
7	00000111	
8	00001000	
9	00001001	
10	00001010	


This circuit can be implemented with only a datapath, there is no controller required.

b. Draw a block diagram of the datapath. Clearly label both the ports of the components and the signals between components.

Problem 3. Come up with a control unit for assignment 5 problem problem 7.

Problem 4 The following datapath can implement operations on the 8-bit A register and the four registers R0 - R3 (also 8 bits) and store the results back to the R0-R3 registers. The ALU has output F that is defined based on the select inputs as follows:

S2	S1	S0	ALU OUTPUT F
0	0	0	$F = A + B + C_{in}$
0	0	1	$F = A + B' + C_{in}$
0	1	0	$F = A$
0	1	1	$F = 0$
1	0	0	$F = A \text{ OR } B$
1	0	1	$F = A \text{ AND } B$
1	1	0	$F = A'$
1	1	1	$F = A \text{ XOR } B$

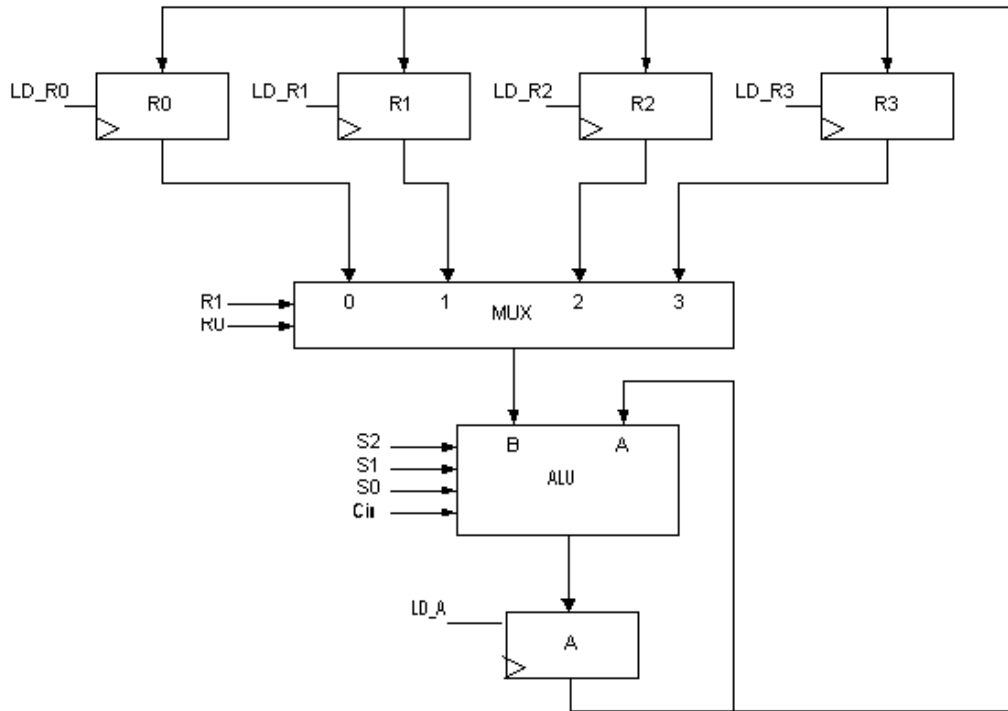

(a) Give the values of the control signals for each state, S0-S4, that would be needed to implement the following sequence of operations on this datapath. State S0 is done for you.

Sequence of operations	Control signals
S0: A ← 0	S2,S1,S0 = 011, LD_A = 1, LD_R0-LD_R3 = 0, R1,R0, Cin = X
S1: A ← A + R3	
S2: R0 ← A	
S3: A ← A XOR R1	
S4: A ← A - R2	

(b) For initial values: R0=F2, R1=CA, R2=03, R3=88, find the final value of A after this sequence of states is executed.

Winter 2013