

Union College

ECE 318

Assignment 2 Solutions

Problem 2.

Code Listing:

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY hw2_1 IS
  PORT(
    A,B,C,D : IN STD_LOGIC;
    X : OUT STD_LOGIC);
END hw2_1;

ARCHITECTURE data_flow OF hw2_1 IS
  SIGNAL AB, CD, ABC: STD_LOGIC; -- internal signals in the circuit
BEGIN
  AB <= A AND B;
  CD <= C OR D;
  ABC <= (NOT C) NOR (NOT AB);
  X <= CD NAND ABC;
END data_flow;
```

Results:

EPM7128SLC84-15

Actual P2P Time	From	To
15.000 ns	C	X
15.000 ns	A	X
15.000 ns	B	X

EPF10K70RC240-4

Actual P2P Time	From	To
19.100 ns	C	X
19.100 ns	B	X
18.800 ns	A	X

EPM7128SLC84-7

Actual P2P Time	From	To
7.500 ns	C	X
7.500 ns	A	X
7.500 ns	B	X

Problem 3.

This is a (clocked) D latch circuit. See the figure below

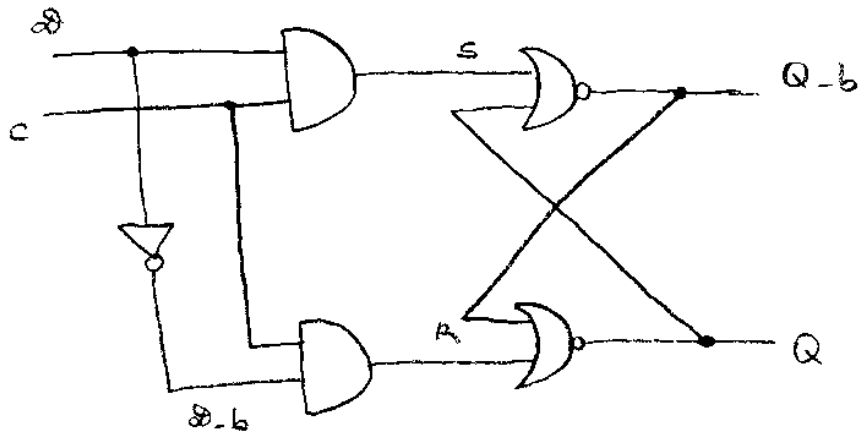


Figure 1. Circuit diagram described by code in Q2

Problem 4.

Code Listing:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY fulladder IS
  PORT(
    Ain: IN STD_LOGIC;
    Bin: IN STD_LOGIC;
    Cin: IN STD_LOGIC;
    Cout: OUT STD_LOGIC;
    Sout: OUT STD_LOGIC);
END fulladder;
```

ARCHITECTURE synthesis OF fulladder IS

```
BEGIN
```

```
Sout <= '1' when (A xor B xor Cin) = '1' else  
    '0';
```

```
Cout <= '1' when ((A and B) or (A and Cin) or (B and Cin)) = '1' else  
    '0';
```

```
END synthesis;
```

Simulation:

The simulation results are shown in figure 2:

 


Figure 2. Simulation results for Q3

Problem 5.

Code Listing:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY decoder IS
```

```
    PORT(  
        S: IN STD_LOGIC_VECTOR(1 downto 0);
```

```
        en: IN STD_LOGIC;
```

```
        Dout: OUT STD_LOGIC_VECTOR(3 downto 0));
```

```
END decoder;
```

ARCHITECTURE when_else OF decoder IS

BEGIN

```
Dout <= "1111" when en = '0' else
      "0111" when S = "11" else
      "1011" when S = "10" else
      "1101" when S = "01" else
      "1110" when S = "00" else
      "XXXX";
```

END when_else;

Simulation:

The simulation results are shown in Figure 3.

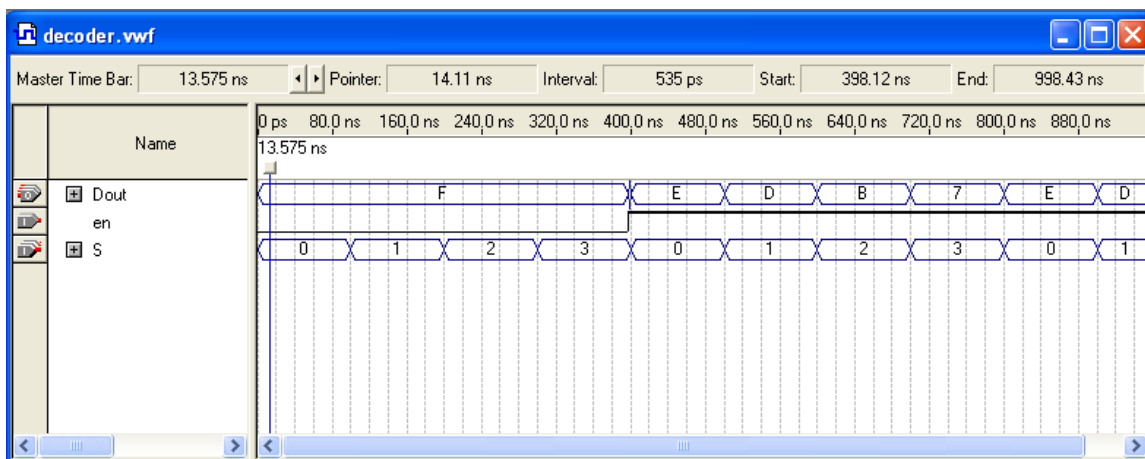


Figure 3. Simulation results for Q4.

Problem 6.

Code Listing:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY decoder2 IS
  PORT(
    S: IN STD_LOGIC_VECTOR(1 downto 0);
    en: IN STD_LOGIC;
    Dout: OUT STD_LOGIC_VECTOR(3 downto 0));
END decoder2;
```

```

ARCHITECTURE with_select OF decoder3 IS
    SIGNAL SEL: STD_LOGIC_VECTOR(2 downto 0);
BEGIN
    SEL(0) <= en;
    SEL (2 downto 1) <= S;
    WITH SEL SELECT
    Dout <=      "1111" when "000" | "010" | "100" | "110",
                "0111" when "111",
                "1011" when "101",
                "1101" when "011",
                "1110" when "001",
                "XXXX" when others;

END with_select;

```

Simulation:

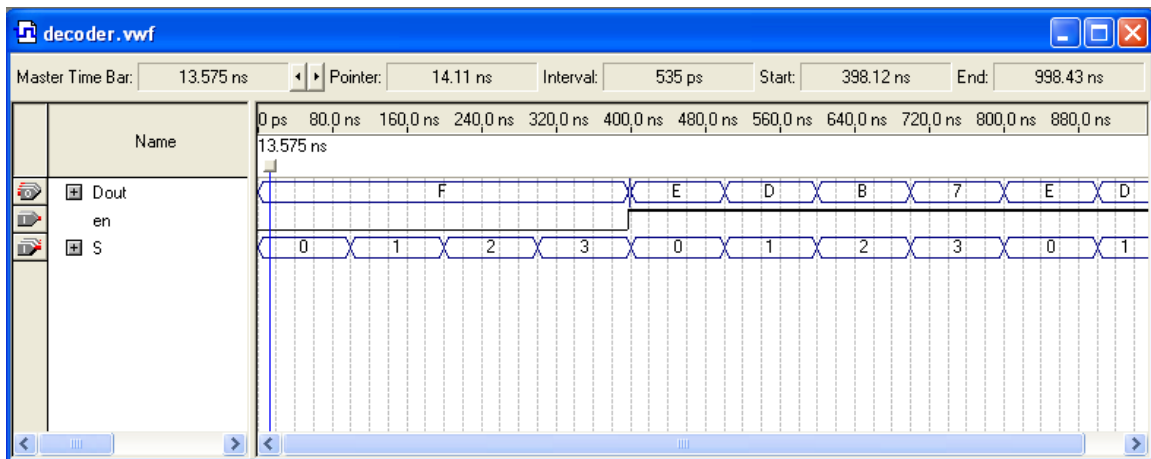


Figure 4. Simulation results for problem 5

Winter 2013