

Union College
ECE363 Fall 2017
Lecture 1 Notes

Professors Buma, Hedrick

Note: These notes are primarily from Professor Buma and do not include some of the Hedrick class notes.

Topics: Introduction, Transistor switch, Op-Amp basics

Read in the Textbook:

1. Transistor switch: sections 6-13, 6-14, 6-8
2. Op-Amp basics: all of chapter 16 but pay particular attention to sections 16-1, 16-3, 16-4


0. Intro

A. The Big Picture


- Interacting with the real world requires us to measure, process, and transmit signals.

⇒ Electronic devices play a very important role!

REAL WORLD

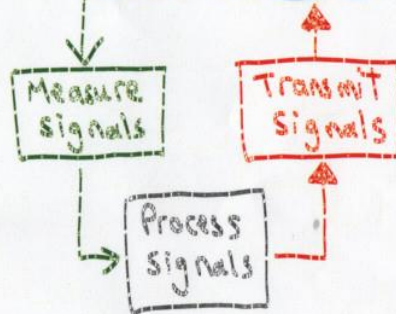

Example:

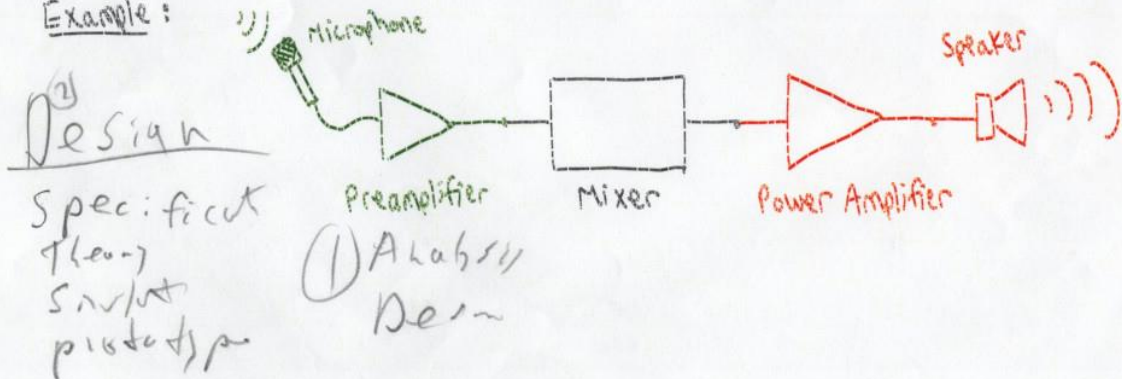

B. Analysis vs. Design

- ECE 248: Analyze circuits with diodes and transistors.

★ ECE 363: Design circuits with op amps and transistors!

↳ "Accuracy"

[e.g. Stable voltage gain]


op amps typically output $< 25\text{ mA}$

↳ "Heavy Lifting"


[e.g. Delivers load current]

Small transistor (100 mA)
Power transistor ($\sim 5\text{ A}$)

Example Emitter Follower

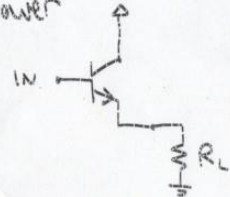

Example Audio Amplifier

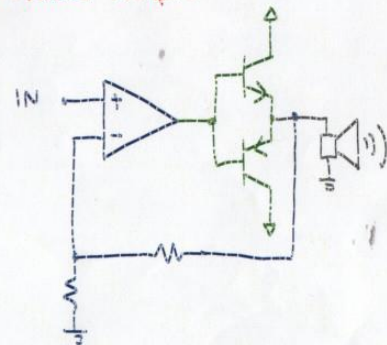


Can we design with out ICs?
1. Transistor Switch

Let's start with an application...
 Optical communication link!


usually a photodiode + op amp



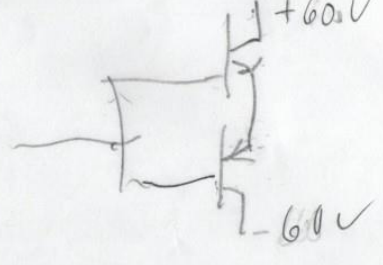simplest approach
 Example HV diode is LED + transistor switch + 60V




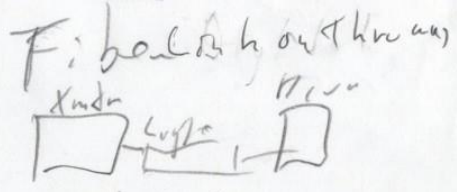NOTE: This example is a digital comm link.




Start with LEDs

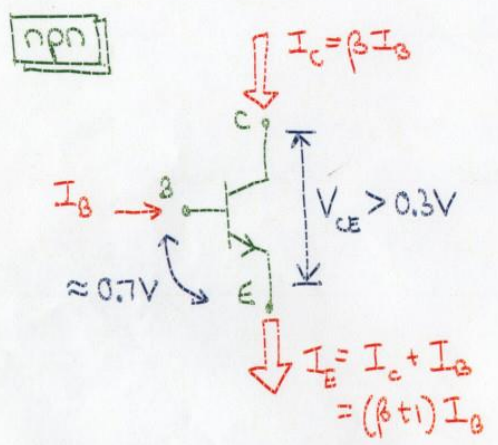A. Quick BJT review
ACTIVE MODE ← Good for amplifiers



SATURATION MODE ← Good for switches

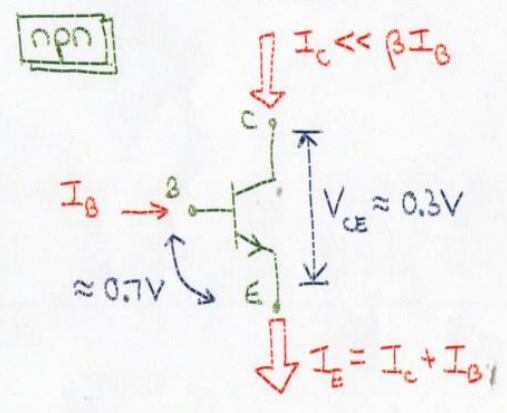


B. BJT switch Analysis

- Example: 12V, 0.12A lamp ($R_L = 100\Omega$)

$$V_{BE,sat} = 0.7V, V_{CE,sat} = 0.3V$$

① 0V input: $V_B = 0V \rightarrow I_B = 0$
 \Rightarrow Transistor is cut-off

Switch is OFF

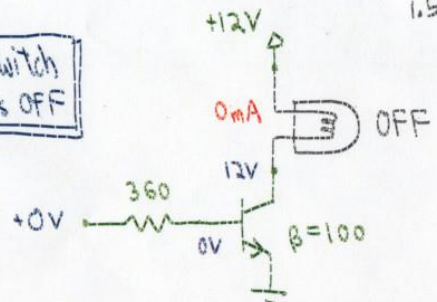


② 5V input $\rightarrow I_B = \frac{5 - 0.7}{360\Omega} = 0.012A$

$$I_C = \frac{V_{CC} - V_C}{R_L} = \frac{12 - 0.3}{100\Omega} = 0.117A$$

• $\frac{I_C}{I_B} = 9.75 \ll 100 \Rightarrow$ Transistor is saturated

Switch is ON

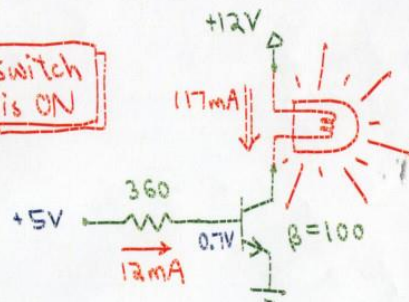

C. BJT switch design


Rule #1 Know your load

Rule #2 When BJT is ON,
 make sure it is saturated ($V_{CE} = V_{CE,sat}$)

Rule #3 Use $I_C \sim 0.1\beta I_B$
 $\Rightarrow I_B = \frac{I_C}{0.1\beta}$

\rightarrow called "hard saturation"

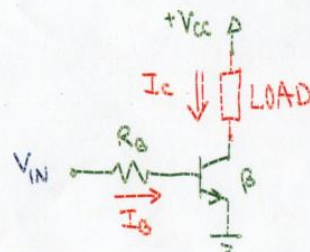\hookrightarrow Ensures that variations in β
 do not affect I_C .



$\sim 0.3V$ for small signal transistor
 $\sim 1V$ for power transistor

• Design example: Driver for LED ($V_F = 2V @ 10mA$)


Rule 1 Load properties

• LED has 2V drop when $I_C = 10mA$

Rule 2 Saturated BJT

• KVL: $5 - V_F - I_C R - V_{CE} = 0 \Rightarrow R = \frac{5 - 2.2}{10mA} = \underline{280\Omega}$

From datasheet, worst-case value is 0.2V

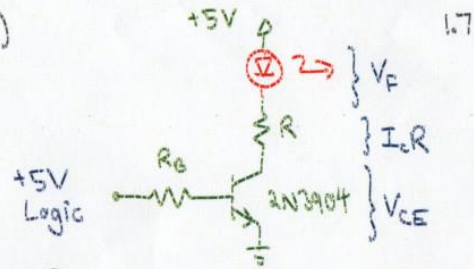

Closest 5% resistors are 270Ω or 300Ω


$I_C = \frac{5 - 2.2}{270} = 10.4mA$

$\frac{5 - 2.2}{300} = 9.3mA$

Choose $R = 270\Omega$

Min $\beta = 100$

Max value = 0.95V

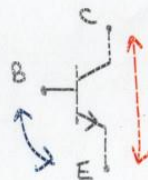

Max value = 0.2V

When transistor is saturated @ $I_C = 10mA$!

(1.8)

From 2N3904 datasheet

		TEST CONDITIONS	MIN	MAX
ON CHARACTERISTICS*				
h_{FE} ↑ Same as β	DC Current Gain	$I_C = 0.1mA, V_{CE} = 1.0V$ $I_C = 1.0mA, V_{CE} = 1.0V$ <u>$I_C = 10mA, V_{CE} = 1.0V$</u> $I_C = 50mA, V_{CE} = 1.0V$ $I_C = 100mA, V_{CE} = 1.0V$	40 70 <u>100</u> 60 30	300
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	<u>$I_C = 10mA, I_B = 1.0mA$</u> $I_C = 50mA, I_B = 5.0mA$		<u>0.2 V</u> 0.3 V
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	<u>$I_C = 10mA, I_B = 1.0mA$</u> $I_C = 50mA, I_B = 5.0mA$	0.65	<u>0.85 V</u> 0.95 V

Show data sheet V_{DES}

Rule 3 Base current drive

$I_b = \frac{1}{\beta} I_c = \frac{1}{10} I_c \implies I_b = \frac{10.4 \text{ mA}}{10} = \underline{1.04 \text{ mA}}$
 $R_b = \frac{V_{in} - V_{be}}{I_b} \implies R_b = \frac{5 - 0.85}{1.04 \text{ mA}} = 3.99 \text{ K}$

Closest 5% resistors are **3.9K** and **4.3K**

$I_b = \frac{5 - 0.85}{3.9 \text{ K}} = 1.06 \text{ mA}$
 (Too big is OK)

$\frac{5 - 0.85}{4.3 \text{ K}} = 0.97 \text{ mA}$
 (Too small :))


Choose $R_b = 3.9 \text{ K}$

2. Op Amp Basics

• How to make a photoreceiver?

METHOD 1


Photocell

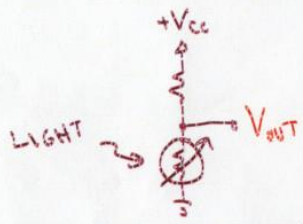

Pro: Cheap, simple
 Con: Wide variation in performance
 Slow

METHOD 2

Phototransistor

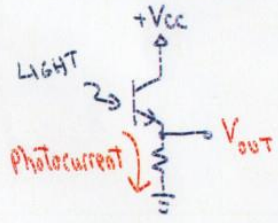


Pro: Large current output
 Con: Somewhat noisy
 Medium speed

choose this

METHOD 3

Photo diode

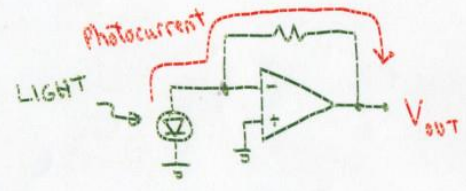


Pro: Low noise
 High speed
 Con: Low current output
 Boost signal w/op amp!

(1.10)

Most op amp circuits can be understood by using 2 Golden Rules:

① $V_{IN(-)} = V_{IN(+)}$ ← called a "virtual short"

② The two inputs draw no current.

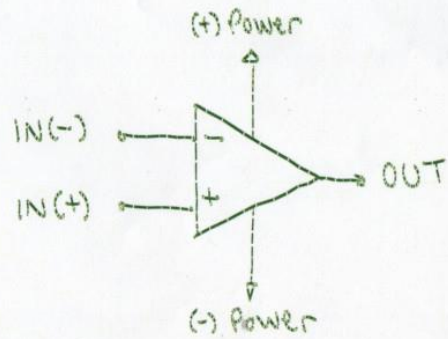

1.11

NOTE: The Golden Rules assume an ideal op amp used with negative feedback!

• Non-inverting Amplifier


① From Rule 2, $V_+ = V_s$

② From Rule 2, $V_- = V_o \frac{R_1}{R_1 + R_2}$


→ From Rule 1, $V_- = V_+$

$$V_o \frac{R_1}{R_1 + R_2} = V_s \Rightarrow \boxed{\frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}}$$

EX: $R_1 = 1K$
 $R_2 = 100K$ } $G = 101$

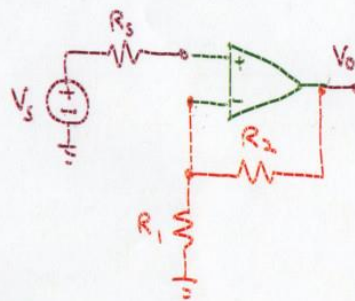

1.12

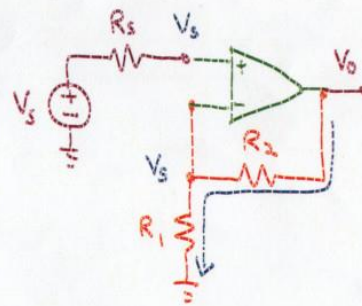

• Inverting Amplifier



1.13

Rule 1 $V_- = V_+ = 0$

Rule 2 $\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$

$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$

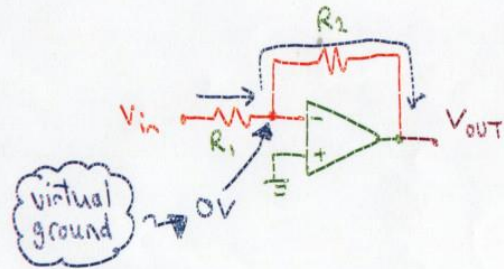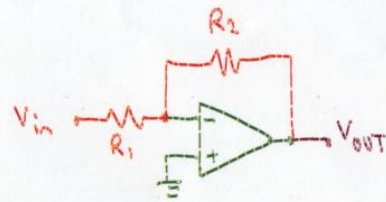EX: $R_1 = 1K$
 $R_2 = 100K$ } $G = \frac{V_{out}}{V_{in}} = -100$



• Transimpedance Amplifier ← Also called "current-to-voltage converter"

1.14

Rule 1 Since $V_+ = 0$
 $\Rightarrow V_- = 0$ (virtual ground)

Rule 2 $i_{in} = \frac{0 - V_{out}}{R_F}$

$\Rightarrow V_{out} = -i_{in} R_F$

