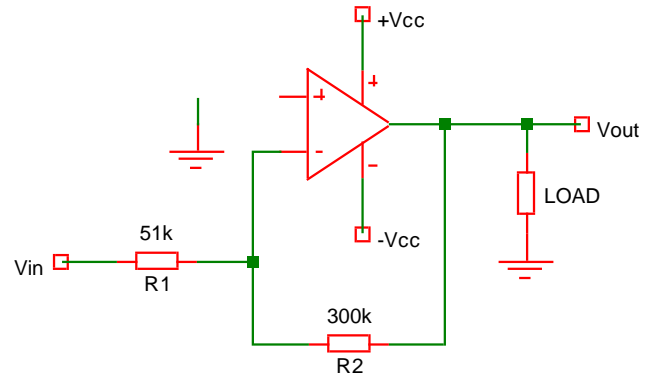


Problem #1: Real Op Amp Analysis

Consider an inverting amplifier using a LM318 op amp (see attachment and use values for 25°C). The (+) input is directly wired to ground.

- (a) Suppose $V_{IN} = 0$ and no trimming network. Given the worst-case values for $I_{IN(bias)}$, $I_{IN(offset)}$, and $V_{in(offset)}$, compute the output voltage offset due to each parameter.
- (b) Is the main source of error due to input bias current, input offset current, or input offset voltage?
- (c) What is the worst-case output voltage offset?



a) From data sheet $I_{IN(bias)} = 500 \text{ nA}$, $I_{IN(offset)} = 200 \text{ nA}$, $V_{in(offset)} = 10 \text{ mV}$

$R_{TH(-)} = 51 \text{ k} \parallel 300 \text{ k} = 43.6 \text{ k}\Omega$ $G = -\frac{300 \text{ k}}{51 \text{ k}} = -5.88$

$R_{TH(+)} = 0 \Omega$

$I_{IN(bias)} \rightarrow \Delta V_{in} = (500 \text{ nA})(43.6 \text{ k} - 0) = 0.0218 \text{ V}$

$\Delta V_{out} \approx (5.88)(0.0218 \text{ V}) = 0.128 \text{ V} = \boxed{128 \text{ mV}}$

$I_{IN(offset)} \rightarrow \Delta V_{IN} = (200 \text{ nA})\left(\frac{43.6 \text{ k} + 0}{2}\right) = 0.00436 \text{ V}$

$\Delta V_{out} \approx (5.88)(4.36 \text{ mV}) = \boxed{25.6 \text{ mV}}$

$V_{in(offset)} \rightarrow \Delta V_{in} = 10 \text{ mV}$

$\Delta V_{out} = (5.88)(10 \text{ mV}) = \boxed{58.8 \text{ mV}}$



b) Main source of error is input bias current.

c) Worst-case output offset = $128 + 25.6 + 58.8$
 $= \boxed{212.4 \text{ mV}}$

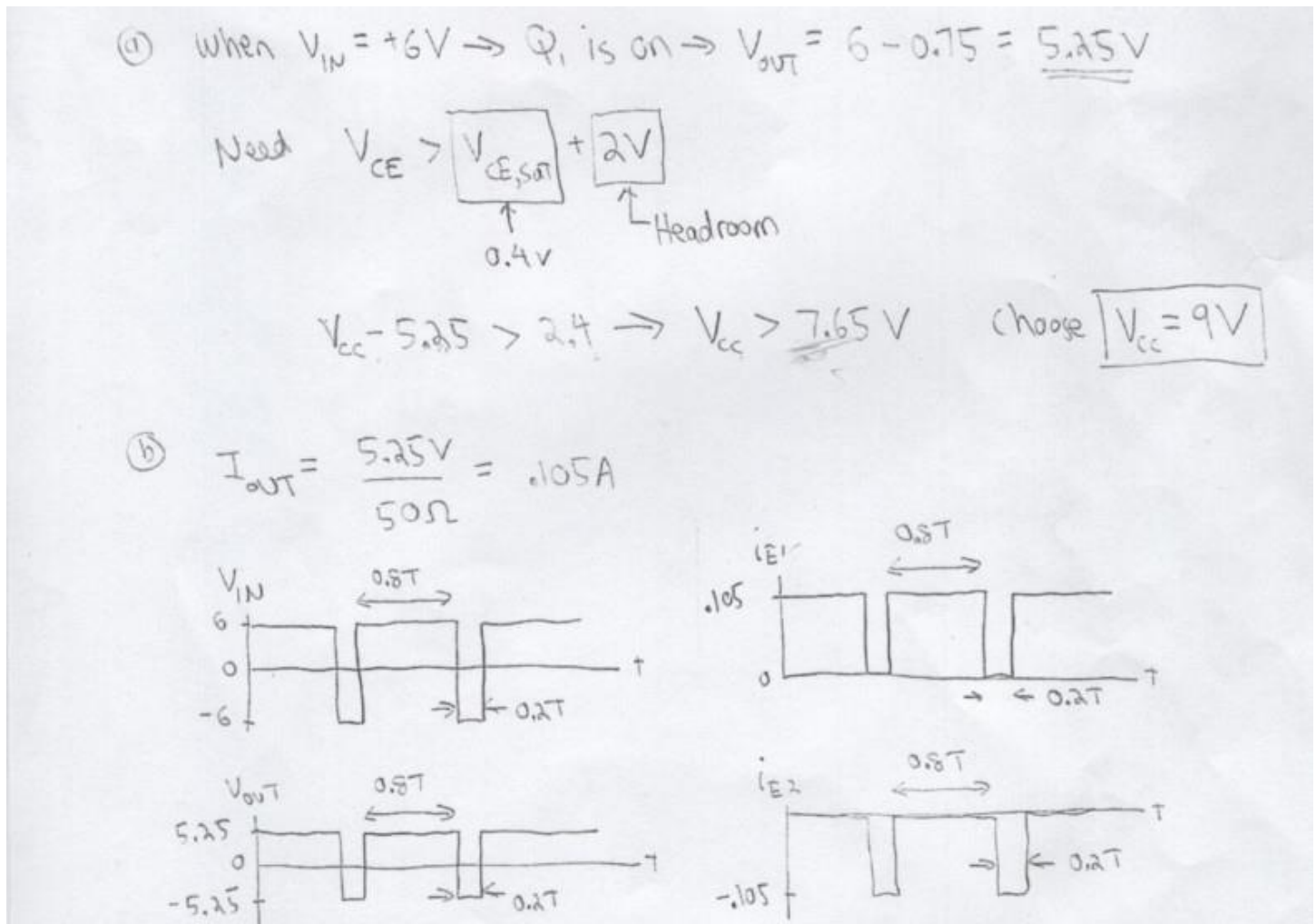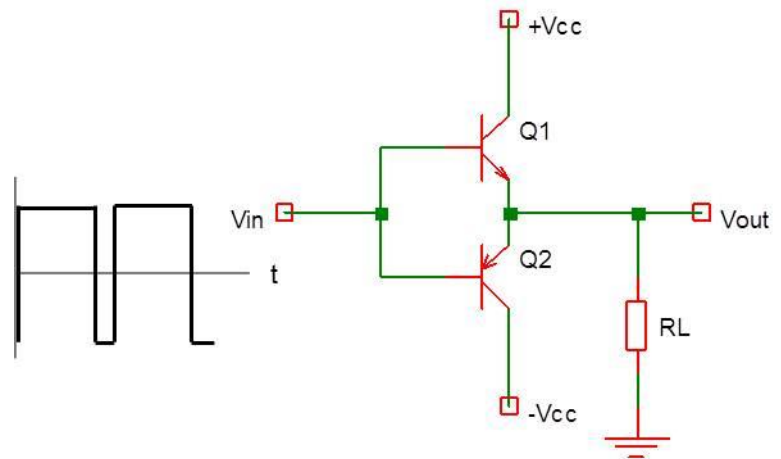Problem #2: Current Booster Analysis

Suppose V_{IN} is a 80% duty cycle square wave that alternates between +6V (HIGH) and -6V (LOW). The load is $R_L = 50 \text{ ohm}$. Both transistors have $V_{BE,ON} = 0.75V$, $V_{CE,SAT} = 0.4V$, and $\beta = 80$.

- You must choose between $V_{CC} = 6, 9, \text{ or } 12V$. Which is the best choice?
- Sketch V_{IN} , V_{OUT} , i_{E1} (Q1 emitter current), and i_{E2} (Q2 emitter current). Label important features.
- Given your choice of V_{CC} , estimate the power dissipation in Q1 and Q2.



© Q_1 : When on, $i_E V_{CE} = (.105A)(9-5.25) = 0.394 W \leftarrow 80\% \text{ of time}$

$$\langle P_1 \rangle = \frac{1}{T} \int_0^{0.8T} (0.394 W) dt + \frac{1}{T} \int_{0.8T}^T 0 dt$$

~~$\rightarrow 0$~~

$$= 0.394 W \times 0.8$$


$$= 0.315 W = \boxed{315 \text{ mW}}$$

Q_2 : When on, $i_E V_{CE} = 0.394 W \leftarrow 20\% \text{ of time}$

$$\langle P_2 \rangle = 0.394 \times 0.2 = .0788 W = \boxed{78.8 \text{ mW}}$$

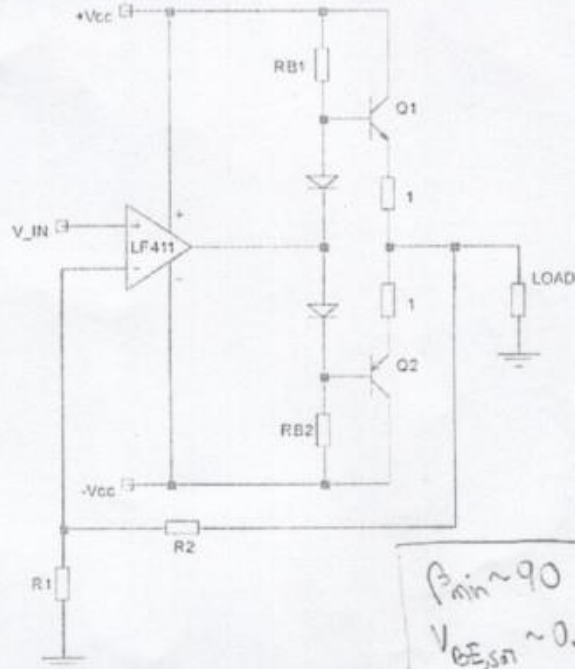Problem #3: Class AB Design

Design a non-inverting voltage amplifier to drive up to 150 mW (or slightly higher) into a 32 ohm load. The input signal is a sine wave with a maximum amplitude of 1V_{pp}. The suggested schematic is shown in the figure, where an LF411 op amp is used. Q1 is a 2N4401, and Q2 is a 2N4403.



- (a) V_{CC} must be 4.5, 6, 9, or 12V. Choose one and explain why.
- (b) Choose RB1 and RB2. Pick standard 5% values.
- (c) Show that the op amp can provide the required output voltage and current.
- (d) Choose R1 and R2. Remember that R1 should be more than a few kohm and R2 is typically less than 1 Mohm. Pick standard 5% values.
- (e) Do your transistors need heat sinks? Use T_A = 60°C for your power rating calculations.

$\beta_{min} \sim 90$
 $V_{BE,sat} \sim 0.95V$
 $V_{CE,sat} \sim 0.4V$

Ⓐ Max output? $0.150W = \frac{V_{MAX}^2}{2 \times 32\Omega} \Rightarrow V_{MAX} = \pm 3.1V$
 For sine wave
 $I_{MAX} = \frac{3.1V}{32\Omega} = 0.0968A$

Max $V_E = (0.0968A)(1 + 32\Omega) = 3.2V$

Need $V_{CC} - V_E > V_{CE,sat} + 2 \Rightarrow V_{CC} > 5.6V$
 choose $V_{CC} = 6V$

Ⓑ $\frac{6V - 3.2 + 0.95 = 4.15V}{R_B} > 1mA + \frac{96.8mA}{90+1}$
 $\frac{6 - 4.15V}{R_B} > 1mA + 1.064mA \Rightarrow R_B < 0.896k$ choose $R_{B1} = R_{B2} = 820\Omega$

$$\textcircled{c} \text{ Max } V_{op,amp} = V_{o1,max} - 0.7 = 4.15 - 0.7 = \underline{3.45V}$$

$$\text{Max } I_{op,amp} = \frac{3.45V}{R_{in,AB}}$$

$$R_{in,AB} = \underbrace{(820 \parallel 820)}_{410\Omega} \parallel \underbrace{(90+1) \left(\frac{0.026V}{0.0968A} + 1 + 32 \right)}_{3027.4\Omega} = \underline{361.1\Omega}$$

$$\text{Max } I_{op,amp} = \frac{3.45V}{361.1\Omega} = 0.00955A = \underline{9.6mA}$$



According to LF411 datasheet, $V_{cc} = 15V$, $V_o = 13.5V @ 13.5mA$ ($R_L = 1K$)
 1.5V difference

$V_{cc} = 6V$, $V_o = \underline{4.5V @ 13.5mA}$

YES, op amp is OK

$$\textcircled{d} \text{ Desired } G = \frac{3.1V}{0.5V} = 6.2 = 1 + \frac{R_2}{R_1} \rightarrow \frac{R_2}{R_1} = 5.2$$

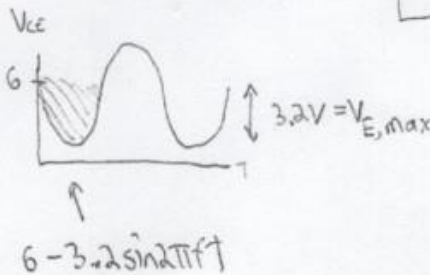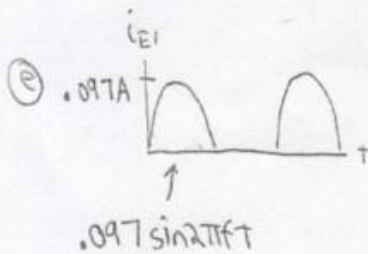Choose $\left. \begin{matrix} R_2 = 68K \\ R_1 = 13K \end{matrix} \right\} G = 6.23$



$$\langle P \rangle = \frac{1}{T} \int_0^{T/2} 0.582 \sin 2\pi f t dt - \frac{1}{T} \int_0^{T/2} 0.31 \sin^2 2\pi f t dt = 0.582 \times \frac{1}{\pi} - 0.31 \times \frac{1}{4} = \underline{0.108W}$$

$$2\langle P \rangle = \underline{0.216W}$$

$$P_{MAX} = 625mW - 5 \frac{mW}{^\circ C} \times (60-25) = \underline{450mW} \quad \left. \begin{matrix} 216mW < 450mW \\ \checkmark \end{matrix} \right\}$$

No heat sink needed