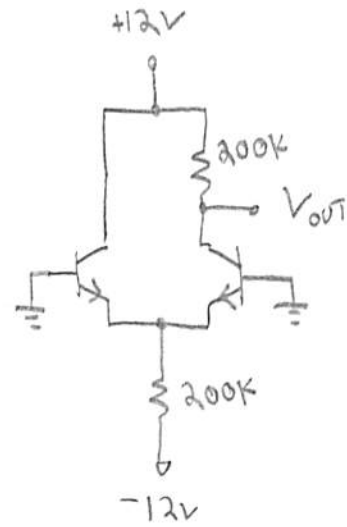


1
+10

a) Tail current $I_T = \frac{12 - 0.7}{200k}$

$I_T = 0.0565 \text{ mA}$



$\beta = 100$
 $\alpha = \frac{100}{101} = 0.99$

b) $r_e' = \frac{0.026}{\frac{1}{2}(0.0565 \text{ mA})} = 0.92 \text{ k}$

c) $V_{CQ} = V_{CC} - \alpha \frac{1}{2} I_T R_C = 12 - 0.99 \frac{1}{2} (0.0565 \text{ mA})(200k)$
 $= 6.4 \text{ V}$


2
+10

a) $A_d = \frac{\alpha R_C}{2r_e'}$
Need I_T !

$I_T = \frac{V_{EE} - V_{BE}}{R_E} = \frac{12 - 0.7}{56k} = 0.202 \text{ mA}$

$r_e' = \frac{0.026 \text{ V}}{\frac{1}{2}(0.202 \text{ mA})} = 0.257 \text{ k}$

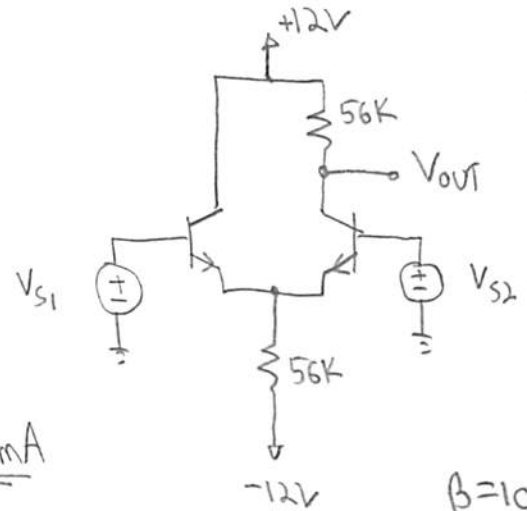$\rightarrow A_d = \frac{0.99 \cdot 56k}{2(0.257k)} = 107.9$



$\beta = 100$
 $\alpha = \frac{100}{101} = 0.99$

b) $V_{CQ} = 12 - 0.99 \frac{1}{2} (0.202 \text{ mA})(56k) = 6.4 \text{ V}$

$\Delta V_{out} = A_d \Delta V_{in} = 107.9 (10 \text{ mV} - -10 \text{ mV}) = 2.16 \text{ V}$

$\Rightarrow V_{out} = 6.4 + 2.16 = 8.56 \text{ V}$

© $\text{Max } (+) \Delta V_{out} = V_{cc} - V_{ceq} = 12 - 6.4 = \underline{5.6V}$

$\text{Max } (-) \Delta V_{out} = V_{ceq} - (V_E + V_{CE,sat}) = 6.4 - (-0.7 + 0.3) = \underline{6.8V}$

This is the limiting factor

$\text{Max } \Delta V_{in} = \frac{5.6V}{107.9} = 0.052V = \boxed{52mV}$


(3)
(10)

a) $A_d = \frac{\alpha R_c}{2r_e'}$ ← Need I_T !

$I_T = \frac{12 - 0.7}{56K} = \underline{0.202mA}$

$r_e' = \frac{0.026}{\frac{1}{2}(0.202mA)} = \underline{0.257K}$

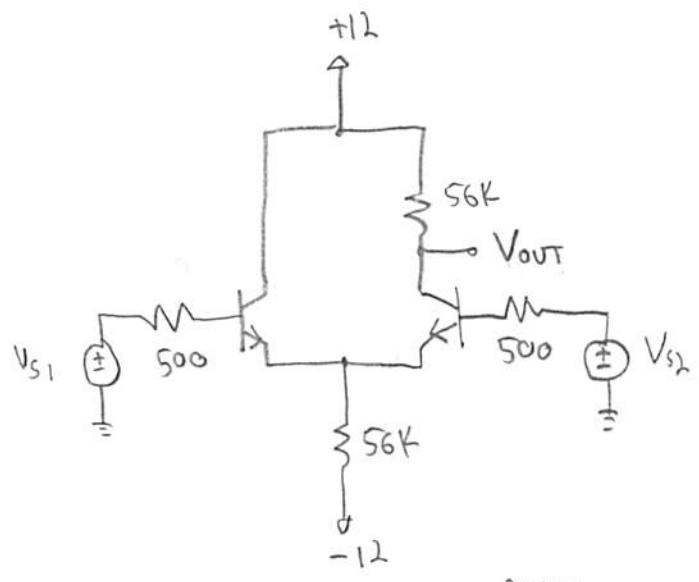$\Rightarrow A_d = \frac{0.99 \times 56K}{2(0.257K)} = \boxed{107.9}$



$\beta = 100$
 $\alpha = \frac{100}{101} = 0.99$

b) $R_{in} = 2(\beta + 1)r_e' = 2(100 + 1)(0.257K) = \boxed{51.9K}$

c) $\Delta V_{in} = \Delta V_s \frac{R_{in}}{R_{in} + R_s} \Rightarrow \frac{\Delta V_{in}}{\Delta V_s} = \frac{51.9K}{51.9K + 5K + 5K} = \boxed{0.98}$

d) $\Delta V_{out} = \underbrace{\frac{\Delta V_{out}}{\Delta V_{in}}}_{A_d} \times \frac{\Delta V_{in}}{\Delta V_s} \Delta V_s = 107.9 \times 0.98 \times (5 - -5mV) = \boxed{1.057V}$

④ 110


a) $R_{in} \geq 50K$

$$2(\beta+1)r_e' \geq 50K$$

$$r_e' \geq \frac{50K}{2(101)} = \underline{0.248K}$$

$$\frac{.026V}{\frac{1}{2} I_T} \geq .248K$$

$$\rightarrow I_T \leq \boxed{0.21mA}$$

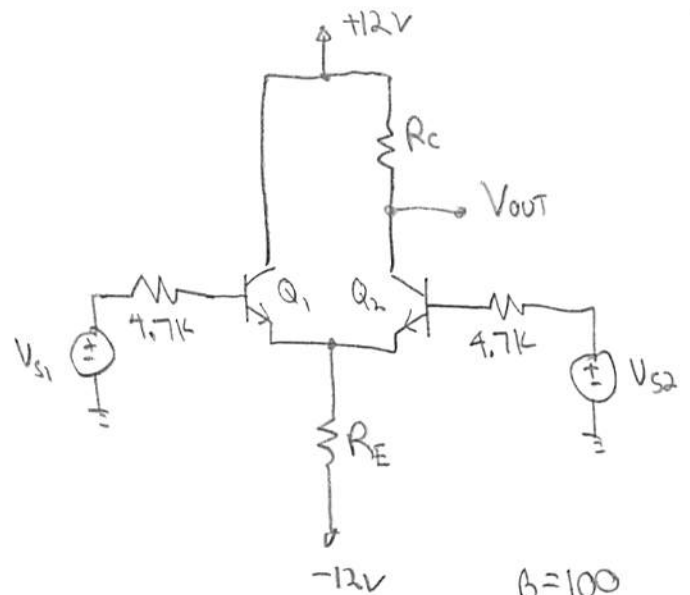

$$\beta = 100$$

$$\alpha = \frac{100}{101} = 0.99$$

b) $I_T = .21mA \geq \frac{12 - 0.7}{R_E} \Rightarrow R_E \geq \frac{12 - 0.7}{.21mA} = 53.8K$

choose $\boxed{R_E = 56K}$

c) $I_T = \frac{12 - 0.7}{56K} = \boxed{0.202mA}$

$$r_e' = \frac{.026}{\frac{1}{2} (.202mA)} = \underline{0.257K} \Rightarrow R_{in} = 2(101)(.257K) = \boxed{51.9K}$$

satisfies
design
requirement

d) $A_v = \frac{\alpha R_C}{2r_e'} \geq 100$

$$R_C \geq \frac{100 \times 2 \times .257K}{.99} = 51.9K$$

choose $\boxed{R_C = 56K}$

e) $A_d = \frac{.99 (56K)}{2 (.257K)} = \boxed{107.9}$ $V_{CQ} = 12 - 0.99 \frac{1}{2} (.202mA)(56K) = \boxed{6.4V}$

f) $\frac{V_{OUT}}{V_S} = \boxed{\frac{V_{OUT}}{V_{IN}}} \frac{V_{IN}}{V_S} = A_d \frac{R_{IN}}{R_{IN} + R_S} = 107.9 \frac{51.9K}{51.9K + 9.4K} = \boxed{91.4}$


5

10

a) $R_{IN} = 2(\beta+1)r_{e'} \geq 20K$
 $r_{e'} \geq \frac{20K}{2(40+1)} = \underline{0.244K}$

$\frac{.026}{\frac{1}{2} I_T} \geq .244K$

$I_T \leq \boxed{0.213mA}$

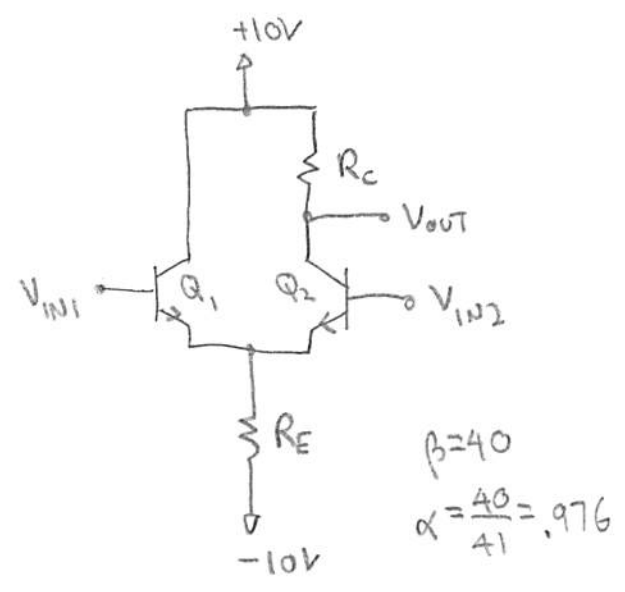

b) $I_T = \frac{10 - 0.72}{R_E} < .213mA$

$R_E > 43.6K$ Choose $R_E = \boxed{47K}$

c) Actual $I_T = \frac{10 - 0.72}{47K} = \boxed{0.197mA}$

$r_{e'} = \frac{.026}{\frac{1}{2} (.197mA)} = 0.264K$

$R_{IN} = 2(41)(.264K) = \boxed{21.65K}$

d) $A_d = \frac{\alpha R_C}{2r_{e'}} \geq 100 \rightarrow R_C \geq \frac{100 \times 2 \times .264K}{0.976} = 54.1K$ Choose $R_C = \boxed{56K}$

e) Actual $A_d = \frac{.976 \cdot 56K}{2 \cdot .264K} = \boxed{103.5}$ $V_{CQ} = 10 - .976 \frac{1}{2} (.197mA)(56K) = \boxed{4.6V}$

6
+10

a) $I_T = \frac{9-0,7}{51K} = \underline{0,163 \text{ mA}}$


$r_e' = \frac{0,026}{\frac{1}{2} (0,163 \text{ mA})} = 0,319K$

$R_{in} = 2(100+1)(0,319K) = \underline{64,44K}$

b) $A_d = \frac{\alpha R_c}{2r_e'} = \frac{0,99 \times 51K}{2 \times 0,319K} = \underline{79,1}$

c) $A_{cm} = \frac{\alpha R_c}{2R_E} = \frac{0,99 \times 51K}{2 \times 51K} = \underline{0,495}$

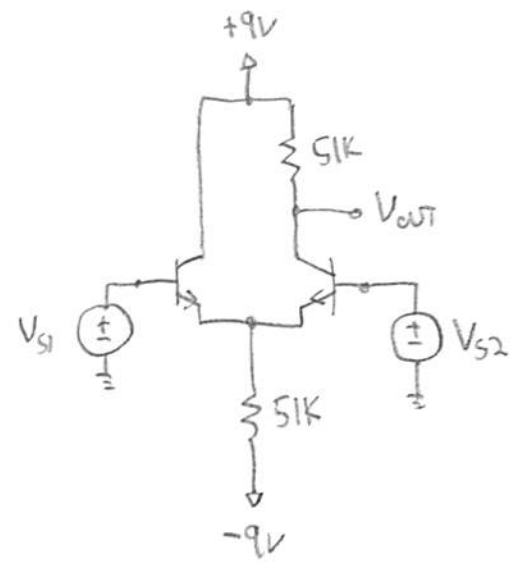d) $CMRR = 20 \log_{10} \frac{79,1}{0,495} = \underline{44,1 \text{ dB}}$



7
+10

Problem 4: $\alpha = 0,99$
 $r_e' = 0,257K$
 $R_c = R_E = 56K$
 $A_d = 107,9$

$A_{cm} = \frac{0,99 \times 56K}{2 \times 56K} = 0,495$

$\Rightarrow CMRR = 20 \log_{10} \frac{107,9}{0,495} = \underline{46,8 \text{ dB}}$

Problem 5: $\alpha = 0,976$
 $r_e' = 0,264K$
 $R_c = 56K, R_E = 47K$
 $A_d = 103,5$

$A_{cm} = \frac{0,976 \times 56K}{2 \times 47K} = 0,58$

$\Rightarrow CMRR = 20 \log_{10} \frac{103,5}{0,58} = \underline{45 \text{ dB}}$

(8)
(10)

(a) $I_2 = I_s - I_B$


Assuming zener is OK,

$V' = -9 + 6.2 = -2.8V$

$I_s = \frac{0 - (-2.8)}{220} = 0.0127A = 12.7mA$

$I_B = \frac{1}{100+1} \cdot \frac{6.2 - 0.7}{27K} = 0.002mA \leftarrow \text{negligible}$

$\rightarrow I_2 = 12.7mA$

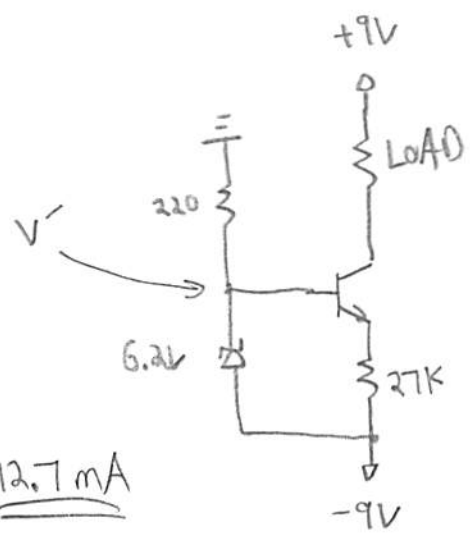

(b) $I_L = \alpha I_E = 0.99 \times \frac{6.2 - 0.7}{27K} = 0.202mA$

(c) $R_{out} = r_o \left[1 + \beta \frac{R_2}{R_2 + (\beta+1)r_e} \right]$

$r_o = \frac{120V}{0.202mA} = 594.1K$

$r_e' = \frac{0.026}{0.204mA} = 0.1275K$

$R_{out} = 594.1K \left(1 + 100 \frac{27K}{27K + 101(0.1275K)} \right) = 4.08 \times 10^4 K = 40.8M\Omega$


(9)
(10)

Problem 4: $I_T = 0.202mA$

$I_T = \alpha I_E = 0.99 \frac{5.1 - 0.7}{R} = 0.202mA$

$R = 21.6K$

Choose $R = 22K$

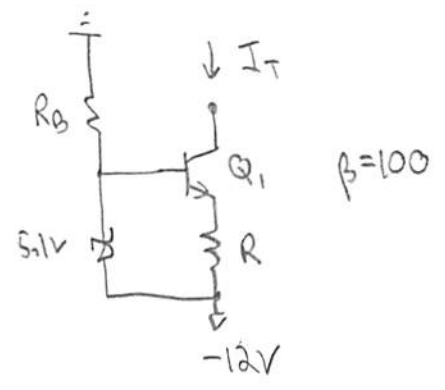

Actual $I_T = 0.99 \frac{5.1 - 0.7}{22k} = \underline{0.198 \text{ mA}}$

↑
0.2 mA

want: $I_2 = I_s - I_B > 10 \text{ mA}$

$$\frac{12 - 5.1}{R_B} - \frac{1}{101} (0.2 \text{ mA}) > 10 \text{ mA}$$

$$R_B < \frac{6.9 \text{ V}}{10.002 \text{ mA}} = 0.69 \text{ k} \quad \text{choose } \boxed{R_B = 680 \Omega}$$

$$\text{CMRR} = 20 \log_{10} \left(\frac{R_{out}}{r_e} \right)$$

$$\uparrow \frac{0.026}{\frac{1}{2} (0.198 \text{ mA})} = 0.263 \text{ k}$$

$$R_{out} = r_o \left(1 + \beta \frac{R}{R + (\beta + 1) r_{e3}'} \right) = 606.1 \text{ k} \left(1 + 100 \frac{22 \text{ k}}{22 \text{ k} + 101 (0.13 \text{ k})} \right)$$

$$\uparrow \frac{120 \text{ V}}{0.198 \text{ mA}} = \underline{606.1 \text{ k}}$$

$$\uparrow \frac{0.026}{0.2 \text{ mA}} = 0.13 \text{ k}$$

$$= 3.86 \times 10^4 \text{ k}$$


$$\text{CMRR} = 20 \log_{10} \left(\frac{3.86 \times 10^4 \text{ k}}{0.263 \text{ k}} \right) = \boxed{103.3 \text{ dB}}$$

(10) Problem 5: $I_T = 0.197 \text{ mA}$

$$I_T = \alpha I_E = 0.99 \frac{2.1 - 0.7}{R} = 0.197 \text{ mA}$$

$$R = 7.04 \text{ k}$$
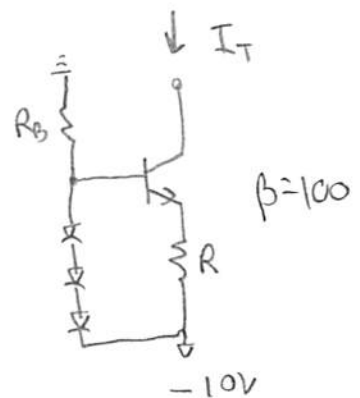
$$\text{choose } \boxed{R = 6.8 \text{ k}}$$



Actual $I_T = .99 \cdot \frac{1.4V}{6.8K} = \underline{0.204 mA}$ ← Problem 5 required $I_T \leq .213 mA$ ✓

↑
0.206 mA

want $I_D = I_S - I_B > 1 mA$

$$\frac{10^{-2.1}}{R_B} - \frac{1}{101} (.206 mA) > 1 mA$$

$$R_B < \frac{10^{-2.1}}{1.002 mA} = 7.88K$$

choose $R_B = 7.5K$

$$CMRR = 20 \log_{10} \left(\frac{R_{out}}{r_e'} \right)$$

↑
 $\frac{.026}{\frac{1}{2} (.204 mA)} = \underline{0.255K}$

$$R_{out} = \left(\frac{120V}{.204 mA} \right) \left[1 + 100 \frac{6.8K}{6.8K + 101 \frac{.026}{.206 mA}} \right] = \underline{2.1 \times 10^4 K}$$

$$CMRR = 20 \log_{10} \left(\frac{2.1 \times 10^4 K}{.255K} \right) = \boxed{98.3 dB}$$