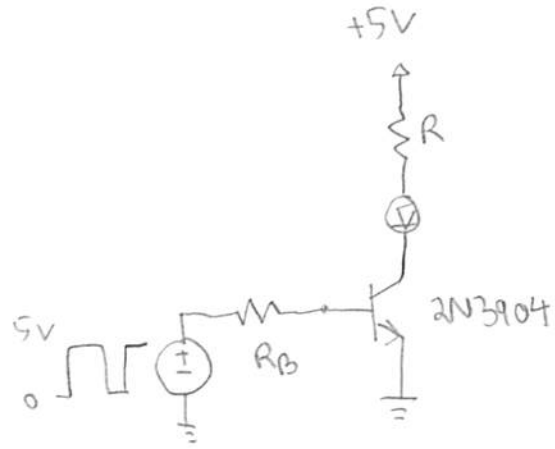


① 2N3904: $\beta_{\min} = 80$

For 50mA, $V_{CE,sat} = 0.3V$
 but use as worst-case for 30mA $V_{BE,sat} = 0.95V$



Actual $I_c = \frac{5 - 2.8}{68\Omega} = 32.4mA$

② Determine R: $5 - .030R - \boxed{2.5} - \boxed{0.3} = 0$

$R = \frac{5 - 2.8}{.030A} = 73.3\Omega$

Choose $R = 68\Omega$

Determine R_B : For hard saturation, $I_B \sim \frac{I_c}{0.1\beta}$

$\frac{5 - 0.95}{R_B} \sim \frac{.030}{0.1 \times 90}$

Don't need exact I_c

Choose $R_B = 1.2k$

$R_B \sim 1215\Omega$


③ $P = I^2 R = (.032)^2 (68) = .0696W$

Include duty cycle: $\boxed{0.75} \times .0696 = 52mW \rightarrow 2P = \underline{104mW}$

$\frac{1}{8}W$ is OK

④ $P = IV = (.032A)(2.5V) = .080W$

instantaneous power

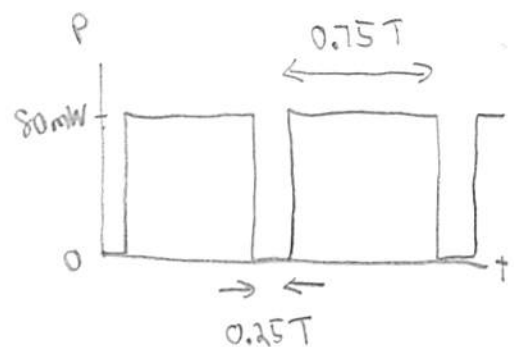


②

$$\textcircled{a} \quad V_+ = V_{cc} \frac{R}{4R} = \frac{1}{4} V_{cc}$$



$$V_- = V_+ = \frac{1}{4} V_{cc}$$

$$I = \frac{V_{sig} - V_-}{R_1} = \frac{V_- - V_{out}}{R_1}$$
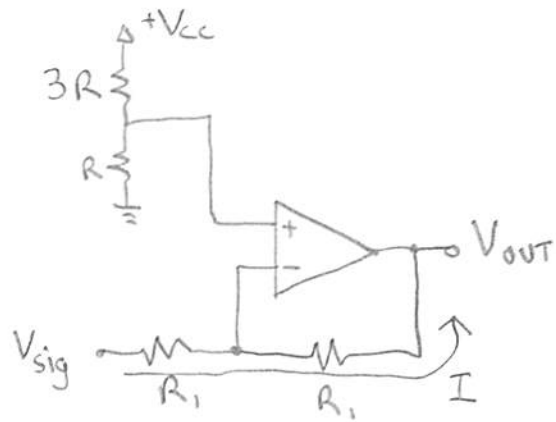
$$V_{out} = 2V_- - V_{sig} = \boxed{\frac{1}{2} V_{cc} - V_{sig}}$$



③

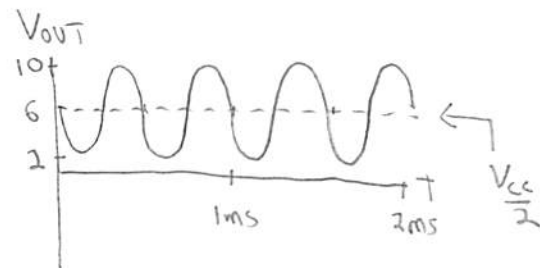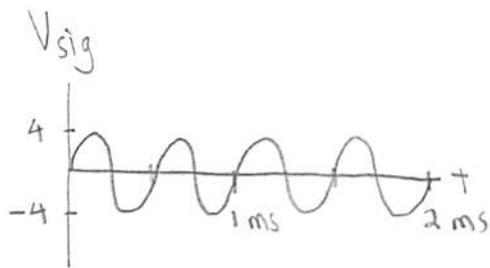

④

$$I = \frac{12V}{4 \times 10K} = 0.3mA$$

$$P = IV = (0.3mA)(12V) = \boxed{3.6mW}$$

③


$$a) V_+ = V_{cc} \frac{R}{22R} = \frac{V_{cc}}{22}$$

$$V_- = V_+$$

$$I = \frac{V_{sig} - V_-}{R_1} = \frac{V_- - V_{out}}{10R_1}$$

$$10V_{sig} = 11V_- - V_{out}$$
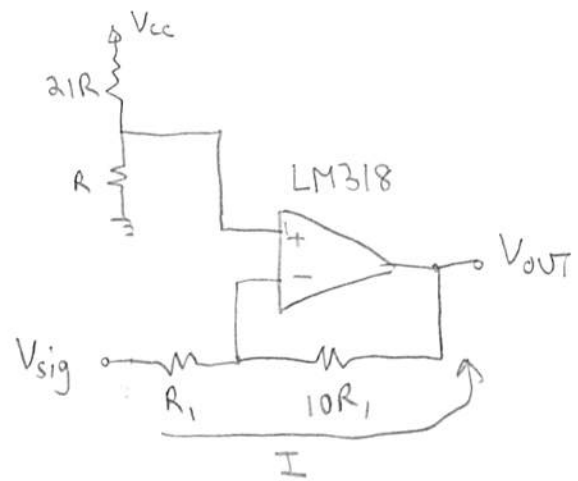
$$V_{out} = \frac{1}{2} V_{cc} - 10V_{sig}$$



$$b) R_{TH(+)} = R \parallel 21R = 10K \parallel 210K = \underline{9.55K}$$

$$G = -\frac{10R_1}{R_1} = \underline{\underline{-10}}$$

$$R_{TH(-)} = R_1 \parallel 10R_1 = 100K \parallel 1000K = \underline{90.9K}$$

For LM318, $I_{IN(BIAS)} = 500nA$, $I_{IN(OS)} = 200nA$, $V_{IN(OS)} = 10mV$
(worst case $T_A = 25^\circ C$)

Input
Bias:
current

$$\Delta V = \boxed{10} \times 500nA \times (90.9K - 9.55K) = 0.407V = \boxed{407mV}$$

↑
|G|

Input
offset
current:

$$\Delta V = 10 \times 200nA \times \frac{90.9K + 9.55K}{2} = 0.101V = \boxed{101mV}$$

Input
Bias
voltage:

$$\Delta V = 10 \times 10mV = \boxed{100mV}$$

c) Main source of error is input bias current

④

a) Determine V_{cc} :

First determine max output!

$$P = 0.5W = \frac{V_{MAX}^2}{2 \times 50\Omega}$$

For sine wave

$$V_{MAX} = \pm 7.07V$$

$$I_{MAX} = \pm \frac{7.07V}{50\Omega}$$

$$= \pm 0.142A$$

$$V_{cc} - V_{E,max} > V_{CE,sat} + 2V$$


↑
↑
↑
↑

$0.4V$
Head room

$$0.142A \times (2 + 50\Omega) = 7.38V$$

$$V_{cc} > 9.78V$$

Choose $V_{cc} = 12V$

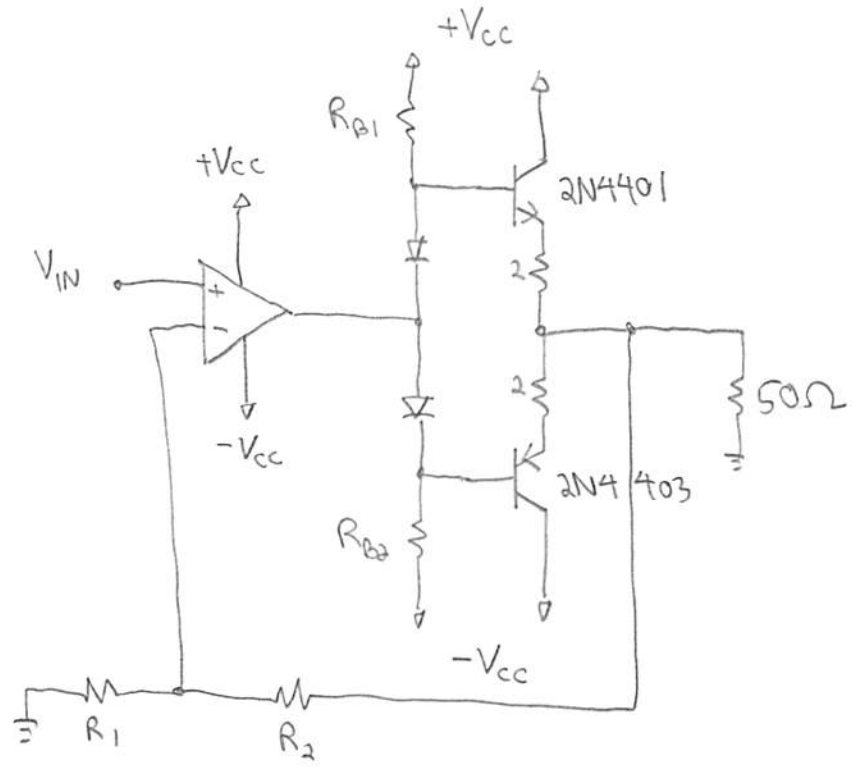

2N4401 @ 150mA is close enough

$$\beta_{min} = 100$$


$$V_{CE,sat} = 0.4V$$

$$V_{BE,sat} = 0.95V$$

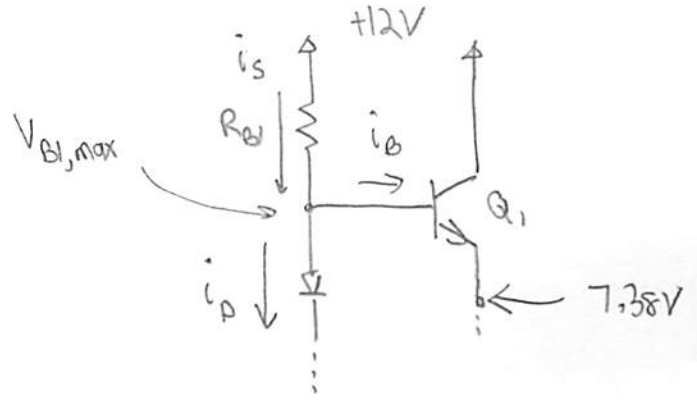b) Determine R_{B1} and R_{B2} :

$$i_{s,min} > i_D + i_{B,max}$$

$$\frac{V_{cc} - V_{BE,max}}{R_{B1}} > 1mA + \frac{142mA}{100+1}$$



$$R_{B1} < \frac{12 - (V_{E,max} + V_{BE,max})}{1\text{mA} + 1.41\text{mA}} = \frac{12 - (7.38 + 0.95)}{2.41\text{mA}} = 1.52\text{k}$$

Choose $R_{B1} = R_{B2} = 1.5\text{k}$

Ⓒ Max $V_{opamp} = V_{B1,max} - 0.7 = (7.38 + 0.95) - 0.7 = \underline{7.63\text{V}}$

Max $I_{opamp} = \frac{7.63\text{V}}{R_{IN,AB}}$

$\Rightarrow R_{IN,AB} = \underbrace{(1500 // 1500)}_{750\Omega} // \underbrace{(100 + 1) \left(\frac{0.026\text{V}}{0.142\text{A}} + 2 + 50 \right)}_{5270.5\Omega} = \underline{656.6\Omega}$

Diagram labels: $\beta+1$, r_e' , R_e , R_L

So, Max $I_{opamp} = \frac{7.63\text{V}}{656.6\Omega} = 0.0116\text{A} \sim \underline{12\text{mA}}$

According to LF356 datasheet: $V_{cc} = 15\text{V}$, $V_o = 12\text{V}_p @ I = \frac{12\text{V}}{1\text{k}} = 12\text{mA}$
 3V difference

So, $V_{cc} = 12\text{V}$, $V_o = 9\text{V} @ 12\text{mA}$

\Rightarrow Op amp is OK!



Ⓓ Desired $G \geq \frac{7.07\text{V}}{0.25\text{V}} = 28.3$

For non-inverting amplifier, $G = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} \geq 27.3$

Choose $R_2 = 330\text{k}$
 $R_1 = 12\text{k}$
 $(G = 27.5)$

© Heat sink needed?
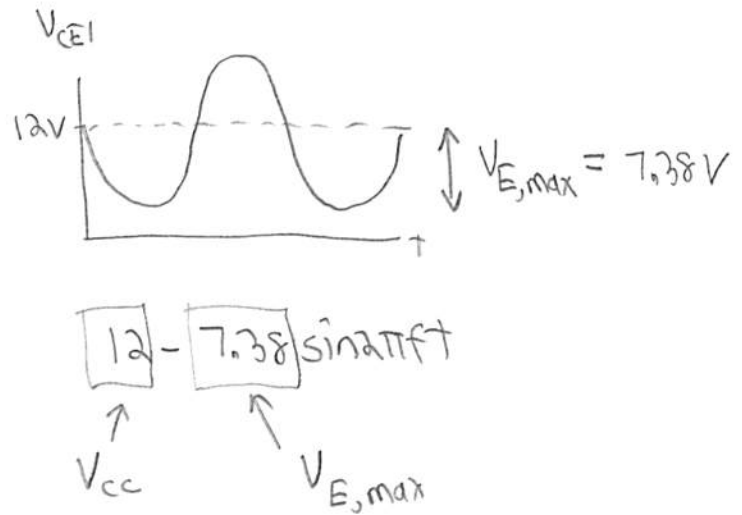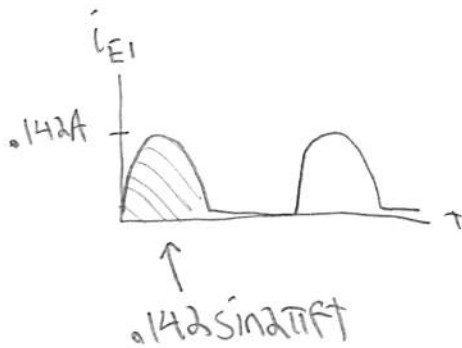
$$P_{MAX} = 625 \text{ mW} - (5 \text{ mW}/^\circ\text{C}) (60^\circ - 25^\circ\text{C}) = \underline{\underline{450 \text{ mW}}}$$



$$P = (0.142)(12) \sin(2\pi f t) - (0.142)(7.38) \sin^2(2\pi f t)$$

$$\langle P \rangle = 1.7 \underbrace{\frac{1}{T} \int_0^{T/2} \sin(2\pi f t) dt}_{1/\pi} - 1.05 \underbrace{\frac{1}{T} \int_0^{T/2} \sin^2(2\pi f t) dt}_{1/4}$$


$$= 1.7 \times \frac{1}{\pi} - 1.05 \times \frac{1}{4} = 0.166 \text{ W}$$

$$2\langle P \rangle = \underline{\underline{332 \text{ mW}}} < P_{MAX} = 450 \text{ mW} \quad \checkmark$$

NO heat sinks needed

5

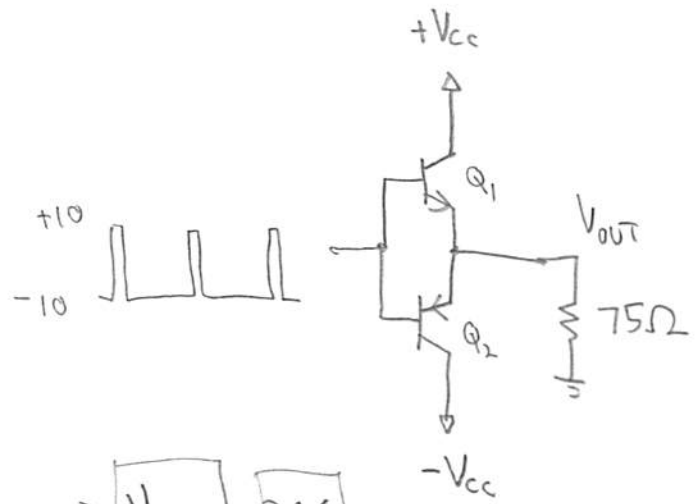a) $V_{OUT} = V_{BI} - V_{BE}$
 $= 10 - 0.75$
 $= \underline{9.25V}$







For active mode, $V_{cc} - V_{E,max} > V_{CE,sat} + 2V$
 (Note: $V_{CE,sat} = 0.4V$, $2V$ is headroom)

$V_{cc} > 9.25 + 0.4 + 2$

$> 11.65V \Rightarrow$ choose $V_{cc} = 12V$

b) $|I_{MAX}| = \frac{9.25V}{75\Omega} = .1233A = \underline{123.3mA}$

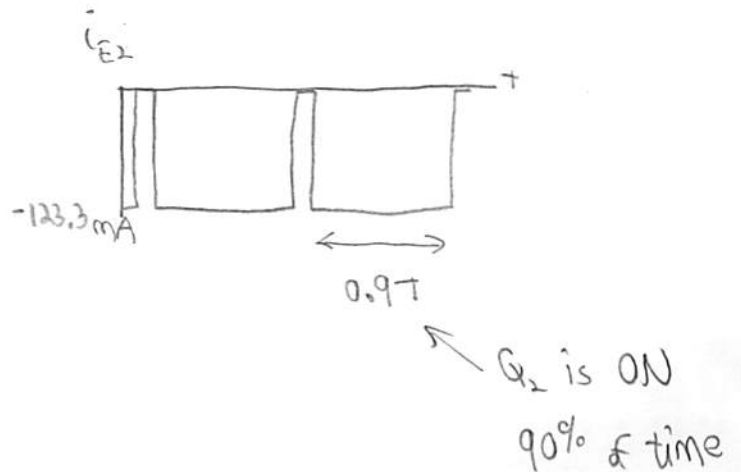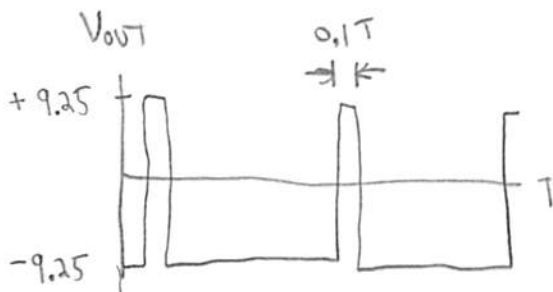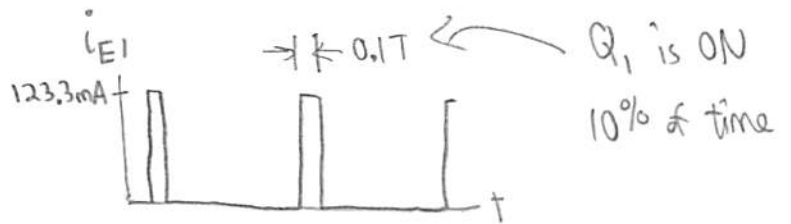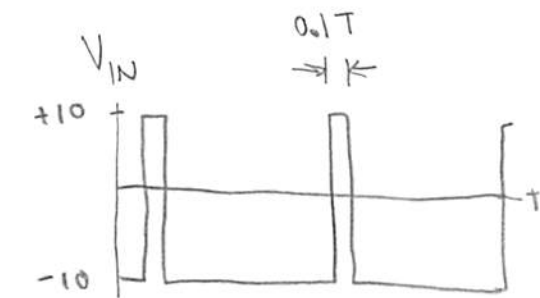

$$\textcircled{c} \quad |V_{CE}| = |12 - 9.25| = 2.75 \text{ V}$$

$$Q_1: \langle P_1 \rangle = \boxed{0.10} \times (.1233 \text{ A})(2.75 \text{ V}) = .0339 \text{ W} = \boxed{34 \text{ mW}}$$

↑
 Q_1 duty cycle

$$Q_2: \langle P_2 \rangle = \boxed{0.90} \times (.1233 \text{ A})(2.75 \text{ V}) = 0.305 \text{ W} = \boxed{305 \text{ mW}}$$

↑
 Q_2 duty cycle