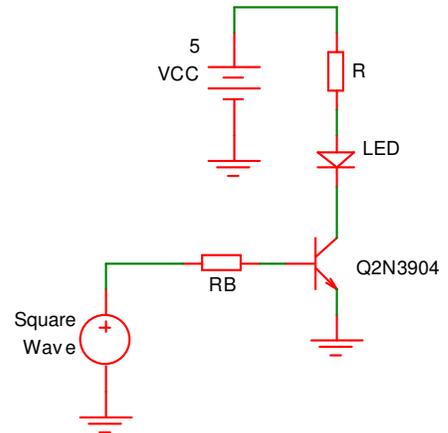


ECE 363 EXAM 1 Practice Problems

Problem #1: Transistor Switch Design

Design a npn BJT switch to drive a green LED ($V_F = 2.5\text{ V}$) with 30 mA of current. The control signal is 0 to +5V square wave with 75% duty cycle, and $V_{CC} = +5\text{ V}$. Use a 2N3904 transistor – check the datasheet (see attachment) for worst-case values of β , $V_{BE,sat}$, and $V_{CE,sat}$.


- Choose standard 5% resistor values (see attachment for table) for R and R_B . Choose R such that I_{LED} is NOT $< 30\text{ mA}$.
- Would you use a 1/8, 1/4, or 1/2 watt resistor for R ?
- Sketch the LED power dissipation. Label important features!



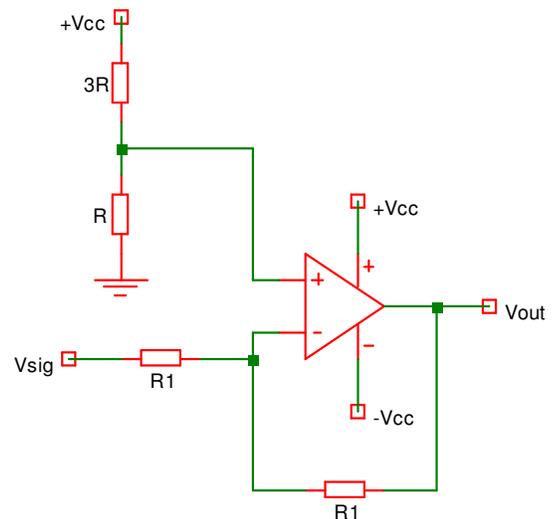Problem #2: Op Amp Analysis

Consider a level-shifting amplifier. The (+) input is connected to a voltage divider consisting of $3R$ and R . The op amp feedback network consists of two identical resistors R_1 .


- Use the Golden Rules to show that $V_{OUT} = 0.5V_{CC} - V_{SIG}$. Show all work.
- Let $R = 10\text{ kohm}$, $R_1 = 100\text{ kohm}$, $V_{CC} = 12\text{V}$. The input V_{SIG} is a $8V_{PP}$ sine wave at 2 kHz. Sketch the input and output voltages over a 2 ms interval. Label important features!
- Compute the total power dissipation in the voltage divider formed by $3R$ and R .



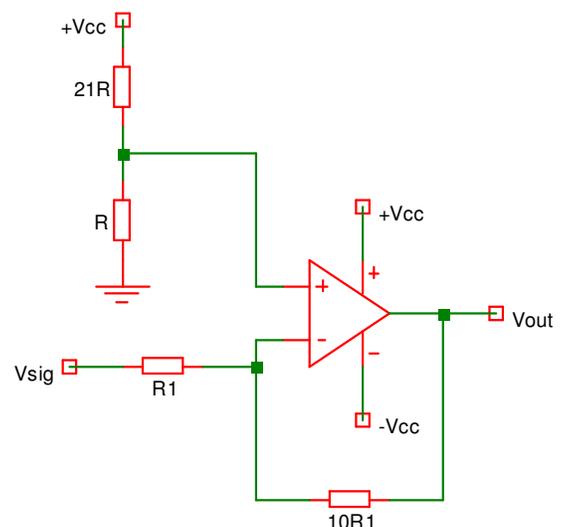Problem #3: Op Amp Output Error

Consider a level-shifting amplifier using a LM318 op amp. The (+) input is connected to a voltage divider consisting of $21R$ and R . The op amp feedback network consists of two resistors R_1 and $R_2 = 10R_1$.


- Use the Golden Rules to show that $V_{OUT} = 0.5V_{CC} - 10V_{IN}$. Show all work.
- Let $R = 10\text{ kohm}$ and $R_1 = 100\text{ kohm}$. When $V_{SIG} = 0$, the output is ideally $V_{OUT} = 0.5V_{CC}$. In reality, the output is $V_{OUT} = 0.5V_{CC} + \Delta V$. Given the worst-case values for $I_{in(bias)}$, $I_{in(offset)}$, and $V_{in(offset)}$, compute ΔV due to each parameter.
- Is the main source of error due to input bias current, input offset current, or input offset voltage?



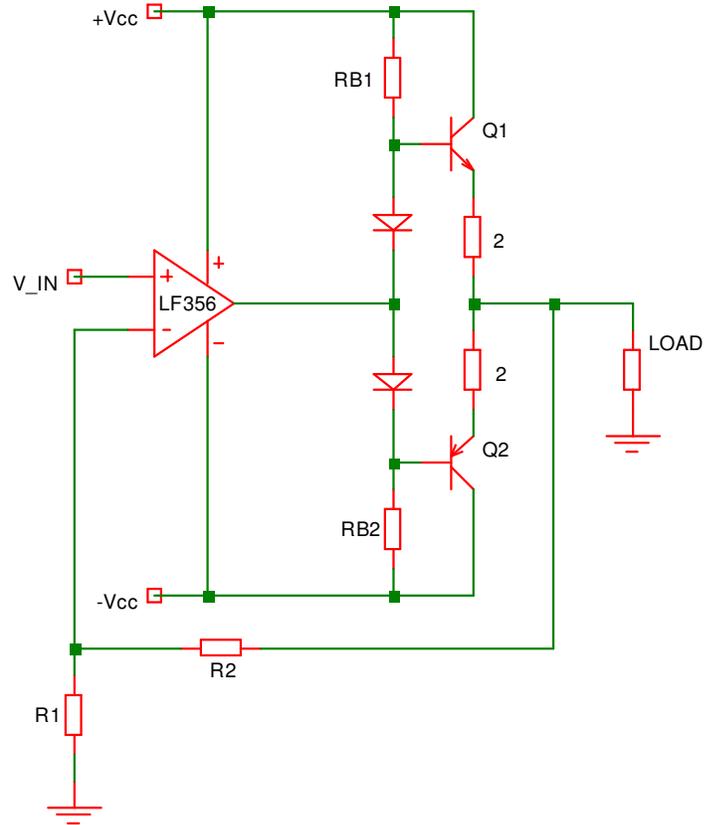Problem #4: Class AB Design

Design a non-inverting voltage amplifier to drive up to 500 mW (or slightly higher) into a 50 ohm load. The input signal is a sine wave with a maximum amplitude of $0.5V_{PP}$. The suggested schematic is shown in the figure, where an LF356 op amp is used. Q1 is a 2N4401, and Q2 is a 2N4403.

- V_{CC} must be 4.5, 6, 9, or 12V. Choose one and explain why.
- Choose R_{B1} and R_{B2} . Pick standard 5% values.
- Show that the op amp can provide the required output voltage and current.
- Choose R_1 and R_2 . Remember that R_1 should be more than a few kohm and R_2 is typically less than 1 Mohm. Pick standard 5% values.
- Do your transistors need heat sinks? Use $T_A = 60^\circ\text{C}$ for your power rating calculations.



Problem #5: Current Booster Analysis

Suppose V_{IN} is a 10% duty cycle square wave that alternates between +10V (HIGH) and -10V (LOW). The load is $R_L = 75 \text{ ohm}$. Both transistors have $V_{BE,ON} = 0.75\text{V}$, $V_{CE,SAT} = 0.4\text{V}$, and $\beta = 80$.

- You must choose between $V_{CC} = 9, 12,$ or 15V . Which is the best choice? Show all work.
- Sketch V_{IN} , V_{OUT} , i_{E1} (Q1 emitter current), and i_{E2} (Q2 emitter current). Label important features.
- Given your choice of V_{CC} , estimate the power dissipation in Q1 and Q2.

