

Lab 3a – Audio Amplifier Design and Prototyping

GOAL

The overall goal of Lab3 is to build a battery powered audio amplifier.

OBJECTIVES

Lab3a: (1) Design an audio amplifier using an op amp and Class AB stage.

(2) Build a prototype on a breadboard.

(3) Test your prototype to validate your design.

Lab3b: (1) Build a soldered version.

(2) Demonstrate a working amplifier.

GENERAL GUIDELINES

- 1) Each student builds his/her own circuits.
- 2) Test stations (e.g. oscilloscope, computer) must be shared.
- 3) You are allowed (even encouraged) to help each other. Of course, Prof. Hedrick will be around to provide assistance as well.
- 4) **Use neat wiring for your circuits! Starting in Lab 2, a messy circuit will cost you 1 pt (out of 10 for the demo).**
- 5) Keep your circuit components organized to make it easier to do the subsequent labs!
- 6) Each student must turn in his/her own lab report. See the course website for the template.

Honor Code Compliance: You must turn in your own work! Blatant duplication of circuit analysis, design, simulations, and/or lab reports will result in ZERO points and possible reporting to the Honor Council.

NOTE: There will be one lab exam near the end of the term. The lab exam will test each student's ability to use Multisim and prototype a circuit.

PARTS AND MATERIALS

- Power supply, scope, scope probes, function generator, BNC+alligator clips, banana cables
- Lab kit containing breadboard, wires, wire stripper, and other tools
- LF411 op amp
- Npn and pnp transistors (you decide)
- Resistors: You choose! (a whole bunch)
 - 16 ohm (brown/blue/black) (one)
- Capacitors: 0.1 uF ceramic (eight)
 - ??? uF electrolytic (four)
- 16 ohm speaker (one)
- Audio cable (one)
- AA batteries (six)

- AA 3-pack battery holder

(two)

INTRODUCTION

The overall goal of Lab3 (two weeks) is to build a battery-powered audio amplifier. You get to keep the soldered version of your amplifier (includes audio cable and speaker)! The overall specifications are the following:

- 1) $\pm V_{CC} = \pm 4.5V$
- 2) Overall voltage gain ≥ 10 from 400 Hz to 4 kHz
- 3) Input impedance $R_{IN} \geq 50 k\Omega$
- 4) Drive a 16Ω speaker with up to 125 mW.

PART 1: AMPLIFIER DESIGN

NOTE: If you have already finished PreLab3, then you can jump to Part 2 of the lab ...

➤ **Show your calculations and simulations to Prof. Hedrick (2 out of 10 pts of lab demo grade).**


Your design calculations should include the following:

- Choice of Q1 (2N3904, 2N4401, or TIP31A). The TIP31A is a power transistor (datasheet on course website).
- The pnp version of the above transistors are (2N3906, 2N4403, or TIP32A).
- Adequate power rating of Q1 (assume Q2 is the same).
- Choice of RB1 and RB2 (choose standard value).
- Confirmation that the LF411 will provide the desired max output with $\pm V_{CC} = \pm 4.5V$.
- Choice of (R_{IN} , R1, R2) for non-inverting amplifier
- Choice of (R1, R2) for inverting amplifier.
- Choice of C_{IN} (choose standard value). Note that $f_C = 1/(2\pi R_{IN} C_{IN})$.
- Choice of C_{OUT} (choose standard value). Note that $f_C = 1/(2\pi R_{LOAD} C_{OUT})$.
- Simetrix simulation of the entire circuit.
 - Provide the schematic.
 - Perform transient simulations at 400 Hz, 1 kHz, and 4 kHz.
 - Provide waveforms of V_{IN} and V_{OUT} for all three cases.
 - Compute the voltage gain V_{OUT}/V_{IN} for all three cases.
 - Measure the input impedance Z_{IN} for all three cases. Remember that $Z_{IN} = V_{IN}/I_{IN}$.
 - Make sure your simulation results satisfy the design requirements!

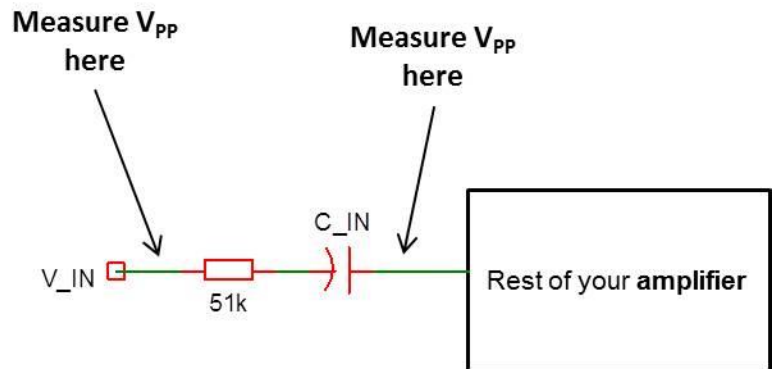PART 2: PROTOTYPE

This is where you validate your design.

- Circuit construction
 - Your breadboard circuit will be your template for soldering, so think carefully about where you place components and how they are wired!
 - Be NEAT!
 - Try to minimize the number of criss-crossing wires (OK to have a few).
 - Remember to include 0.1 μF bypass capacitors for the op amp and push-pull transistors!
- Circuit testing
 - Use a 16 ohm resistor as the test load.
 - Configure the Agilent function generator to “High Z” output.
 - Think about how to test your circuit’s ability to produce the desired V_{OUT} (4V_{PP} into 16 ohm). Your prelab simulations should help here.
 - Go ahead and configure the Agilent function generator and oscilloscope to measure V_{OUT} at 400 Hz, 1 kHz, and 4 kHz.
 - Determine the voltage gain at all three frequencies.
 - Does your gain satisfy the design requirement?
 - Record a snapshot of your circuit with a 1 kHz signal.
 - Measure R_{IN} using the following method:
 - Insert a 51 kohm resistor between the function generator and the input coupling capacitor.
 - Configure V_{IN} to be 4 kHz.
 - Measure the peak-to-peak voltage at the two locations in the figure.
 - Assuming C_{IN} is a perfect short, figure out R_{IN} by the voltage divider effect.
 - After you are done measuring R_{IN} , remove the 51 kohm resistor.



- Demo scope traces of max V_{OUT} (400 Hz, 1 kHz, and 4 kHz sine wave) to Prof. Hedrick (4 out of 10 pts of lab demo grade).
- Present your measurements (gain and R_{IN}) to Prof. Hedrick (4 out of 10 pts of lab demo grade).

(End of Lab 3a)