

- AA batteries (three)
- AA 3-pack battery holder (one)

INTRODUCTION

The overall goal of Lab6 (two weeks) is to build a battery-powered LED night light. The LED brightness depends on the ambient light level. You get to keep the soldered version of your circuit (includes battery pack)! The overall specifications are the following:

- 1) $+V_{CC} = 4.5 \text{ V}$ (three AA batteries) and $-V_{EE} = 0 \text{ V}$
- 2) Lamp is a single white LED
- 3) Automatic dimmer: A light sensor (phototransistor) measures the ambient light level. High ambient light will cause the LED to turn off. Low ambient light will cause the LED to become bright.
- 4) LED dimming is performed with PWM, where the PWM signal is implemented with a triangle wave generator and comparator.

Some other circuit features are the following:

- 1) Use a LM358 chip, which contains TWO op amps (suitable for single-supply operation).
- 2) Use a LM311 voltage comparator (suitable for single-supply operation with output current up to 50 mA).
- 3) The phototransistor is the SFH3310, which is good for detecting visible wavelengths.
- 4) The white LED is the C503B-WAN made by Cree.
- 5) The peak current of the LED should be $I_{LED} \approx 20 \text{ mA}$ (can be slightly higher or lower).
- 6) You can directly drive the LED with the LM311 comparator – this keeps the parts count low (nice!).

PART 1: BREADBOARD PROTOTYPE


It is a good idea to confirm your breadboarded amplifier still works!

- Clean up the wiring – this produces an easier-to-follow “blueprint” for your soldering.
- Hook up $V_{CC} = +4.5\text{V}$
- Use the scope to measure the triangle wave.
- Wave your hand across the phototransistor to change the LED brightness.
- You do NOT have to demo your completed prototype.
- Professor Hedrick can provide assistance if your prototype is no longer working and you cannot figure out the reason.

PART 2: SOLDERING

When you first solder your circuit, you should do the following:


- Use the benchtop supply to power your circuit (see right figure).
- Use the 8-pin IC sockets for the LM358 op amp and LM311 comparator. You can then plug in the actual chips into these sockets.

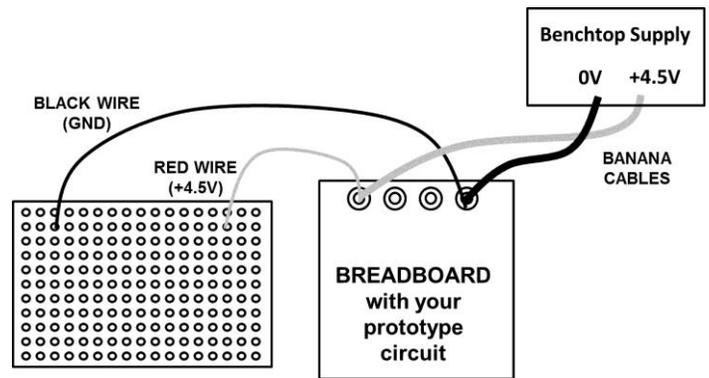

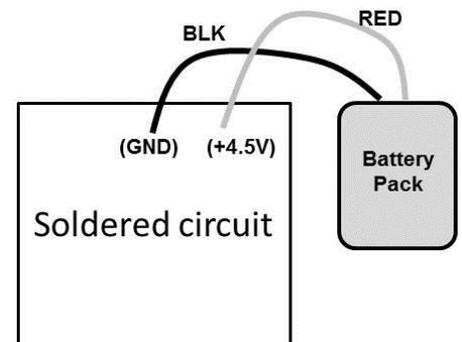PART 3: TESTING

- Make the following two tests:
 - 1) Use the scope to confirm the triangle wave peak-to-peak amplitude and frequency.
 - 2) Wave your hand across the phototransistor to change the LED brightness.
- Once you have confirmed that your soldered circuit works, replace the benchtop supply with the battery pack.
 - 1) Record a scope trace of the triangle wave output.
 - 2) Measure the peak-to-peak amplitude and frequency.

➤ **Demo your battery-powered LED night light to Professor Hedrick.**



Extra time:

- There is a chance you will need extra time. There will be some soldering irons in N108 for the next week.

(End of Lab 5 part C)